

# Bipolar Junction Transistors

Peng Mei

Department of Electronic Systems

Email: [mei@es.aau.dk](mailto:mei@es.aau.dk)



AALBORG UNIVERSITY  
DENMARK





## Learning objectives:

- Transistor-based amplifier
- Lab session



Using a diagram to analyze a BJT amplification circuit:

First step: draw the DC circuit

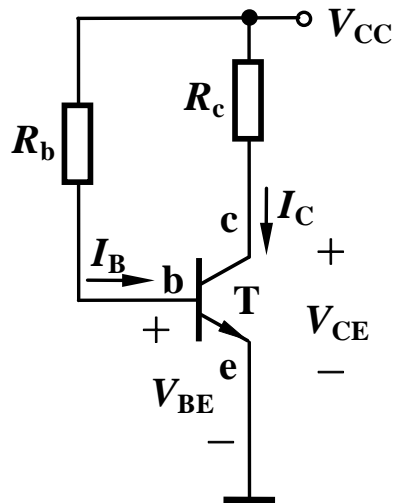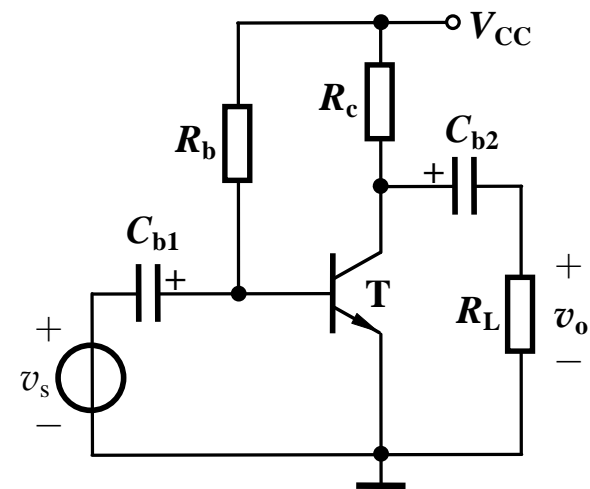

Input  $i - v$  curve:



$$v_{BE} = V_{CC} - i_B R_b$$

Output  $i - v$  curve:
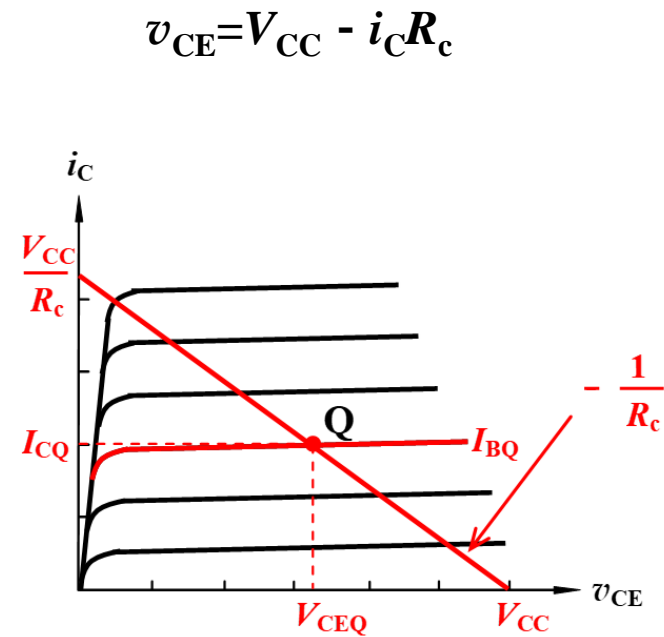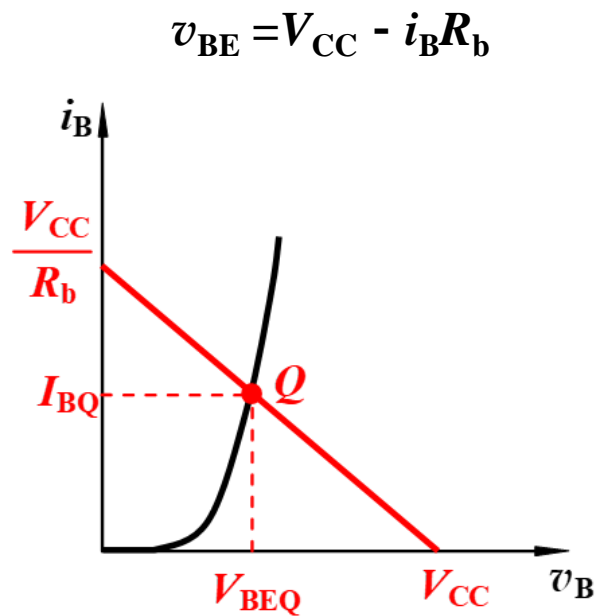
$$v_{CE} = V_{CC} - i_C R_c$$


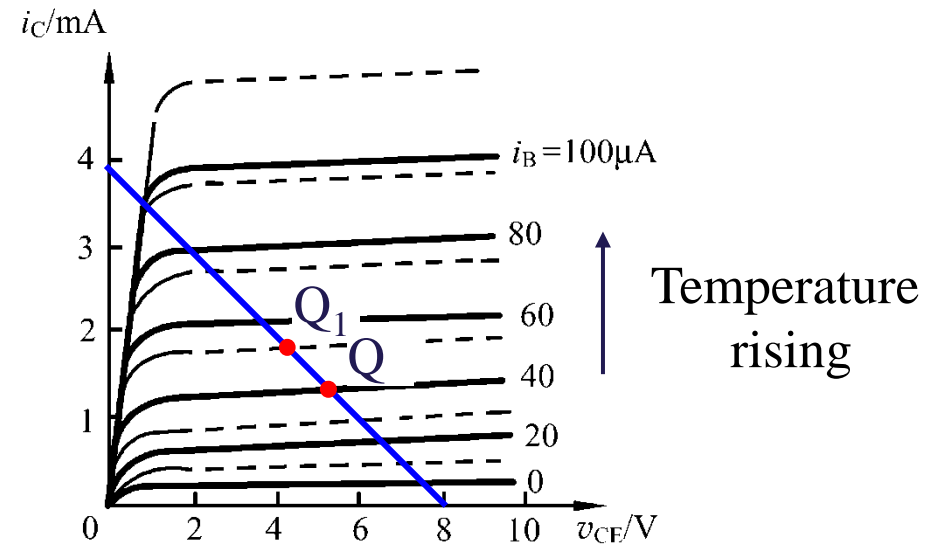


Diagram analysis of static operating point :

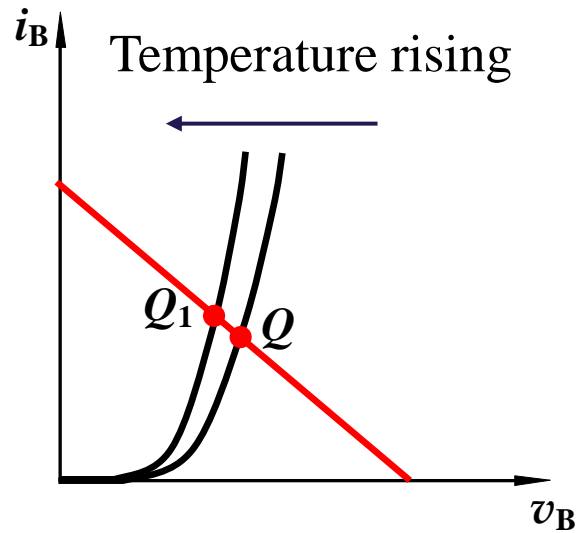





Effects of temperature on Q point :






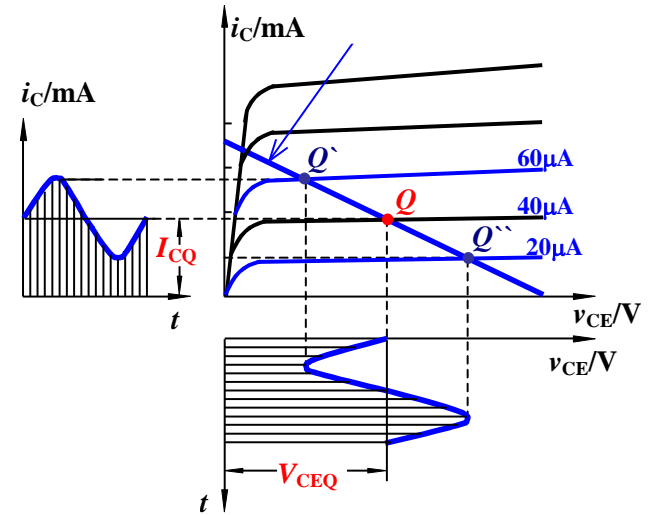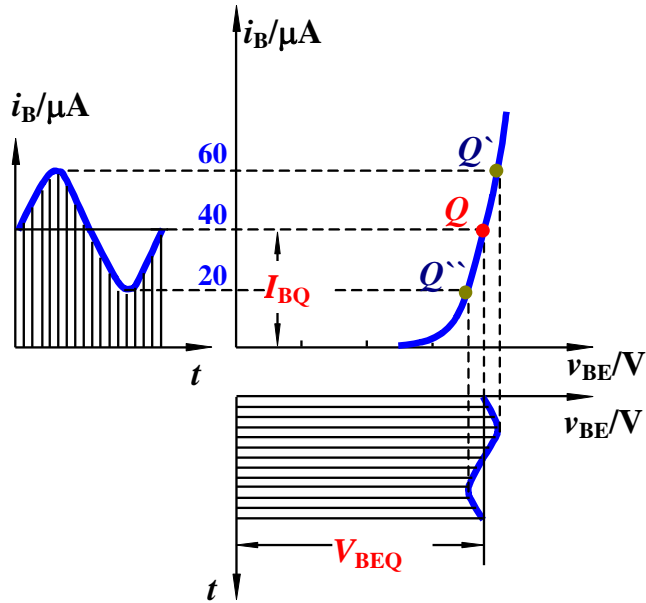The effects of Q point on waveform distortion:







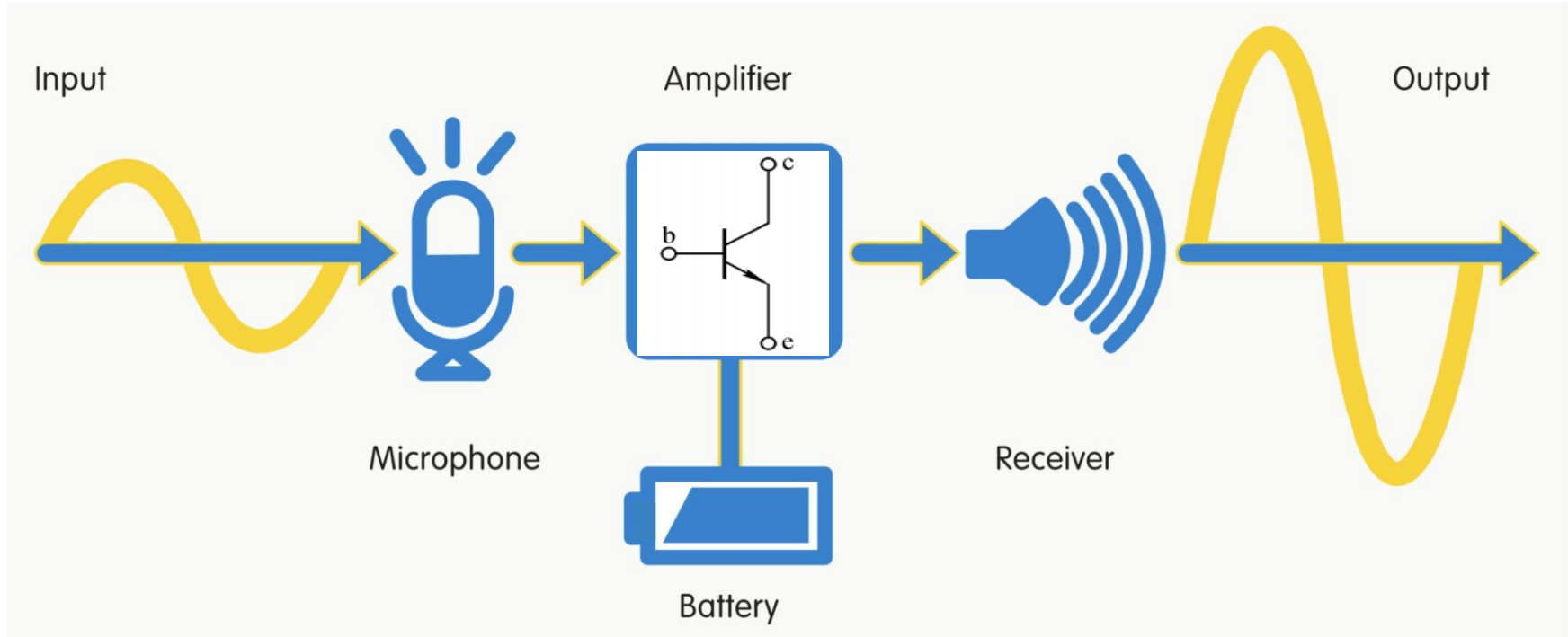







For the AC signal diagram:

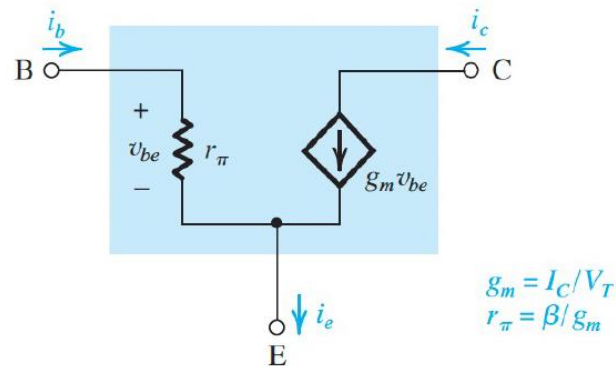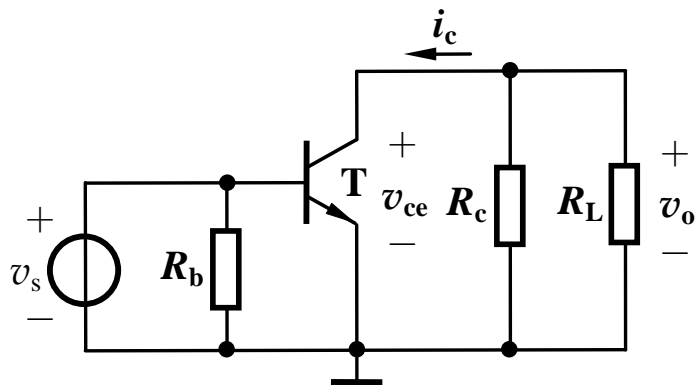

Small-signal model of a BJT

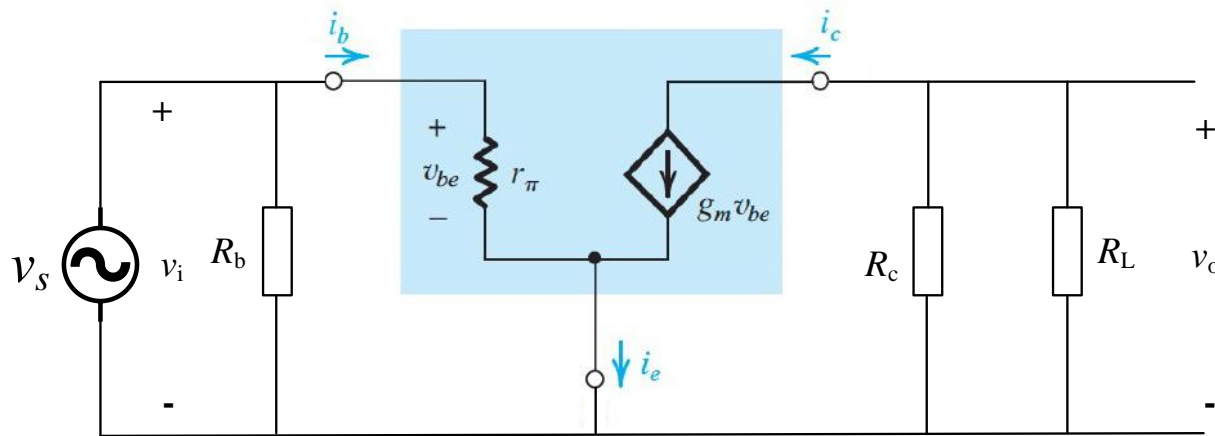

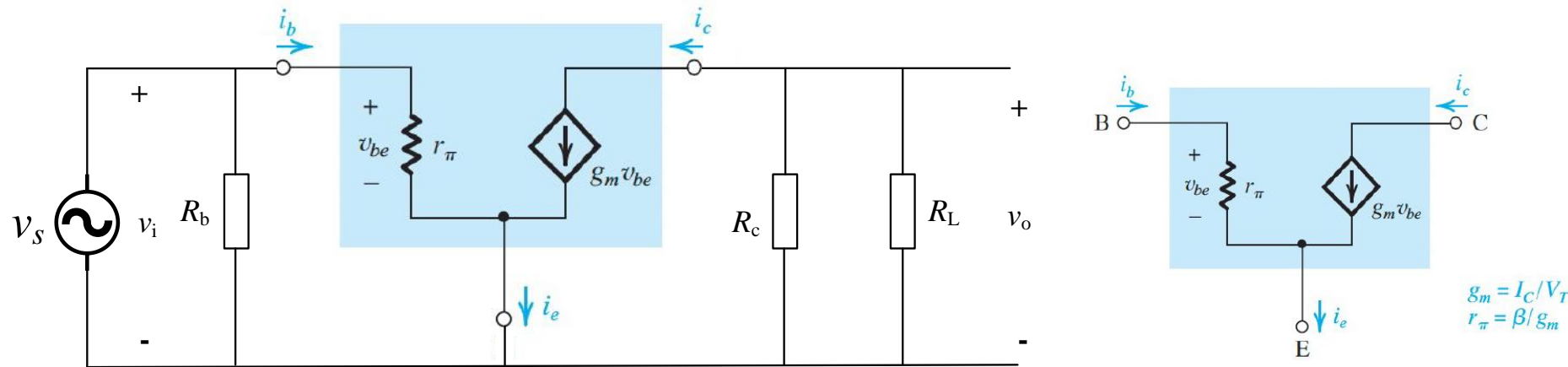

$$v_i = v_{be} = i_b r_\pi$$

$$v_o = -i_c \cdot \left( \frac{R_c R_L}{R_c + R_L} \right)$$


$$i_c = g_m v_{be} = g_m i_b r_\pi = g_m i_b \beta / g_m$$
$$= \beta i_b$$

AC small-signal amplification coefficient:

$$A_V = \frac{v_o}{v_i} = \frac{-i_c \cdot \left( \frac{R_c R_L}{R_c + R_L} \right)}{i_b r_\pi} = -\frac{\beta \cdot R_c R_L}{r_\pi (R_c + R_L)}$$




## Input and output impedances:

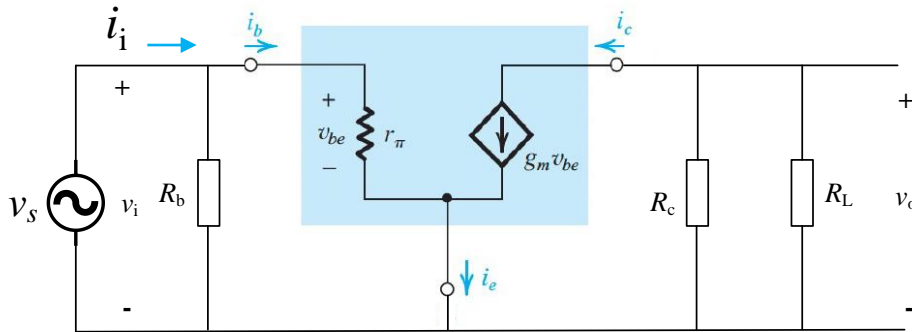

Input impedance:
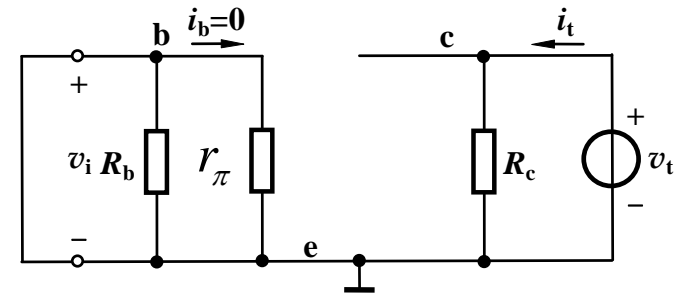
$$R_i = \frac{v_i}{i_i} = \frac{R_b r_\pi}{R_b + r_\pi}$$



Output impedance:


$$R_o = \left. \frac{v_t}{i_t} \right|_{v_s=0, R_L=\infty} = R_c$$

$R_L$  is replaced with a voltage source ( $v_t$ ):

Input source is short:



For a more complicated circuit:

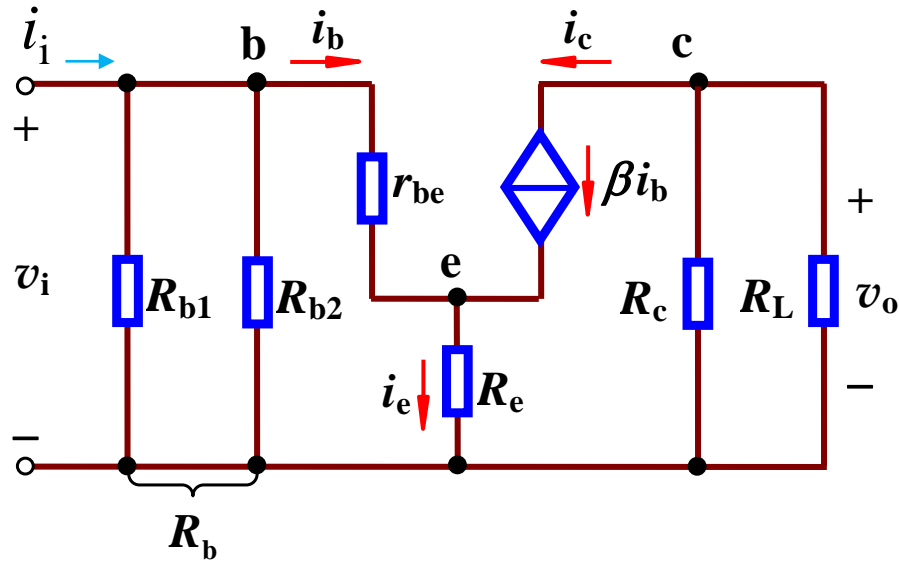

Input impedance:

$$R_i = \frac{v_i}{i_i}$$


$$R_i = R_{b1} \parallel R_{b2} \parallel [r_{be} + (1 + \beta)R_e]$$

Output impedance:

$$R_o = \left. \frac{v_t}{i_t} \right|_{v_s=0, R_L=\infty} \approx R_c$$





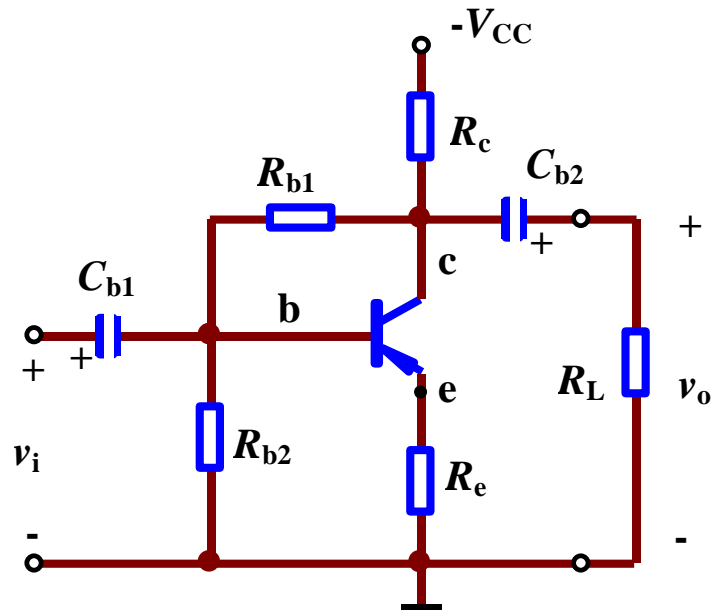
Please draw the corresponding small-signal equivalent circuit:





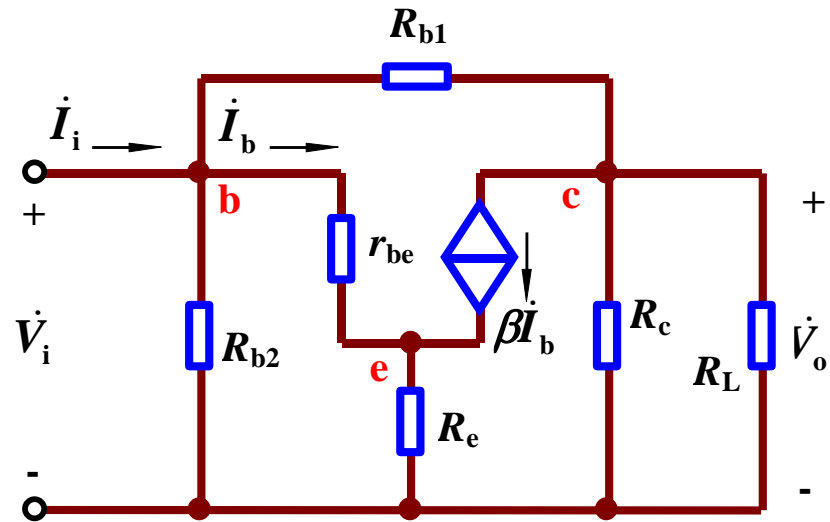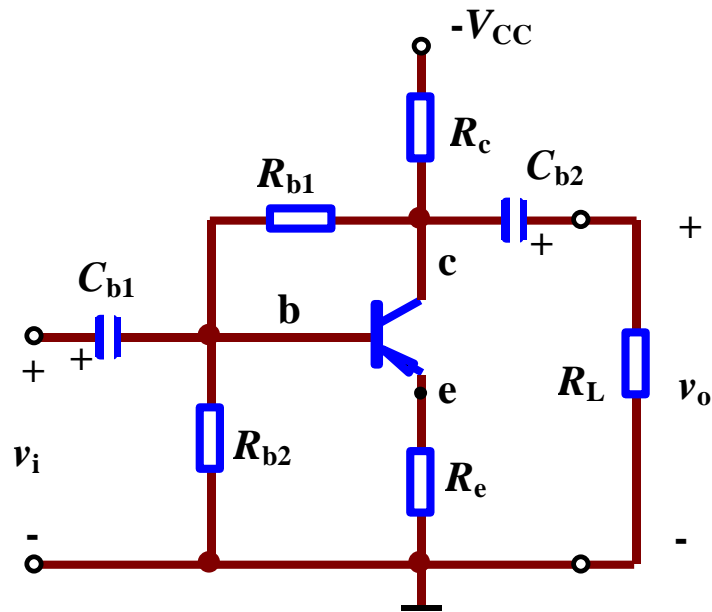Please draw the corresponding small-signal equivalent circuit:



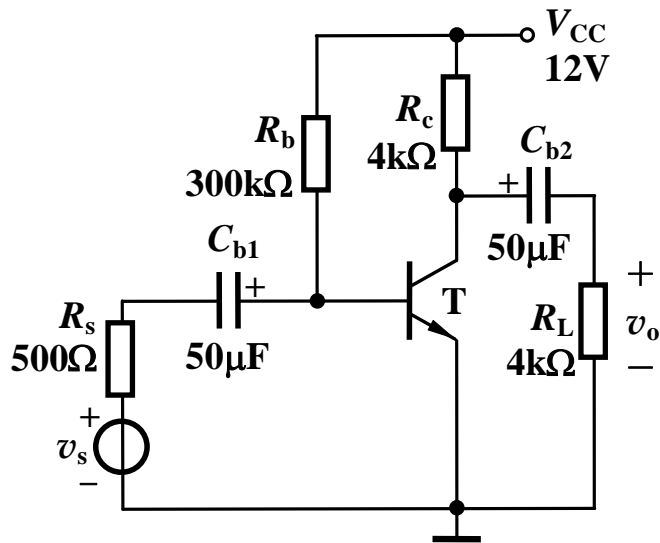


$$\beta = 50$$

a. Calculate Q point ?



b. Calculate AC small-signal amplification coefficient ?

Draw the small-signal equivalent circuit

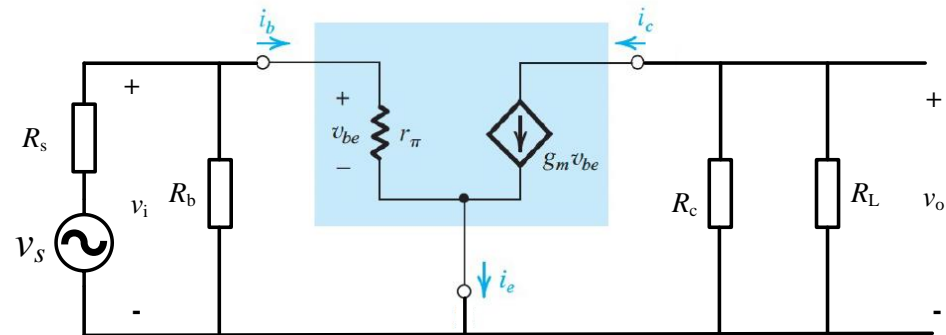



For a more complicated BJT circuit:

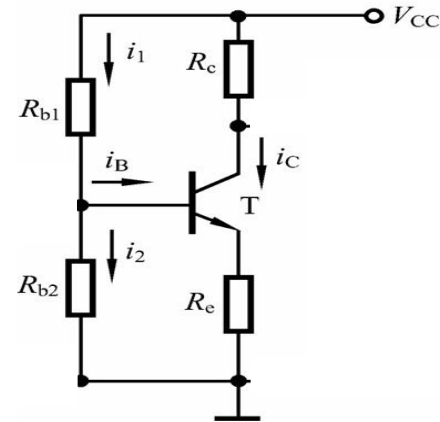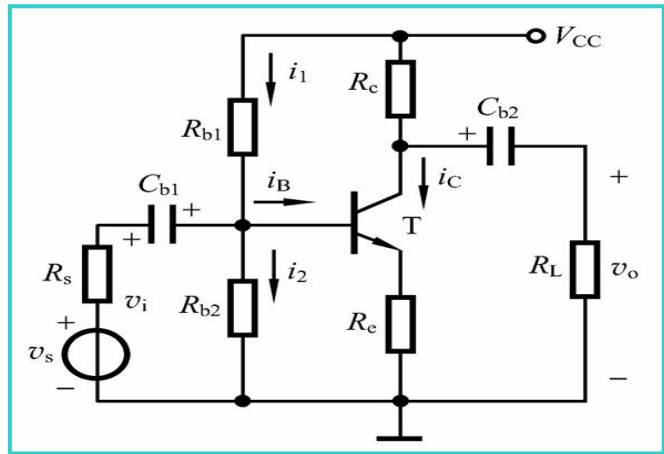

DC circuit

Q point:

$$V_{BQ} \approx \frac{R_{b2}}{R_{b1} + R_{b2}} \cdot V_{CC}$$

$$I_{CQ} \approx I_{EQ} = \frac{V_B - V_{BEQ}}{R_e}$$



$$I_{BQ} = \frac{I_{CQ}}{\beta}$$

$$V_{CEQ} \approx V_{CC} - I_{CQ}(R_c + R_e)$$





For a more complicated BJT circuit:

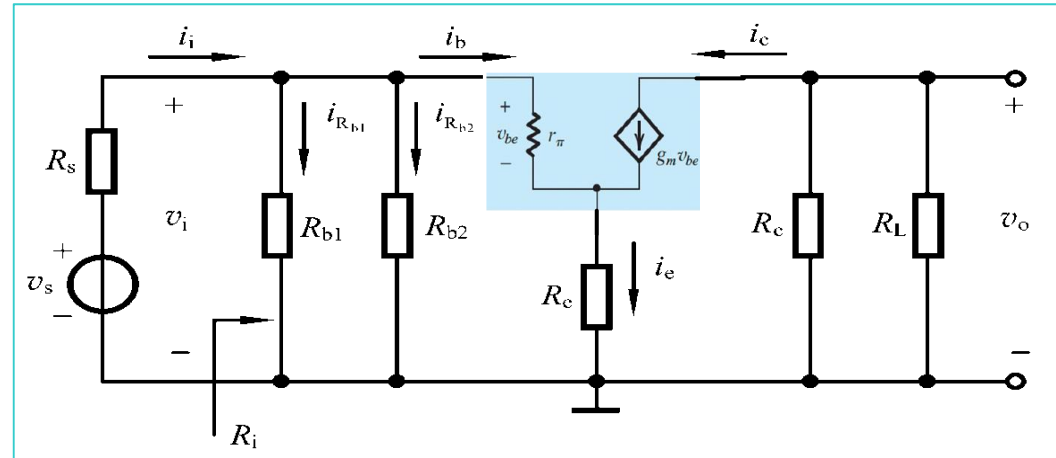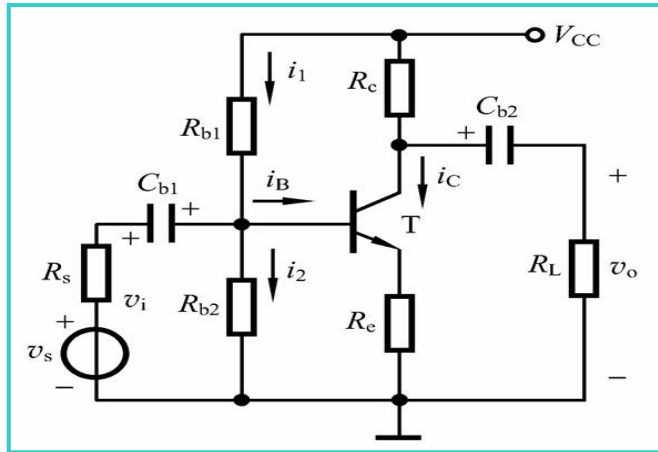

AC circuit

$$v_i = v_{be} + i_e R_e = i_b r_\pi + i_e R_e = i_b r_\pi + (1 + \beta) i_b R_e$$


$$i_c = g_m v_{be} = g_m i_b r_\pi = g_m i_b \beta / g_m \\ = \beta i_b$$

$$v_o = -i_c \cdot \left( \frac{R_c R_L}{R_c + R_L} \right)$$

$$A_V = \frac{v_o}{v_i} = \frac{-i_c \cdot \left( \frac{R_c R_L}{R_c + R_L} \right)}{i_b r_\pi + (1 + \beta) i_b R_e} = - \frac{\beta \cdot R_c R_L}{(r_\pi + (1 + \beta) R_e)(R_c + R_L)}$$



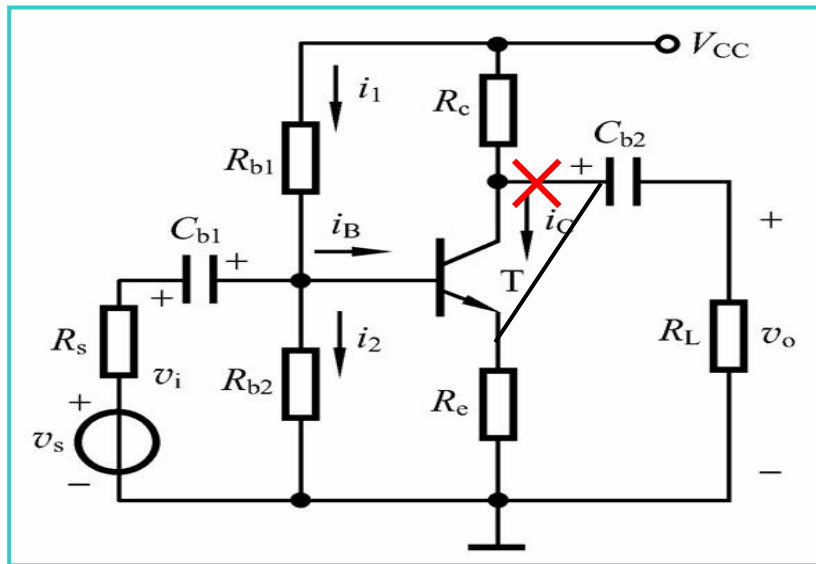
Formulate the voltage amplification coefficient:



*Interesting results found here!*




## Lab session:

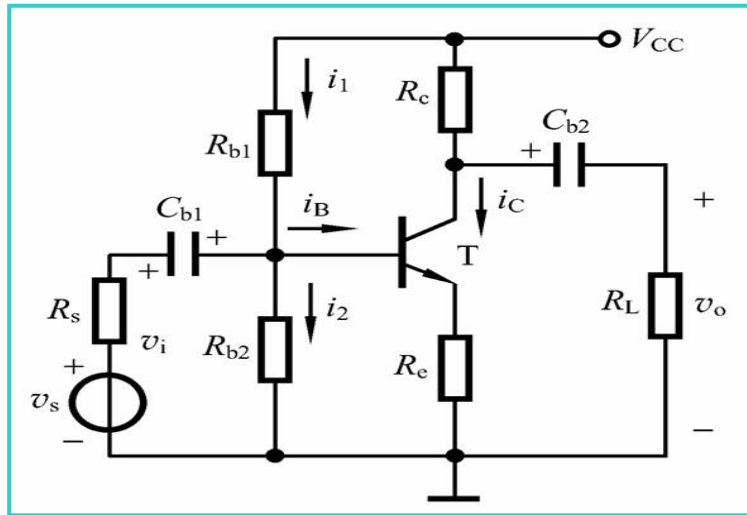

$V_{CC} = 15 \text{ V}$ ,  $R_{b1} = 309 \text{ k}\Omega$ ,  $R_{b2} = 110 \text{ k}\Omega$ ,  
 $R_e = 3.01 \text{ k}\Omega$ ,  $R_c = 6.98 \text{ k}\Omega$ ,  $C_{b1} = 1 \text{ }\mu\text{F}$ ,  
 $C_{b2} = 1 \text{ }\mu\text{F}$ ,  $R_L = 10 \text{ k}\Omega$ .




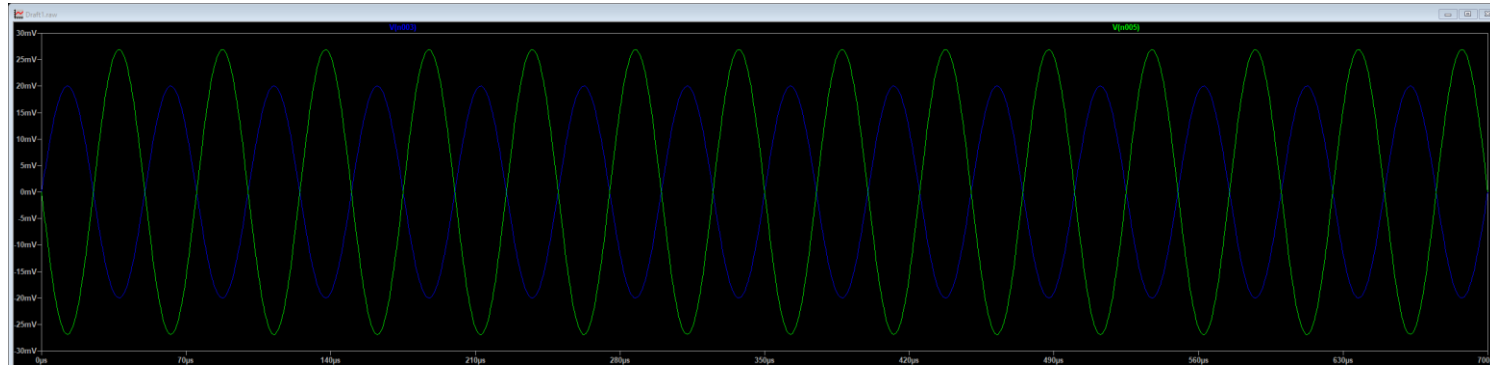If  $v_s = 20\sin(2\pi f)$  mV,  $f = 20$  kHz, please measure  $v_i$  and  $v_o$ , and calculate the amplitude amplification coefficient  $A_v$ .






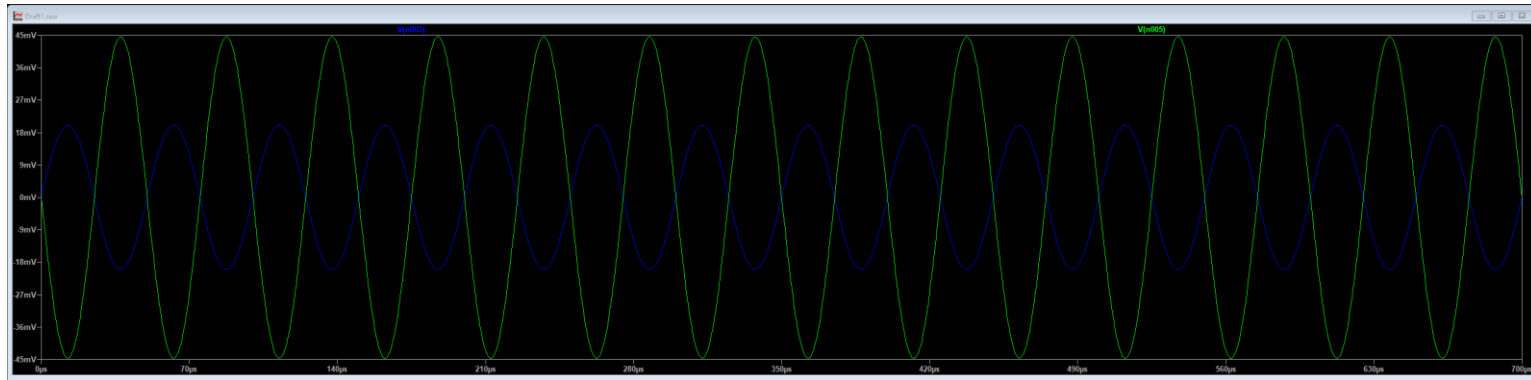If  $R_L = 300 \text{ k}\Omega$ , please please measure  $v_i$  and  $v_o$ , and calculate the amplitude amplification coefficient  $A_v$ .





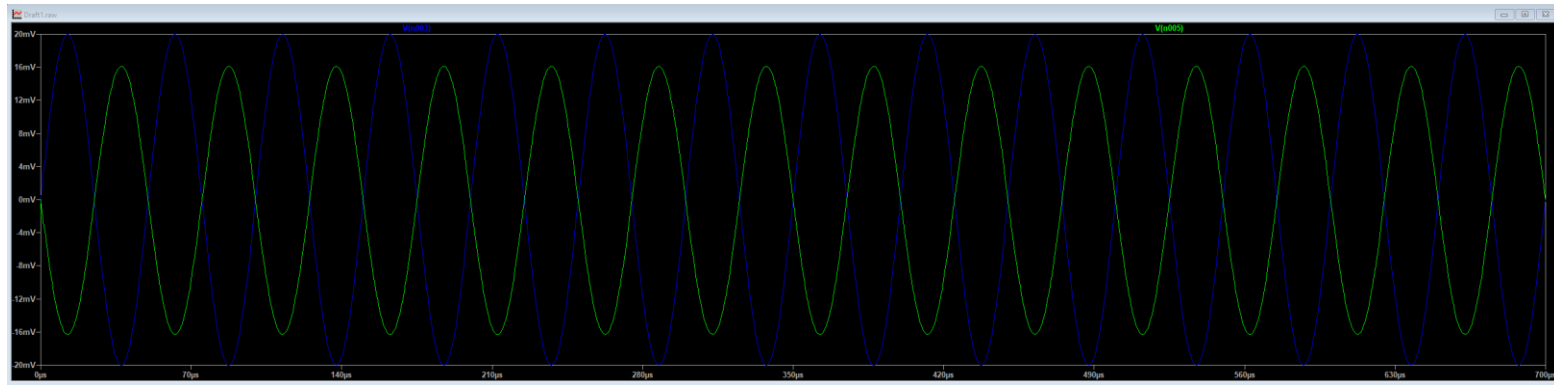If  $R_e = 5 \text{ k}\Omega$ , please measure  $v_i$  and  $v_o$ , and calculate the amplitude amplification coefficient  $A_v$ .





*Thanks*