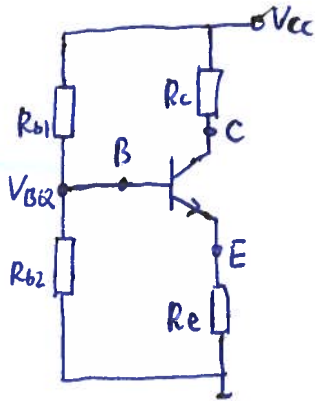


Answers to practice exercise of lecture - 4

a. DC circuit:



$$V_{BEQ} \approx \frac{R_{b2}}{R_{b1} + R_{b2}} \cdot V_{CC} = 4.21 \text{ V}$$


$$I_{CQ} \approx I_{EQ} = \frac{V_{BEQ} - V_{BEQ}}{R_e} = 1.755 \text{ mA}$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_c - I_{EQ} R_e \approx V_{CC} - I_{CQ} (R_c + R_e) = 6.69 \text{ V}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{1.755 \text{ mA}}{80} = 21.9 \mu\text{A}$$

$$\underline{Q (21.9 \mu\text{A}, 1.755 \text{ mA}, 6.69 \text{ V})}$$

b.

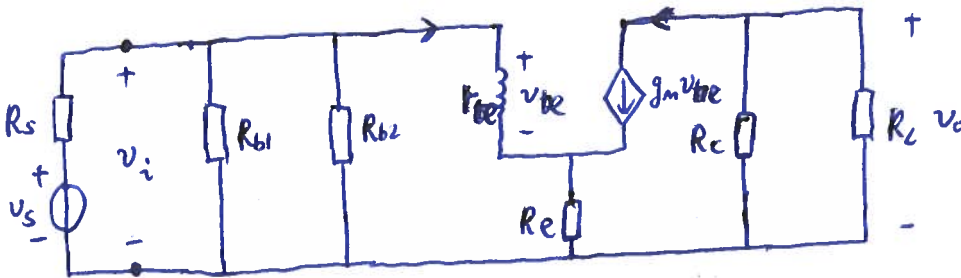

$$\underline{R_i = R_{b1} \parallel R_{b2} \parallel [r_{be} + (1 + \beta) R_e] \approx 13.5 \text{ k}\Omega}$$

$$r_{be} = \frac{\beta}{g_m}, \quad g_m = \frac{I_{CQ}}{V_T} = \frac{1.755 \text{ mA}}{26 \text{ mV}} = 0.0675 \text{ S}$$

$$r_{be} = 80 / 0.0675 \approx 1185 \Omega = 1.185 \text{ k}\Omega$$


$$\underline{R_o \approx R_c = 3.3 \text{ k}\Omega}$$

$$\underline{A_v = \frac{v_o}{v_i} = - \frac{\beta \cdot (R_c \parallel R_L)}{r_{be} + (1 + \beta) R_e} \approx -1.05}$$

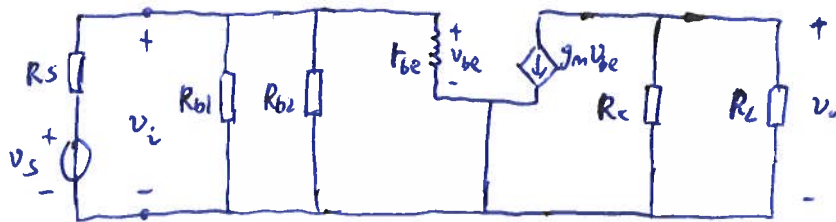c. if a capacitor is parallel with R_E , ~~recalculate a.~~

the Q point is the same as the capacitor is regarded as open in DC circuit.

recalculate (b). since capacitor is regarded as short for AC circuit.



$$R_i = R_{b1} // R_{b2} // r_{be} \approx 1.1 \text{ k}\Omega$$

$$R_o \approx R_C = 3.3 \text{ k}\Omega$$

$$\underline{A_v = \frac{v_o}{v_i} \approx - \frac{\beta \cdot (R_{b1} // R_{b2})}{r_{be}} \approx -995}$$