

Analog Electronics


Fengchun Zhang

fz@es.aau.dk

Agenda

- Recap feedback system
- Solutions of the assignments
- Gain optimization and harmonic distortion improvement for BJT
- Introduction to biasing
 - BJT case
 - MOSFET case

General feedback system

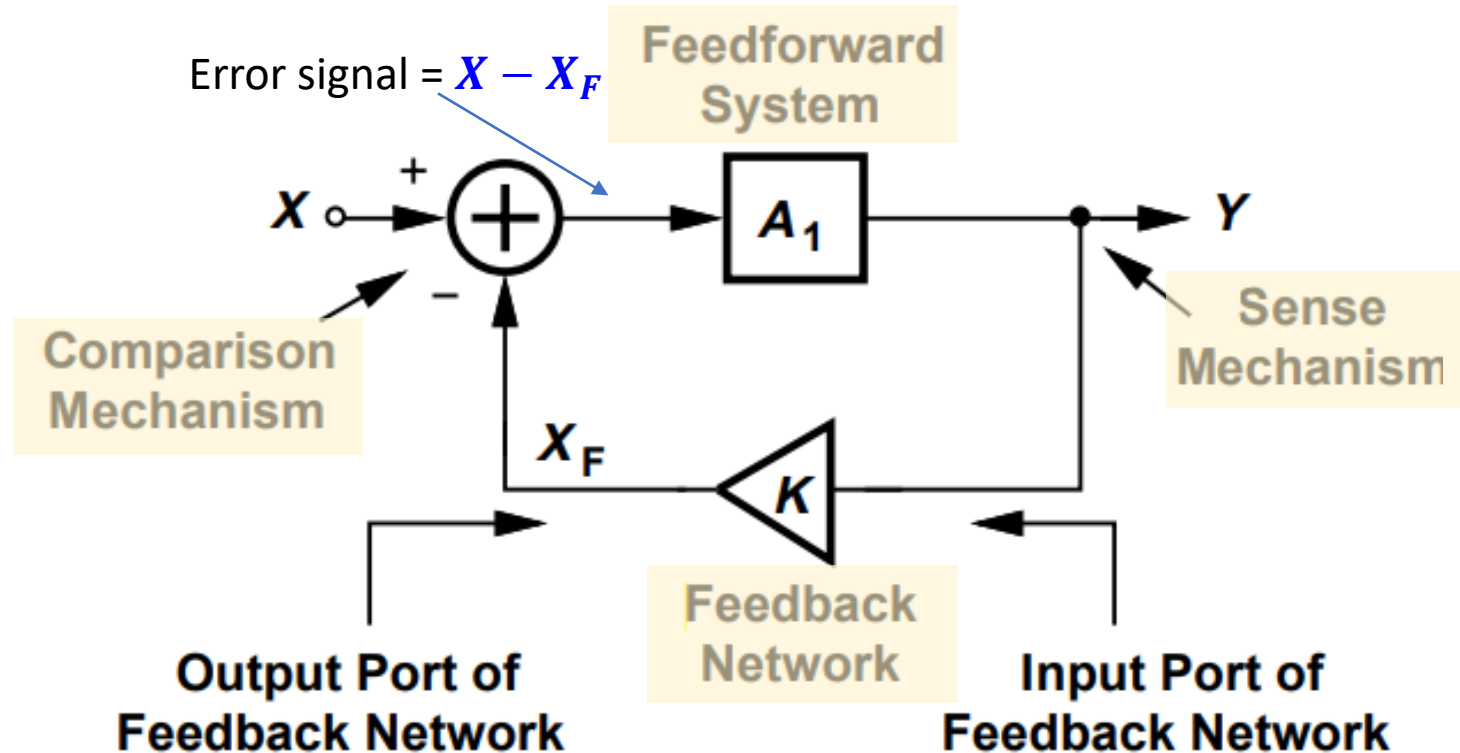


Negative feedback system:

- X and X_F change in the same direction;
- The error signal should be minimized;
- Open-loop system: break the feedback network, $K = 0$
- Closed-loop system: $K \neq 0$

Loop-gain

- Open-loop gain: A_1
- Closed-loop gain: $A_{cL} = \frac{Y}{X} = \frac{A_1}{1+KA_1}$
- Loop-gain: KA_1
 - Procedure to measure loop-gain
 - Set the input X to zero (X is voltage \rightarrow AC ground; if X is current \rightarrow open)
 - Break the loop at an arbitrary point
 - Apply a test signal V_{test} at one terminal and measure the signal V_F at the other terminal
 - Calculate the loop-gain $-\frac{V_F}{V_{test}} = KA_1$
 - $\frac{V_F}{V_{test}} < 0 \rightarrow$ negative feedback
 - $\frac{V_F}{V_{test}} > 0 \rightarrow$ positive feedback

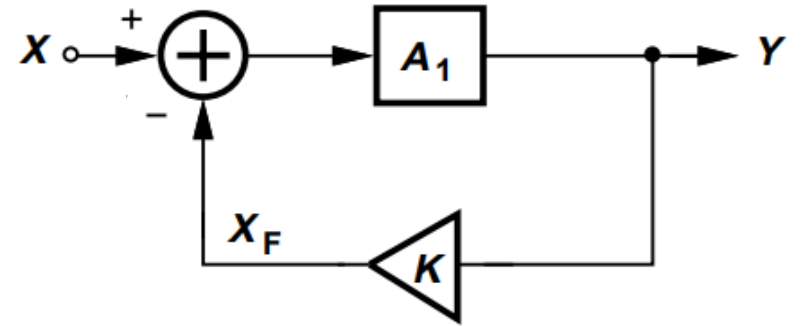


Properties of negative feedback

- Cons:
 - Smaller gain
- Pros:
 - Gain desensitization
 - Bandwidth extension
 - Linearity improvement
 - Modification of input and output impedance

Agenda

- Recap feedback system
- Solutions of the assignments
- **Gain optimization and harmonic distortion improvement for BJT**
- Introduction to biasing
 - BJT case
 - MOSFET case

Gain optimization for BJT

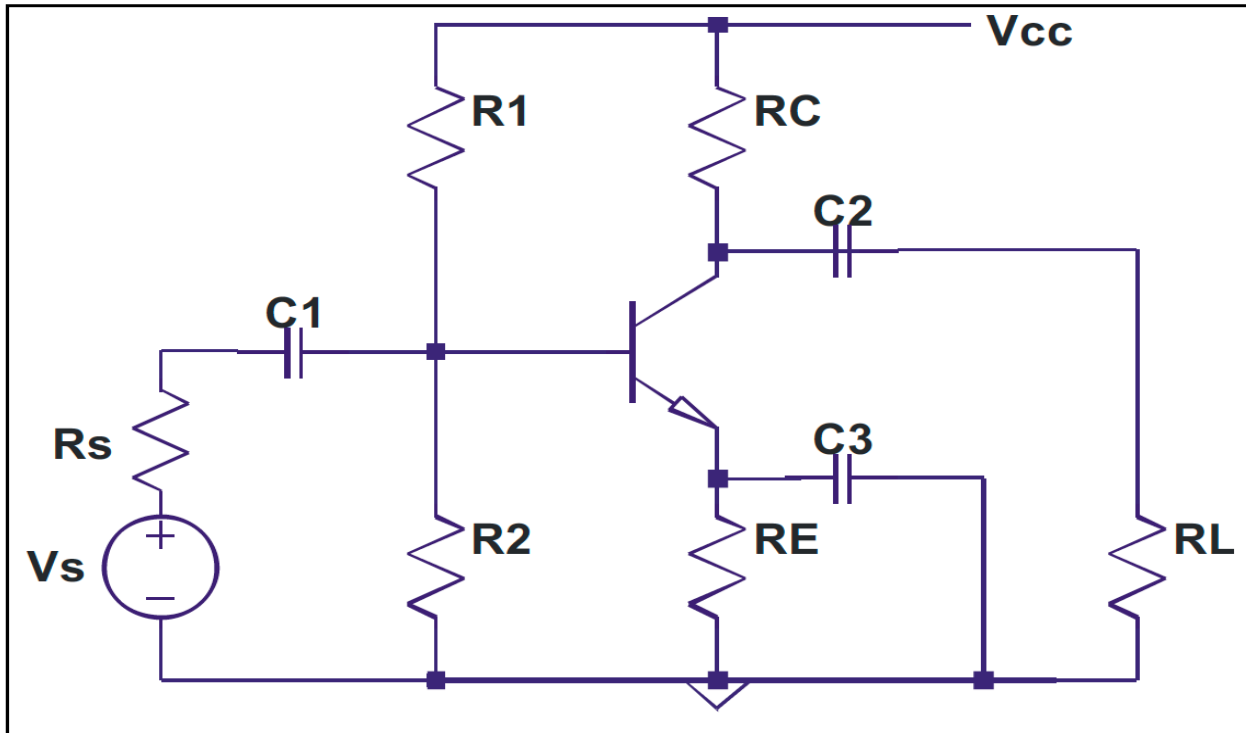

Definition & assumption:


$$v'_s = \frac{R_B}{R_B + R_S} v_s$$

$$R'_S = R_S \parallel R_B$$

$$r_o \gg R_C \parallel R_L$$

$$R_B = R_1 \parallel R_2$$

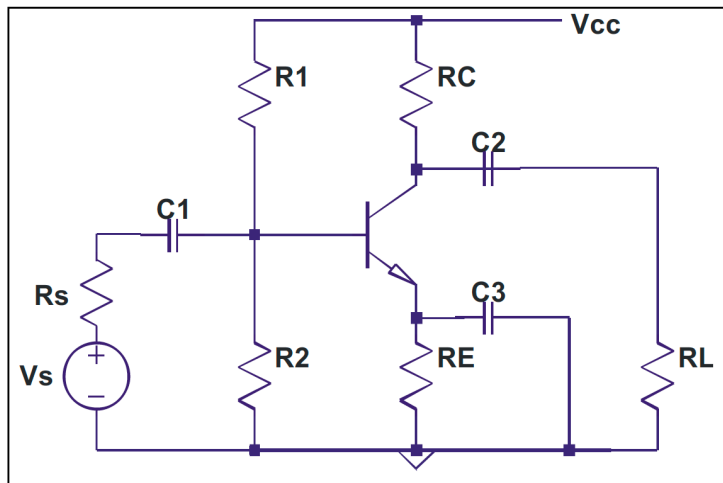Optimize R_C to maximize gain for the fixed V_{RC}




Definition & assumption:

$$v'_s = \frac{R_B}{R_B + R_S} v_s$$

$$R'_S = R_S \parallel R_B$$

$$r_o \gg R_C \parallel R_L$$

$$R_B = R_1 \parallel R_2$$

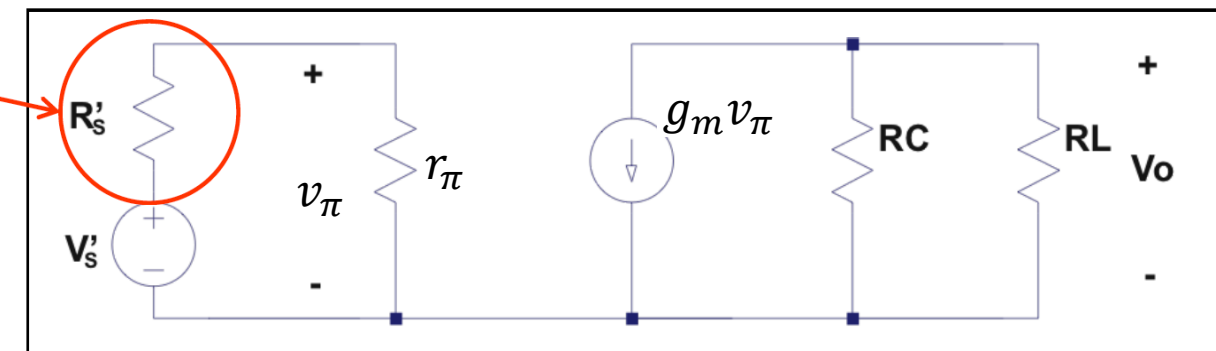


$$A_v = \frac{v_o}{v_s} = \frac{v_o}{v'_s} \cdot \frac{v'_s}{v_s} = A'_v \cdot \frac{R_B}{R_B + R_S}$$

$$A'_v = -\frac{g_m(R_C \parallel R_L)}{1 + \frac{R'_S}{r_\pi}} = -\frac{1}{\left(\frac{1}{g_m} + \frac{R'_S}{g_m r_\pi}\right)\left(\frac{1}{R_C} + \frac{1}{R_L}\right)}$$

$$g_m = \frac{I_C}{V_T} \text{ and } \beta = g_m r_\pi$$

$$\begin{aligned} \Rightarrow A'_v &= -\frac{1}{\left(\frac{V_T + R'_S}{I_C} + \frac{1}{\beta}\right)\left(\frac{1}{R_C} + \frac{1}{R_L}\right)} = -\frac{1}{\frac{V_T}{I_C R_C} + \frac{R'_S}{\beta R_C} + \frac{V_T}{I_C R_L} + \frac{R'_S}{\beta R_L}} \\ &= -\frac{1}{\frac{V_T}{V_{RC}} + \frac{R'_S}{\beta R_C} + \frac{R_C V_T}{V_{RC} R_L} + \frac{R'_S}{\beta R_L}} = -\frac{1}{N} \end{aligned}$$

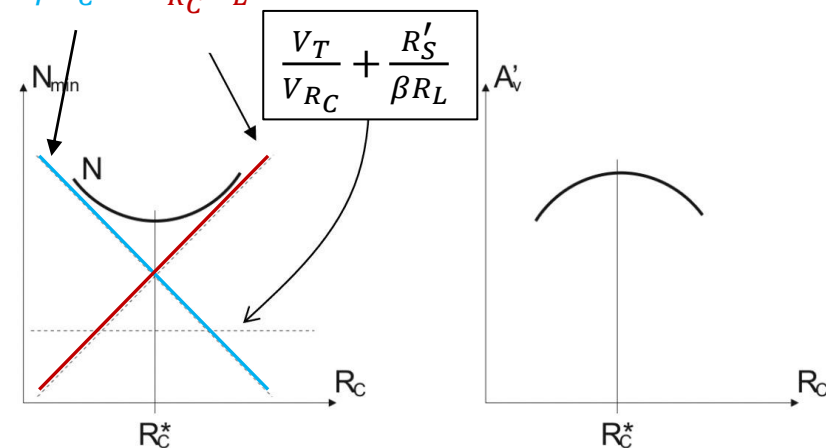Minimize $\frac{R'_S}{\beta R_C} + \frac{R_C V_T}{V_{RC} R_L} \rightarrow \text{minimize } N \rightarrow \text{maximize } A'_v$



Optimized R_C

$$\frac{\partial N}{\partial R_C} = 0 \Rightarrow R_C^* = \sqrt{\frac{R'_S \cdot R_L \cdot V_{RC}}{\beta \cdot V_T}} \Rightarrow$$

$$|A'_{v,\max}| = \frac{1}{\left(\sqrt{\frac{V_T}{V_{RC}}} + \sqrt{\frac{R'_S}{R_L \cdot \beta}}\right)^2}$$

Gain optimization

- Max gain based *exclude* $r_o = \frac{V_A}{I_C}$


$$|A'_{v,\max}| = \frac{1}{\left(\sqrt{\frac{V_T}{V_{R_C}}} + \sqrt{\frac{R'_S}{R_L \cdot \beta}}\right)^2} \Rightarrow R_C^* = \sqrt{\frac{R'_S \cdot R_L \cdot V_{R_C}}{\beta \cdot V_T}}$$

- Max gain based *include* $r_o = \frac{V_A}{I_C}$


$$|A'_v| = \frac{r_o \parallel R_C \parallel R_L}{\frac{1}{g_m} + \frac{R'_S}{\beta}} \Rightarrow R_C^* = \sqrt{\frac{R'_S \cdot R_L \cdot V_{R_C}}{\beta \cdot V_T} \left(1 + \frac{V_{R_C}}{V_A}\right)}$$

- Adding emitter resistor R_e reduce the gain

$$|A'_v| = \frac{r_o \parallel R_C \parallel R_L}{R'_e + \frac{1}{g_m} + \frac{R'_S}{\beta}} \Rightarrow R'_e = \frac{r_o \parallel R_C \parallel R_L}{A'_v} - \frac{1}{g_m} - \frac{R'_S}{\beta} = R_e \parallel R_E$$

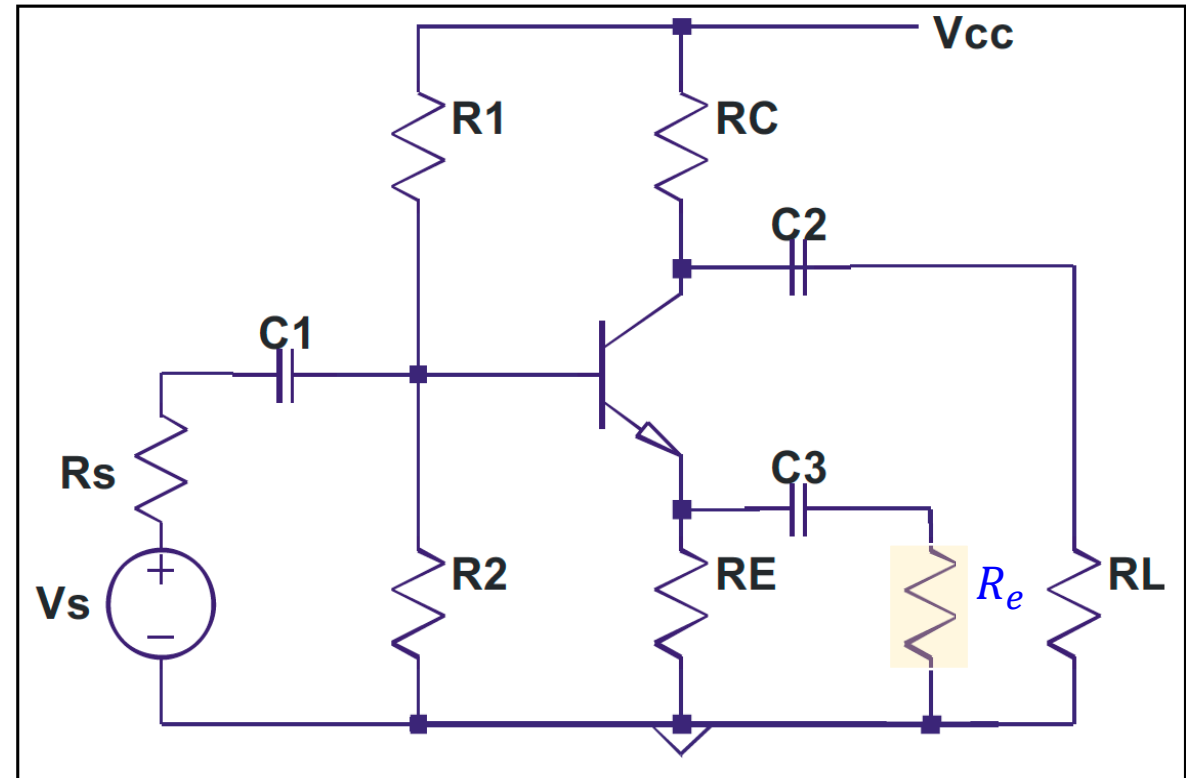

Improving the THD for a BJT

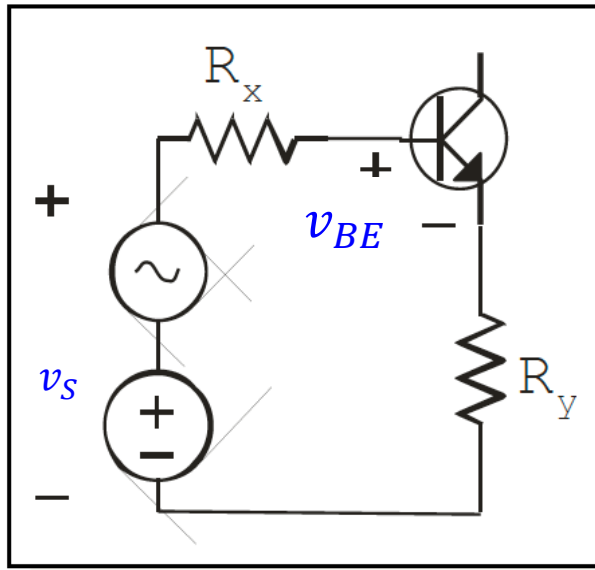

Large-signal model

$$v_s = V_s + \Delta V_s$$

$$i_c = I_C + \Delta I_C$$

- $i_c = f(v_s)$ must be found and then $f^{(1)}$ and $f^{(2)}$ are found at the operating point given by I_C
- Determine f^1 and f^2 by implicitly differentiation

$$v_s = \frac{i_c}{\beta} R_x + v_{BE} + i_c R_y$$
$$= \left(\frac{R_x}{\beta} + R_y \right) i_c + V_T \ln \left(\frac{i_c}{I_s} \right)$$

$$i_c = I_s \cdot e^{\left(\frac{v_{BE}}{V_T} \right)}$$

Improving the THD for a BJT

Determination of $f^{(1)}$:

$$v_s = \left(\frac{R_x}{\beta} + R_y \right) i_c + V_T \ln \left(\frac{i_c}{I_s} \right)$$

\Downarrow

$$1 = \left(\frac{R_x}{\beta} + R_y \right) \frac{\partial i_c}{\partial v_s} + 0 + V_T \frac{1}{i_c} \frac{1}{I_s} \frac{\partial i_c}{\partial v_s}$$

\Downarrow

$$1 = \left(\frac{R_x}{\beta} + R_y + \frac{V_T}{i_c} \right) \frac{\partial i_c}{\partial v_s} = \left(\frac{R_x}{\beta} + R_y + \frac{V_T}{i_c} \right) f^1$$

\Downarrow

$$f^{(1)}(i_c) = \frac{1}{\left(\frac{R_x}{\beta} + R_y + \frac{V_T}{i_c} \right)}$$

Diff. With v_s on both sides

$$(fg)' = (f)'g + f(g)'$$

$$(f(g))' = (f(g))'g'$$

Determination of $f^{(2)}$:

$$1 = \left(\frac{R_x}{\beta} + R_y + \frac{V_T}{i_c} \right) \frac{\partial i_c}{\partial v_s}$$

\Downarrow

$$0 = \left(\frac{R_x}{\beta} + R_y \right) \frac{\partial^2 i_c}{\partial v_s^2} + \frac{V_T}{i_c} \frac{\partial^2 i_c}{\partial v_s^2} + \frac{\partial i_c}{\partial v_s} \left(-\frac{V_T}{i_c^2} \right) \frac{\partial i_c}{\partial v_s}$$

\Downarrow

$$0 = \left(\frac{R_x}{\beta} + R_y + \frac{V_T}{i_c} \right) \frac{\partial^2 i_c}{\partial v_s^2} - \left(\frac{\partial i_c}{\partial v_s} \right)^2 \left(\frac{V_T}{i_c^2} \right)$$

\Downarrow

$$f^{(2)}(i_c) = \frac{(f^1)^2 \frac{V_T}{i_c^2}}{\frac{R_x}{\beta} + R_y + \frac{V_T}{i_c}}$$

Diff. With v_s on both sides one more time

$$(fg)' = (f)'g + f(g)'$$

$$(f(g))' = (f(g))'g'$$

Improving the THD for a BJT


We have now determined $f^{(1)}$ and of $f^{(2)}$ and are thus able to assess which effect R_x and R_y might have on, for example, HD2

$$HD_2 = \frac{1}{4} \left| \frac{f^{(2)}}{f^{(1)}} \right| A = \frac{1}{4} \frac{\left(f^{(1)} \right) \frac{V_T}{i_C^2}}{\frac{R_x}{\beta} + R_y + \frac{V_T}{i_C}} A = \frac{1}{4} \frac{\frac{V_T^2}{i_C^2}}{\left(\frac{R_x}{\beta} + R_y + \frac{V_T}{i_C} \right)^2} \frac{A}{V_T}$$

$$= \frac{1}{4} \frac{1}{\left(\frac{i_C}{V_T} \left(\frac{R_x}{\beta} + R_y \right) + 1 \right)^2} \frac{A}{V_T} = \frac{1}{4} \frac{A}{V_T F^2}$$

$$i_C = I_C + \Delta I_C \approx I_C$$
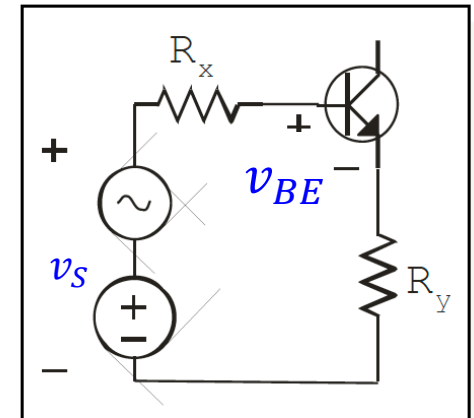
$$F = \frac{i_C}{V_T} \left(\frac{R_x}{\beta} + R_y \right) + 1 = g_m \left(\frac{R_x}{\beta} + R_y \right) + 1$$



$$f^{(1)}(i_C) = \frac{1}{\left(\frac{R_x}{\beta} + R_y + \frac{V_T}{i_C} \right)}$$


$$f^{(2)}(i_C) = \frac{\left(f^{(1)} \right)^2 \frac{V_T}{i_C^2}}{\frac{R_x}{\beta} + R_y + \frac{V_T}{i_C}}$$

Agenda

- Recap feedback system
- Solutions of the assignments
- Gain optimization and harmonic distortion improvement for BJT
- Introduction to biasing
 - BJT case
 - MOSFET case

Dispersion/spread -BJT

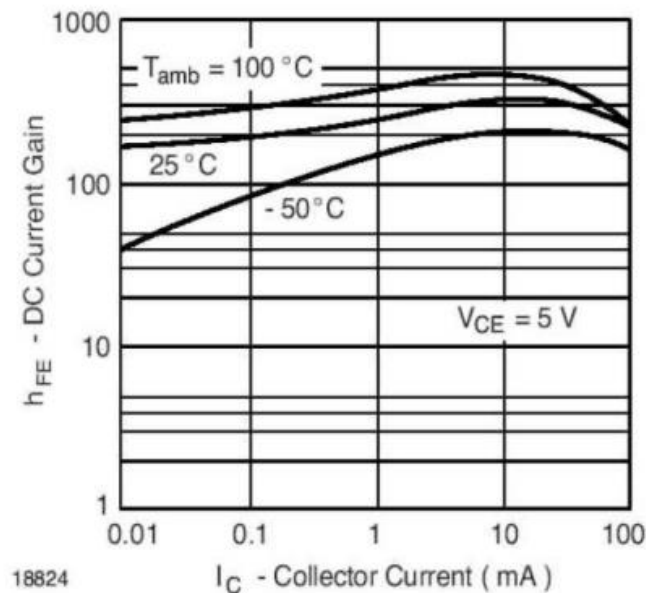- Key parameter:
 - V_{BE} : $\pm 10\%$ spread; vary with temperature $-2 \text{ mV}/^\circ\text{C}$
 - β : typical β_{DC} and β_{AC} are given, variation of $\pm 50\%$ is normal; vary with temperature $-0.5\% / ^\circ\text{C}$




$$[V_{BE}, I_C] = [0.7 \text{ V}, 10 \text{ mA}]$$

+10% $\rightarrow 80 \text{ mA}$


-10% $\rightarrow 2 \text{ mA}$

-80% \leftrightarrow +70%

I_C tolerance

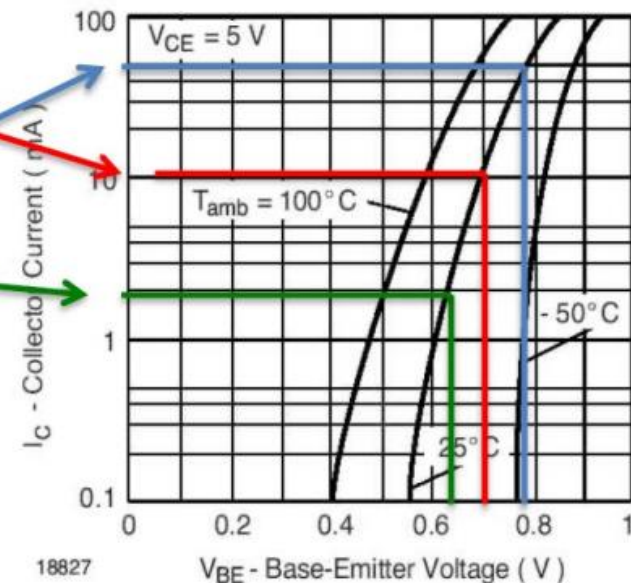


Bias circuit – BJT

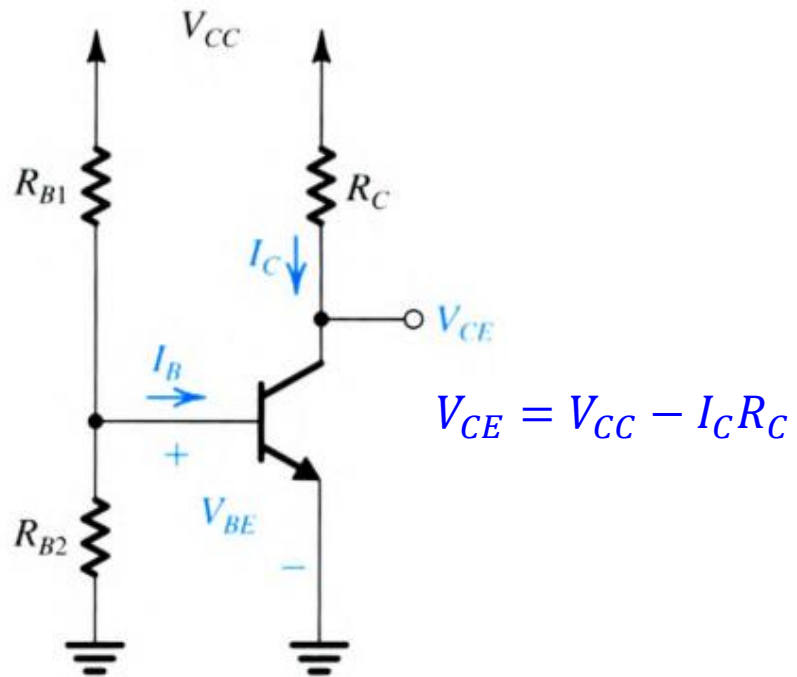

Fix V_{BE} is not a good design:

$$I_C = I_S e^{\frac{V_{BE}}{V_T}}$$

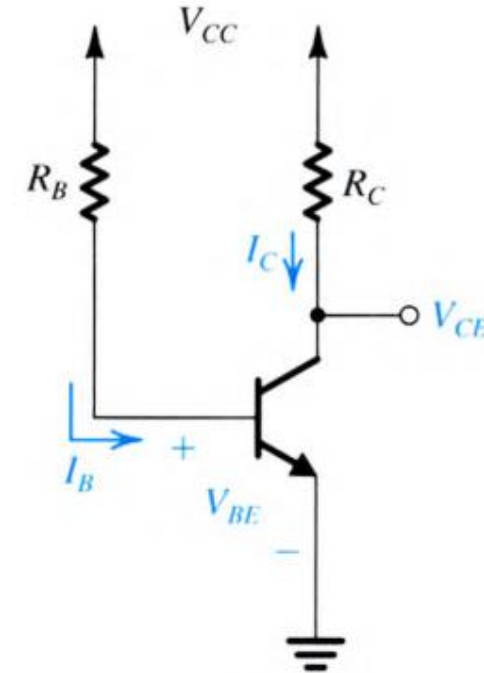- Small variation in $V_{BE} \rightarrow$ large variation in I_C
- I_S and V_T is temperature dependent




Fix I_B is not a good design:

$$I_C = \beta I_B$$


- Large variation in β among units of the same device type \rightarrow large variation in I_C

The classical discrete circuit bias design--BJT

Single-power supply

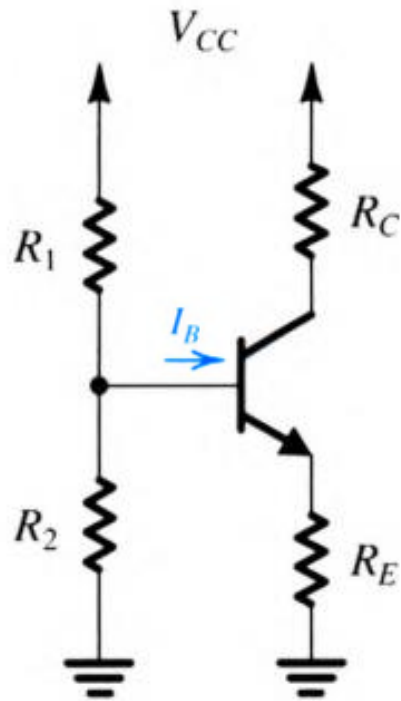

(a)

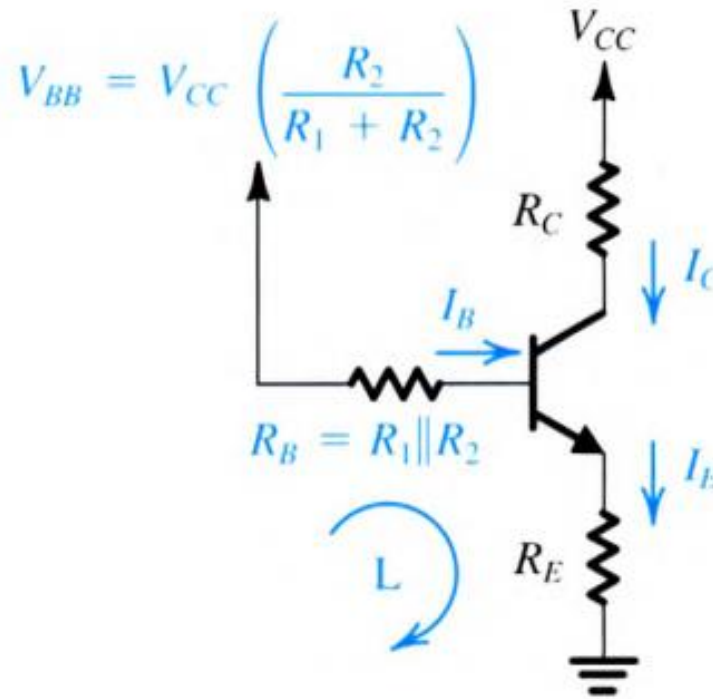

(b)

$$V_{BB} = V_{CC} \frac{R_2}{R_1 + R_2}$$

$$R_B = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + \frac{R_B}{\beta + 1}}$$

To make I_E insensitive to

- Temperature (V_{BE}) $\rightarrow V_{BB} \gg V_{BE}$
- $\beta \rightarrow R_E \gg \frac{R_B}{\beta + 1}$

Fix I_E is a good design: $I_E \approx \frac{V_{BB}}{R_E}$

The classical discrete circuit bias design -BJT

Stable operating point despite of uncertainty in V_{BE} & β

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + \frac{R_B}{\beta + 1}} \approx \frac{V_{BB}}{R_E}$$

Cond 1: $V_{BB} \gg V_{BE}$

$$V_{CC} = V_{RC} + V_{CB} + V_{BB}$$


- $V_{BB} \uparrow \rightarrow (V_{RC} + V_{CB}) \downarrow$
- V_{RC} needs be large to have a large $A_v \approx -g_m R_C = -\frac{I_C}{V_T} R_C = -\frac{V_{RC}}{V_T}$ (CE, R_E bypassed in AC)
- V_{CB} needs to be large \rightarrow large signal swing

\rightarrow trade-off in designing V_{RC} & V_{CB} & V_{BB}

Cond 2: $R_E \gg \frac{R_B}{\beta + 1}$


- small $R_B \rightarrow$ small R_1 & R_2 :
 - large bias current drained from V_{CC}
 - Smaller input impedance

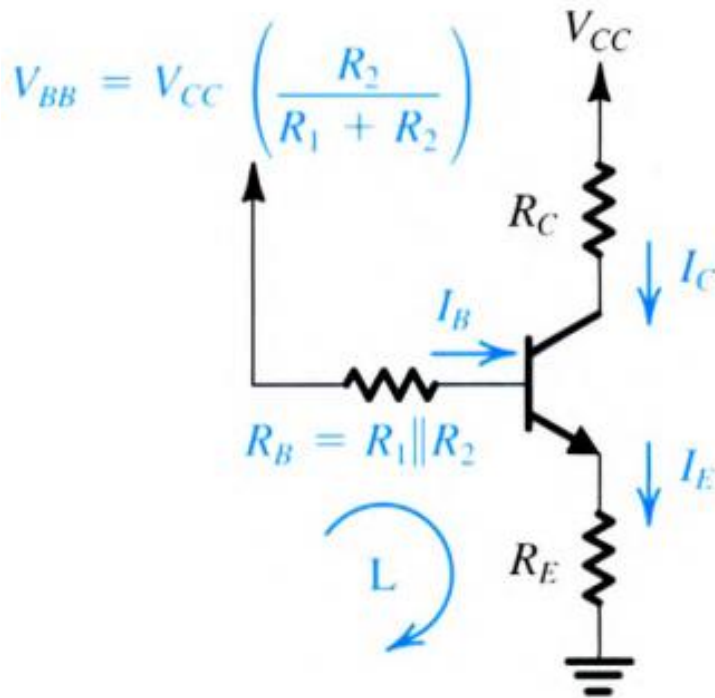\rightarrow trade-off in design R_1 & R_2




Rules of thumb for practical bias design: BJT amplifiers

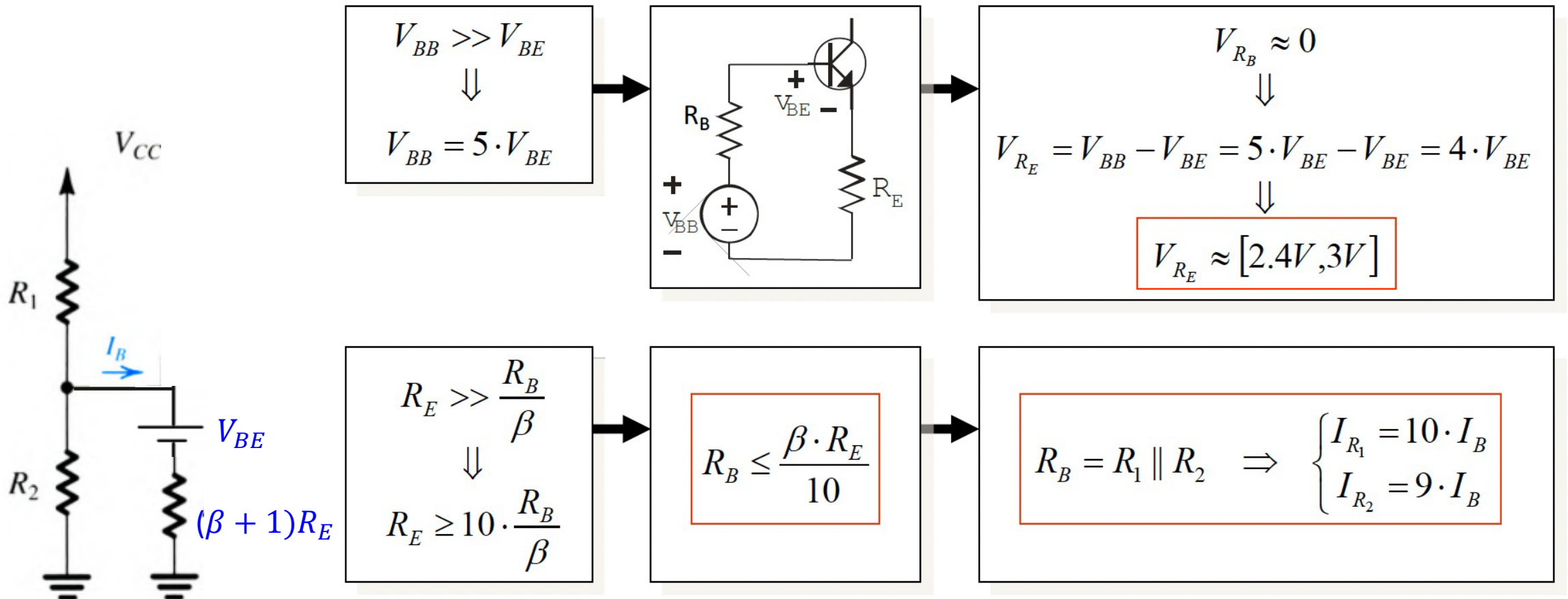
Using these rules, a design based on data for a **BC547b** transistor can ensure $\sim 3\%$ spread at operating point due to V_{BE} and β tolerances



Design procedure - BJT

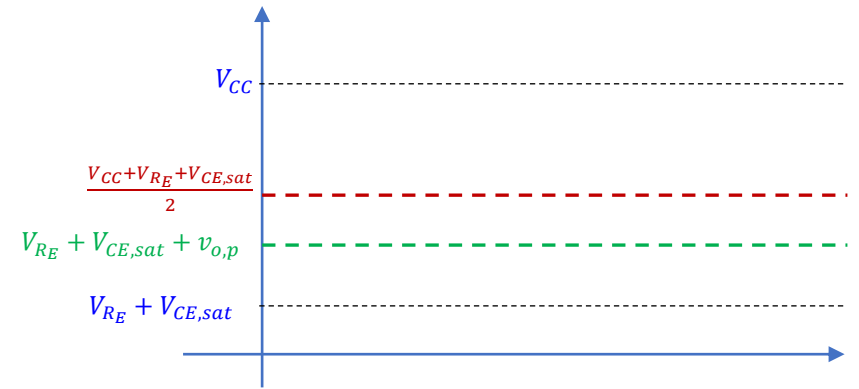

- Determine V_C or V_{RC} : $V_{RE} + V_{CE,sat} \leq V_C \leq V_{CC}$
 - Maximum output swing case:** $V_C = \frac{V_{CC} + V_{RE} + V_{CE,sat}}{2} \Rightarrow V_{RC} = V_{CC} - V_C = \frac{V_{CC} - (V_{RE} + V_{CE,sat})}{2}$
 - Known $v_{o,p}$ for highest A_v case:** $V_C = V_{CE,sat} + V_{RE} + v_{o,p} \Rightarrow V_{RC} = V_{CC} - V_C = V_{CC} - V_{CE,sat} - V_{RE} - v_{o,p}$
- Determine R_C to achieve maximum gain: $R_C = \sqrt{\frac{R'_S \cdot R_L \cdot V_{RC}}{\beta V_T}} \approx \sqrt{\frac{R_S \cdot R_L \cdot V_{RC}}{\beta V_T}}$, as $R_S \ll R_B$
- Determine $I_C = V_{RC} / R_C$
- Determine $R_E = \frac{V_{RE}}{I_C} = \frac{3V}{I_C}$
- Determine $R_B = \beta R_E / 10$ -- to approx $R_E \gg R_B / \beta$
- Calculate $V_{BB} = I_C R_E + V_{BE} + \frac{I_C}{\beta} R_B$
- Determine R_1 and R_2 : $R_B = \frac{R_1 R_2}{R_1 + R_2}$ & $V_{BB} = V_{CC} \frac{R_2}{R_1 + R_2}$
- Calculate the gain and compare with requirement
- Check harmonic distortion

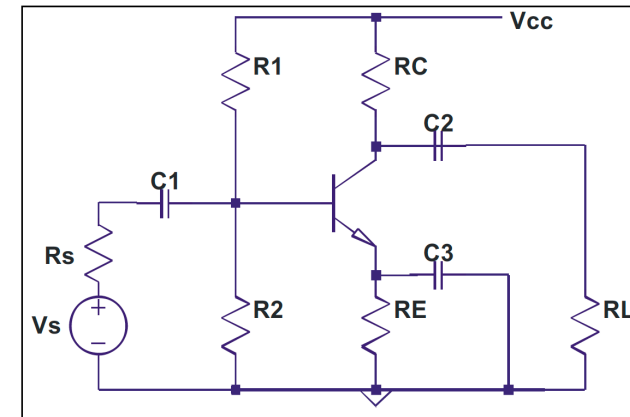

Definitioner/antagelser:

$$v'_s = \frac{R_B}{R_B + R_S} v_s$$


$$R'_S = R_S \parallel R_B$$

$$r_o \gg R_C \parallel R_L$$

$$A_v = -\frac{R_{in}}{R_{in} + R_S} g_m (R_C \parallel R_L) \text{ -- } R_{in} = R_1 \parallel R_2 \parallel r_\pi$$

$$\text{Or } A_v = A'_v \frac{R_B}{R_B + R_S} \text{ with } A'_v = \frac{R_C \parallel R_L}{\frac{1}{g_m} + \frac{R'_S}{\beta}}$$

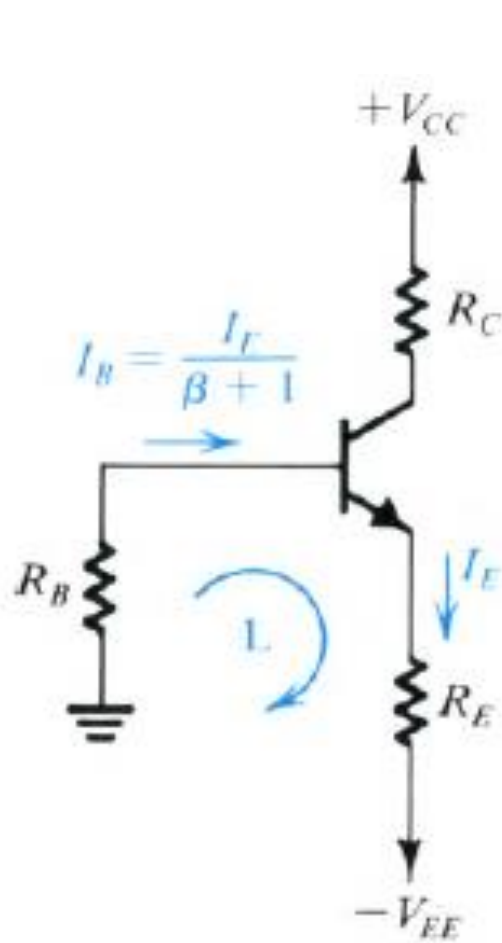Classical configuration with two power supplies



$$I_E = \frac{V_{EE} - V_{BE}}{R_E + \frac{R_B}{\beta + 1}}$$

Cond 1: $V_{EE} \gg V_{BE}$

Cond 2: $R_E \gg \frac{R_B}{\beta + 1}$


$$V_{EE} \geq 5V_{BE}$$

$$R_E \geq 10 \frac{R_B}{\beta}$$


A good configuration:
a stable operating point that is robust to changes in V_{BE} , β
and temperature.

$$A_v = -g_m R_C \text{ -- without AC } R_e$$

$$A_v = -\frac{R_C}{\frac{1}{g_m} + R'_e} \text{ -- with AC } R_e \text{ \& } R'_e = R_E || R_e$$

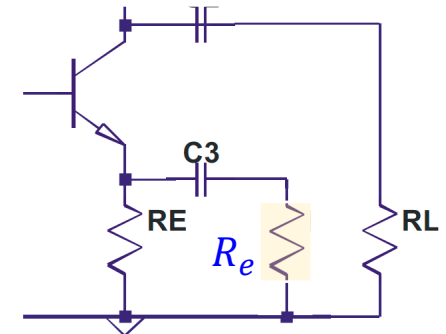

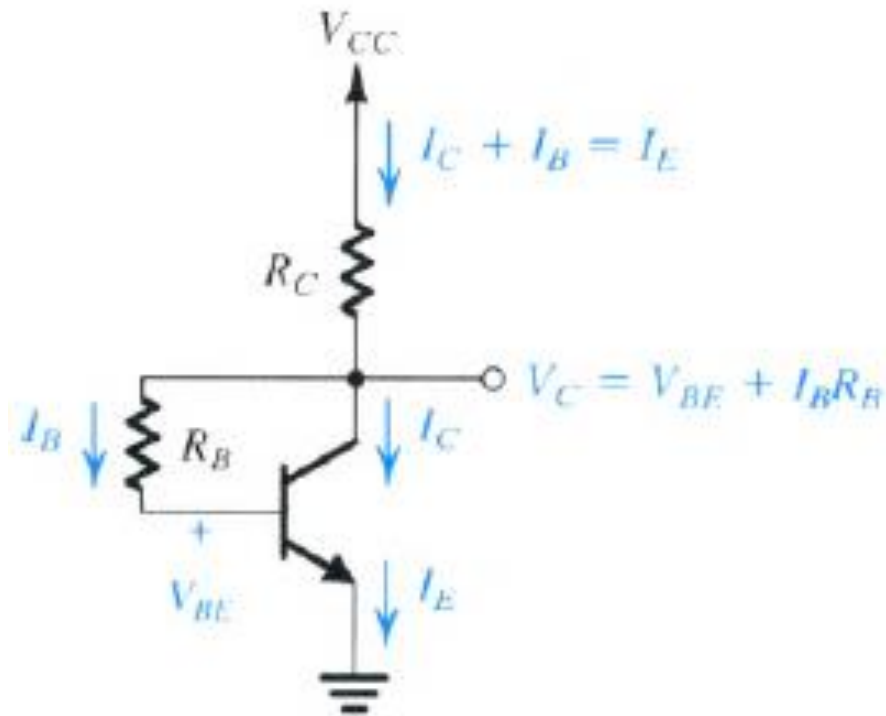Biasing with collector-to-base feedback R_B



$$I_E = \frac{V_{CC} - V_{BE}}{R_C + \frac{R_B}{\beta + 1}}$$

Cond 1: $V_{CC} \gg V_{BE}$

Cond 2: $R_C \gg \frac{R_B}{\beta + 1}$


$$R_C \geq 10 \frac{R_B}{\beta}$$

- Small $R_B \rightarrow$ small signal swing, as $V_{CB} = I_B R_B$
- Large $R_C \rightarrow$ large V_{CC}

$$A_v = -g_m(R_C || R_B) \text{ -- without AC } R_e$$

Gain drops due to the feedback

Quiz:

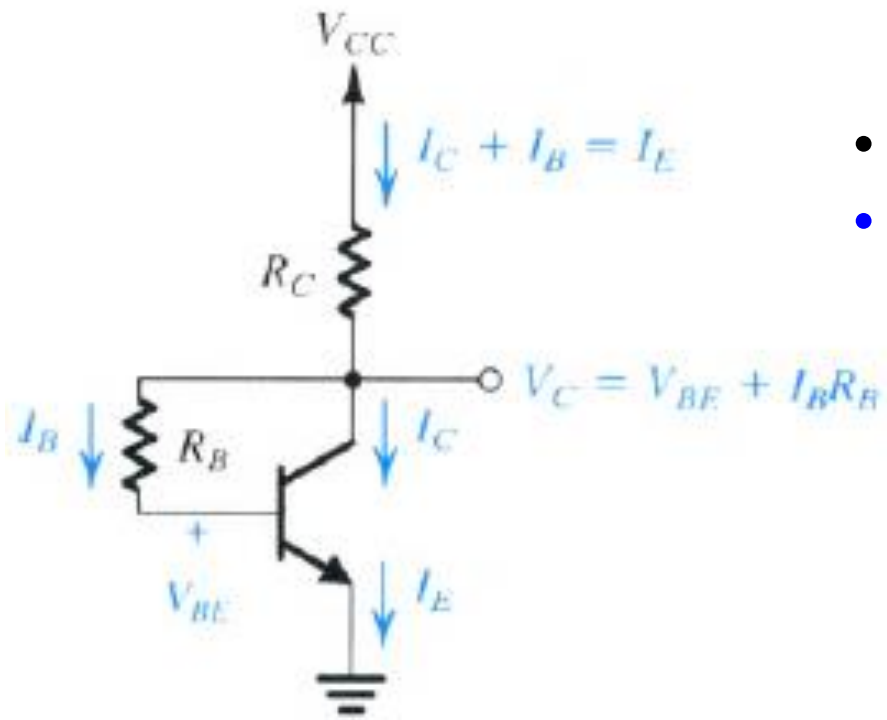

- The small-signal model of the circuit for CE stage?
- $A_v = ?$

Bais design - MOSFET

$$I_D = \frac{1}{2} k_n (V_{GS} - V_{TH})^2 = \frac{1}{2} \mu_n C_{ox} W / L (V_{GS} - V_{TH})^2$$


- μ_n : mobility of the electrons at the surface of the channel
- C_{ox} : oxide capacitance
- W & L : width & length of the channel

I_D variation:

- For different devices: V_{TH} , C_{ox} and W / L vary among devices even for devices with the same nominal values due to fabrication.
- For the same device due to temperature

Fix V_{GS} is not good.


Bias design - MOSFET

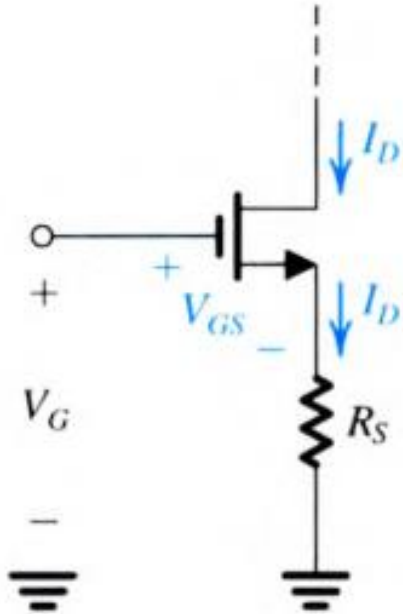

Fix V_G and connecting R_S
in source lead

$$V_G = V_{GS} + I_D R_S \approx I_D R_S$$


Cond : $V_G \gg V_{GS}$

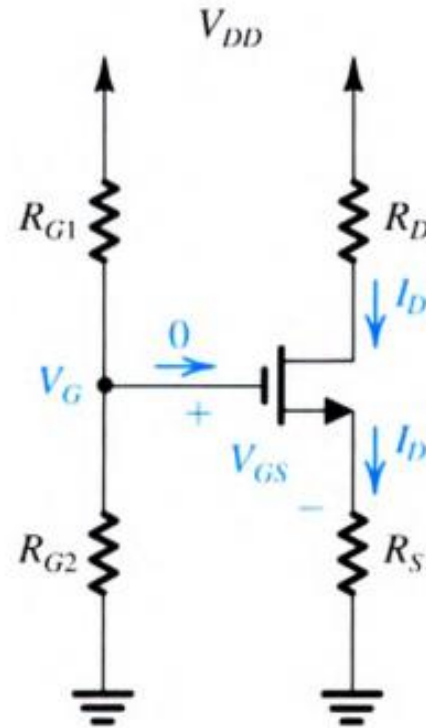

$$V_G = V_{DD} \frac{R_{G2}}{R_{G1} + R_{G2}}$$

$$V_G = V_{GS} + I_D R_S$$

Cond : $V_G \gg V_{GS}$

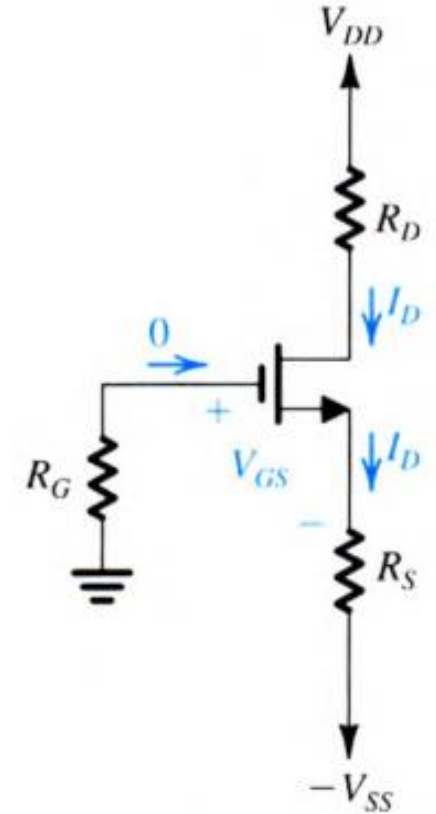

$$V_{SS} = V_{GS} + I_D R_S \approx I_D R_S$$

Cond : $V_{SS} \gg V_{GS}$

Bias design procedure - MOSFET

- Determine V_{GS} , for a required $THD = HD_2 = \frac{A}{4(V_{GS}-V_{TH})}$, A input amplitude
- Determine $I_D = \frac{1}{2}k_n(V_{GS} - V_{TH})^2$, k_n and V_{TH} from datasheet
- Determine $V_G = 5 V_{GS}$ to approx $V_G \gg V_{GS}$
- Determine $R_S = \frac{V_G - V_{GS}}{I_D}$
- Determine V_D or V_{R_D} : $V_G \leq V_D \leq V_{DD}$
 - *Maximum output swing case*: $V_D = \frac{V_{DD} + V_G}{2} \Rightarrow V_{R_D} = V_{DD} - V_D = \frac{V_{DD} - V_G}{2}$
 - *Known $v_{o,p}$ for highest A_v case*: $V_D = V_G + v_{o,p} \Rightarrow V_{R_D} = V_{DD} - V_D = V_{DD} - V_G - v_{o,p}$
- Determine $R_D = \frac{V_{R_D}}{I_D}$
- Determine R_{G1} and R_{G2} in $M\Omega$ range (provide high input impedance) using $V_G = V_{DD} \frac{R_{G2}}{R_{G1} + R_{G2}}$
- Calculate the gain and compare with requirement
- Check harmonic distortion

