

# Analog Electronics

Fengchun Zhang



[fz@es.aau.dk](mailto:fz@es.aau.dk)

# Agenda

- Recap Frequency response analysis and nonlinear systems
- Solutions of the assignments
- Feedback system

# High-frequency response
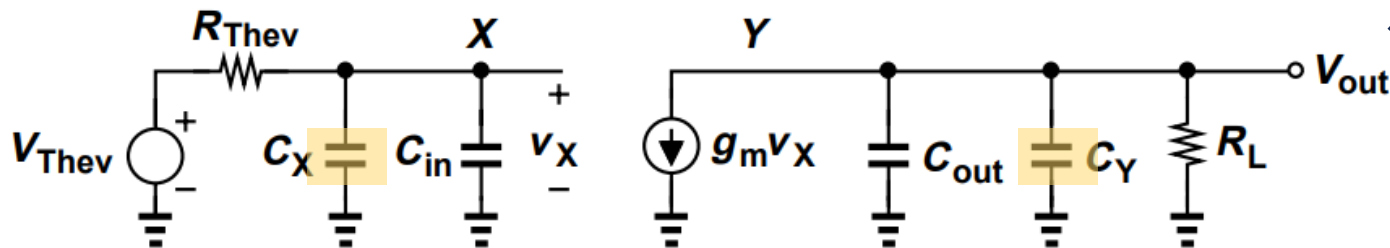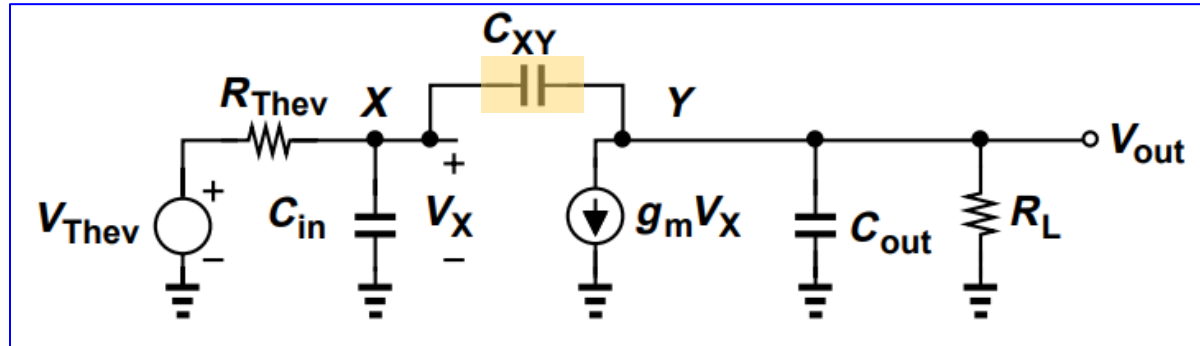
## Approach I: finding poles by inspection



CE Stage

$$V_{Thev} = V_{in} \frac{r_{\pi}}{r_{\pi} + R_S}$$

$$R_{Thev} = R_S \parallel r_{\pi}$$

$$C_X = C_{\mu} (1 + g_m R_L)$$

$$C_Y = C_{\mu} \left(1 + \frac{1}{g_m R_L}\right)$$

CS Stage

$$V_{Thev} = V_{in}$$

$$R_{Thev} = R_S$$


$$C_X = C_{GD} (1 + g_m R_L)$$

$$C_Y = C_{GD} \left(1 + \frac{1}{g_m R_L}\right)$$


Apply Miller's theorem to  $C_{XY}$

$$|\omega_{p,in}| = \frac{1}{R_{Thev} [C_{in} + C_{XY} (1 + g_m R_L)]}$$

$$|\omega_{p,out}| = \frac{1}{R_L [C_{out} + C_{XY} (1 + \frac{1}{g_m R_L})]}$$

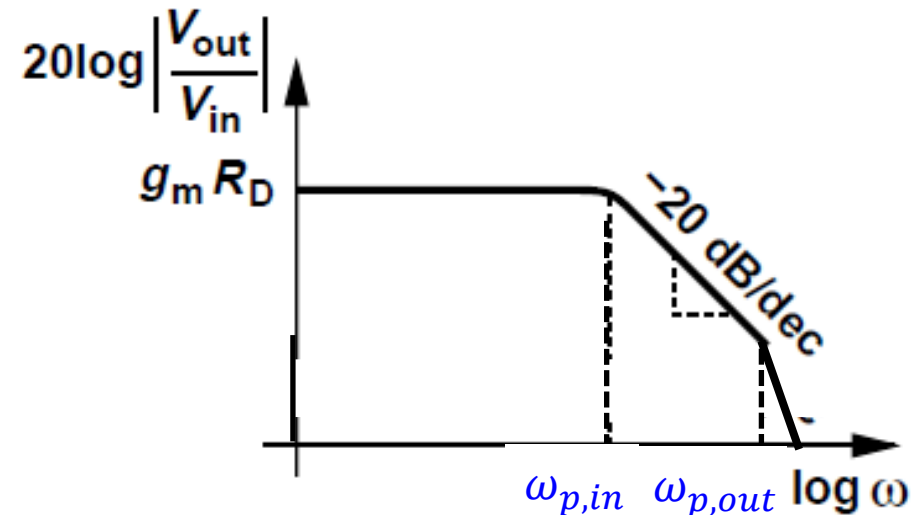

# Approach II: exact analysis

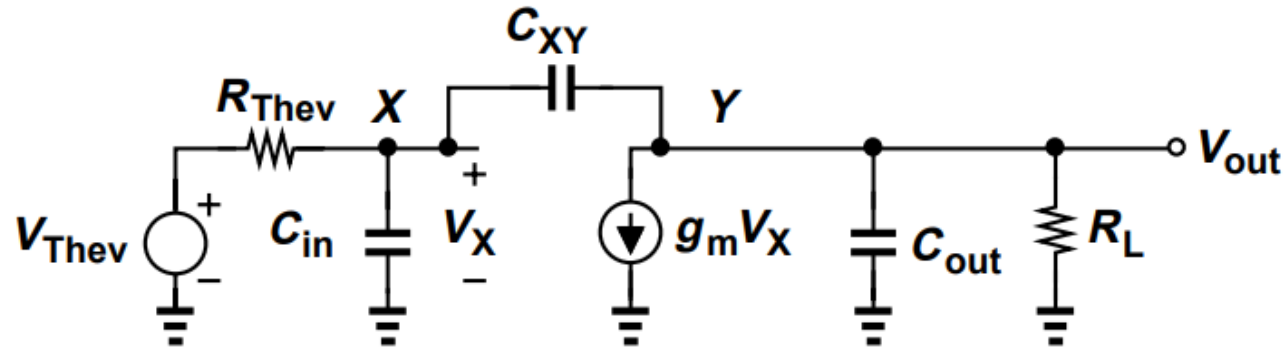

$$\frac{V_{out}}{V_{Thev}}(s)$$

$$= \frac{(C_{XY}s - g_m)R_L}{R_{Thev}R_L[C_{in}C_{XY} + C_{out}C_{XY} + C_{in}C_{out}]s^2 + [R_{Thev}C_{XY}(1 + g_mR_L) + R_{Thev}C_{in} + R_L(C_{XY} + C_{out})]s + 1}$$

- If  $s = 0$ ,  $\frac{V_{out}}{V_{Thev}}(s) = -g_mR_L$
- If  $s = \infty$ ,  $\frac{V_{out}}{V_{Thev}}(s) = 0$ ,  $C_{in}$  and  $C_{out}$  as short circuits  $\rightarrow V_{out} = V_{Thev} = 0$
- One zero:  $\omega_z = \frac{g_m}{C_{XY}}$ , e.g.,  $g_m \sim 0.01$ ,  $C_{XY} \sim 10^{-12} \rightarrow \omega_z \sim 10$  GHz, very high frequency, so typically not important
- Two poles: dominant pole approximation, i.e.,  $\omega_{p1} \ll \omega_{p2}$

$$\rightarrow \omega_{p1} = \frac{1}{[R_{Thev}C_{XY}(1+g_mR_L)+R_{Thev}C_{in}+R_L(C_{XY}+C_{out})]}$$

# Low-frequency response-BJT

$$\frac{V_o}{V_{sig}} = A_M \frac{s}{s+\omega_{p1}} \frac{s+\omega_z}{s+\omega_{pE}} \frac{s}{s+\omega_{p2}}$$

$$\omega_{p1} = \frac{1}{\tau_{c1}} = \frac{1}{C_{C1}(R_B || r_{\pi} + R_{sig})}$$

$$\omega_{pE} = \frac{1}{\tau_{cE}} = \frac{1}{C_E [R_E || (\frac{1}{g_m} + \frac{R_B || R_{sig}}{\beta + 1})]} \quad \text{Dominant pole}$$




$$\omega_{p2} = \frac{1}{\tau_{c2}} = \frac{1}{C_{C2}(R_C + R_L)}$$

$$\omega_z = \frac{1}{C_E R_E}$$


$$R_B = R_{B1} || R_{B2} \quad r_{\pi} = \frac{\beta}{g_m} = \beta r_e$$

Short-circuit time constant method:

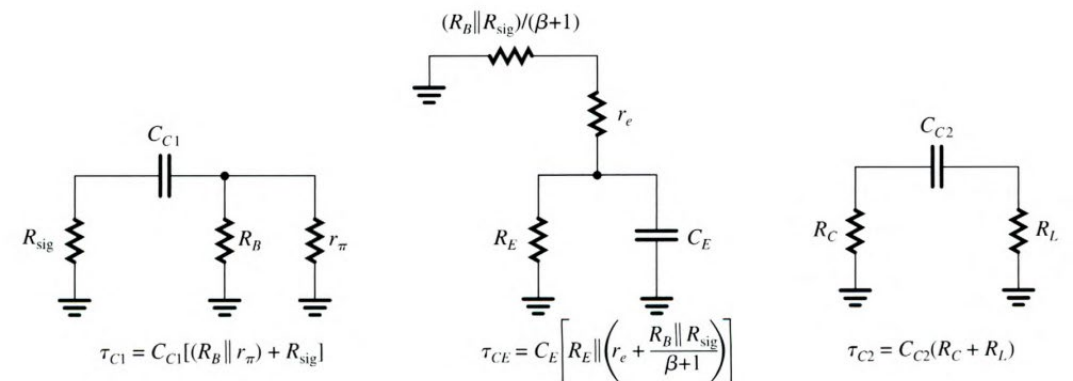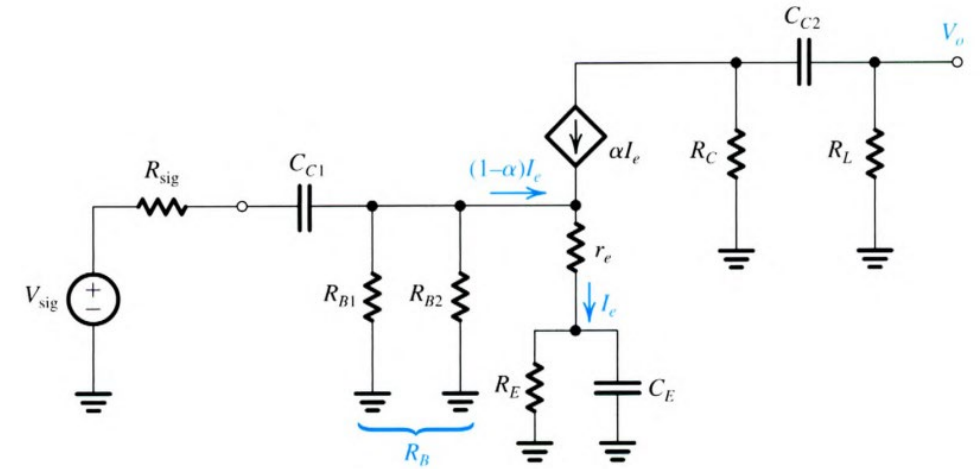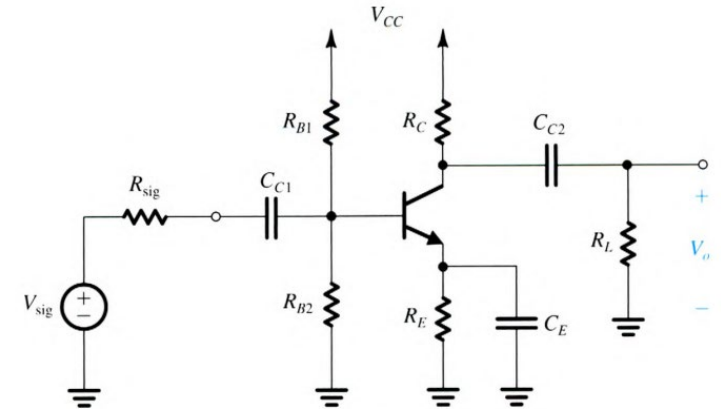- Short other capacitors
- turn off sources:
  - Voltage source  $\rightarrow$  short circuit
  - Current source  $\rightarrow$  open circuit




# The role of capacitors

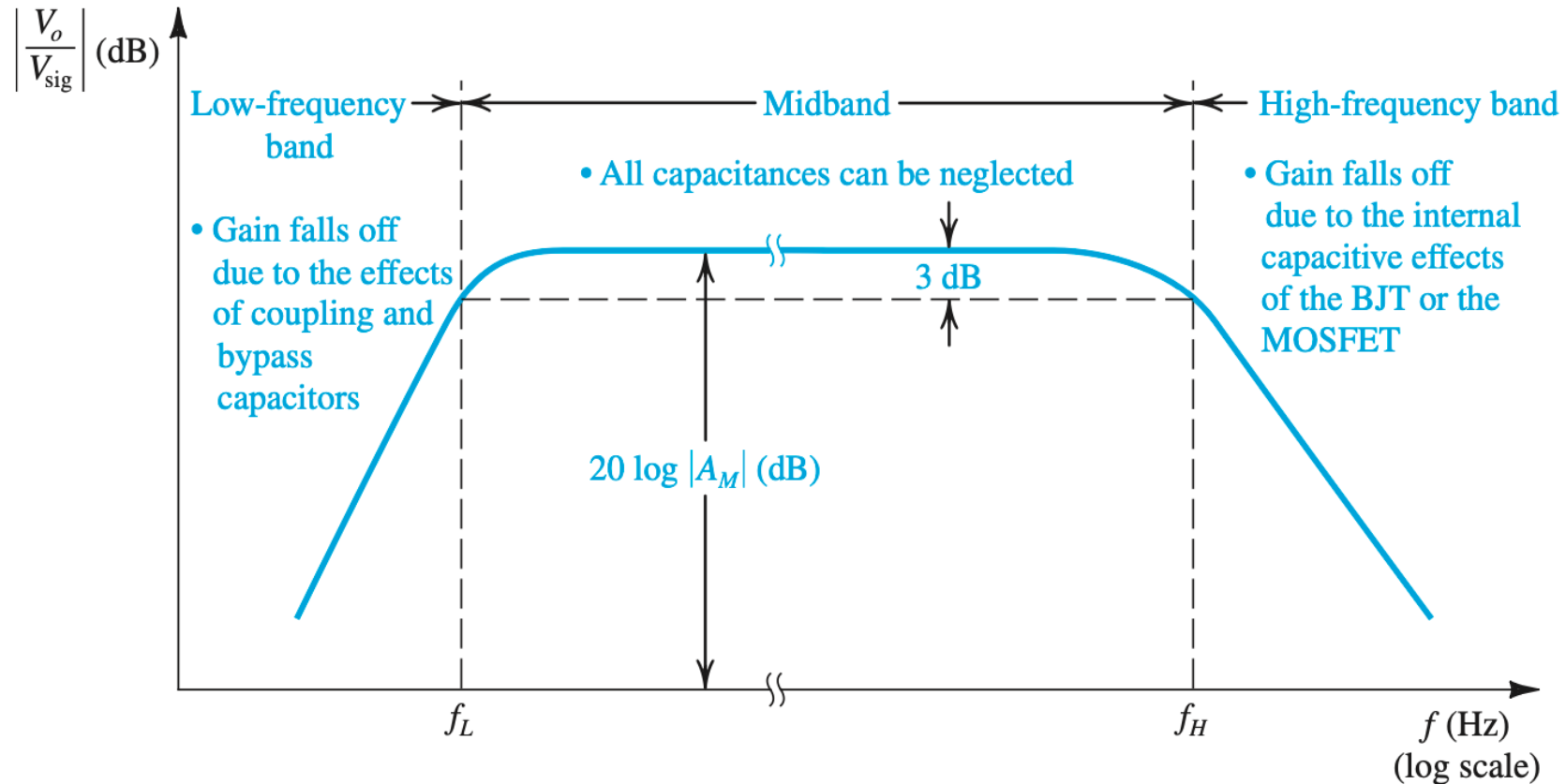

**Figure 10.1** Sketch of the magnitude of the gain of a discrete-circuit BJT or MOS amplifier versus frequency. The graph delineates the three frequency bands relevant to frequency-response determination.

# Nonlinear system example--BJT

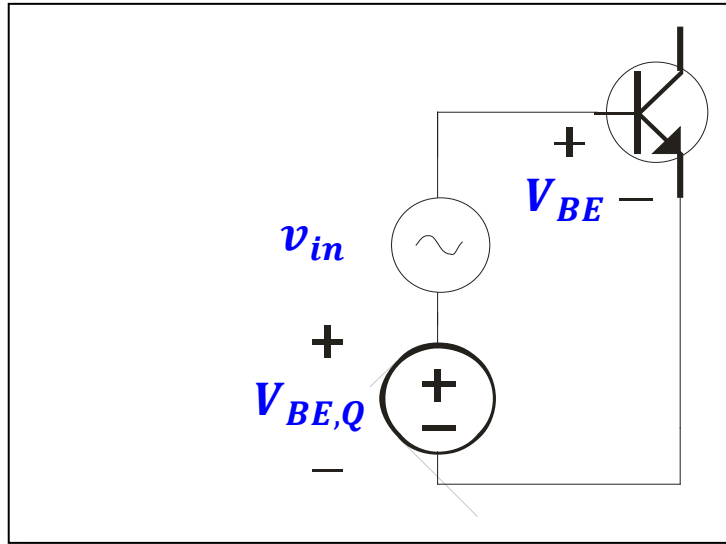

**Taylor series expansion:**

$$e^{x/a} = 1 + \frac{1}{a}x + \frac{1}{2! \cdot a^2}x^2 + \dots + \frac{1}{n! \cdot a^n}x^n + \dots$$

$$\begin{aligned} I_C &= I_S e^{V_{BE}/V_T} = I_S e^{(V_{BE,Q} + v_{in})/V_T} = I_S e^{V_{BE,Q}/V_T} e^{v_{in}/V_T} = I_{CQ} e^{v_{in}/V_T} \\ &= I_{CQ} \left( 1 + \frac{1}{V_T} v_{in} + \frac{1}{2! \cdot V_T^2} v_{in}^2 + \frac{1}{3! \cdot V_T^3} v_{in}^3 + \dots \right) \\ &= I_{CQ} + \frac{I_{CQ}}{V_T} v_{in} + \frac{I_{CQ}}{2! \cdot V_T^2} v_{in}^2 + \frac{I_{CQ}}{3! \cdot V_T^3} v_{in}^3 + \dots \\ &= \alpha_0 + \alpha_1 v_{in} + \alpha_2 v_{in}^2 + \alpha_3 v_{in}^3 + \dots \end{aligned}$$

DC:

$$\beta_0 = \alpha_0 + \alpha_2 \frac{A^2}{2}$$

2nd Harmonic:

$$\beta_2 = \alpha_2 \frac{A^2}{2}$$

**Total harmonic distortion (THD):**

$$\begin{aligned} THD &= \sqrt{HD_2^2 + HD_3^2 + HD_4^2 + \dots} \\ &= \sqrt{\left(\frac{\beta_2}{\beta_1}\right)^2 + \left(\frac{\beta_3}{\beta_1}\right)^2 + \left(\frac{\beta_4}{\beta_1}\right)^2 + \dots} \end{aligned}$$


Fundamental:

$$\beta_1 = \alpha_1 A + \alpha_3 \frac{3A^3}{4} \approx \alpha_1 A$$

3rd Harmonic:

$$\beta_3 = \alpha_3 \frac{A^3}{4}$$

# Nonlinear system example--MOSFET

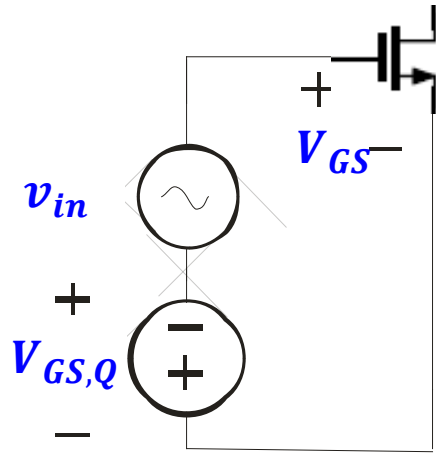

$$\begin{aligned}
 I_D &= \frac{1}{2} k_n (V_{GS} - V_{TH})^2 = \frac{1}{2} k_n (V_{GS,Q} - V_{TH} + v_{in})^2 \\
 &= \frac{1}{2} k_n (V_{GS,Q} - V_{TH})^2 \left( 1 + \frac{v_{in}}{V_{GS,Q} - V_{TH}} \right)^2 \\
 &= I_{DQ} \left( 1 + \frac{2}{V_{GS,Q} - V_{TH}} v_{in} + \frac{1}{(V_{GS,Q} - V_{TH})^2} v_{in}^2 \right) \\
 &= I_{DQ} + \frac{2I_{DQ}}{V_{GS,Q} - V_{TH}} v_{in} + \frac{I_{DQ}}{(V_{GS,Q} - V_{TH})^2} v_{in}^2 \\
 &= \alpha_0 + \alpha_1 v_{in} + \alpha_2 v_{in}^2
 \end{aligned}$$

DC:

$$\beta_0 = \alpha_0 + \alpha_2 \frac{A^2}{2}$$

2nd Harmonic:

$$\beta_2 = \alpha_2 \frac{A^2}{2}$$

Fundamental:

$$\beta_1 = \alpha_1 A$$

3rd Harmonic:

$$\beta_3 = 0$$

**Total harmonic distortion (THD):**


$$\begin{aligned}
 THD &= \sqrt{HD_2^2 + HD_3^2 + HD_4^2 + \dots} \\
 &= \frac{\beta_2}{\beta_1} = HD_2
 \end{aligned}$$



# Some practical problems of amplifiers

- Gain variation: e.g.  $A_v = -g_m R_1$ 
  - Temperature:  $g_m = I_{C,Q}/V_T$
  - Supply voltage:  $g_m = I_{C,Q}/V_T$
  - Manufacture:  $R_1$  varies from sample to sample
- Nonlinear distortion
- Bandwidth
- Input and output impedance
- Some applications, e.g. analog-to-digital converters, require very precise voltage gain e.g.  $A_v = 2.000$

# General feedback system

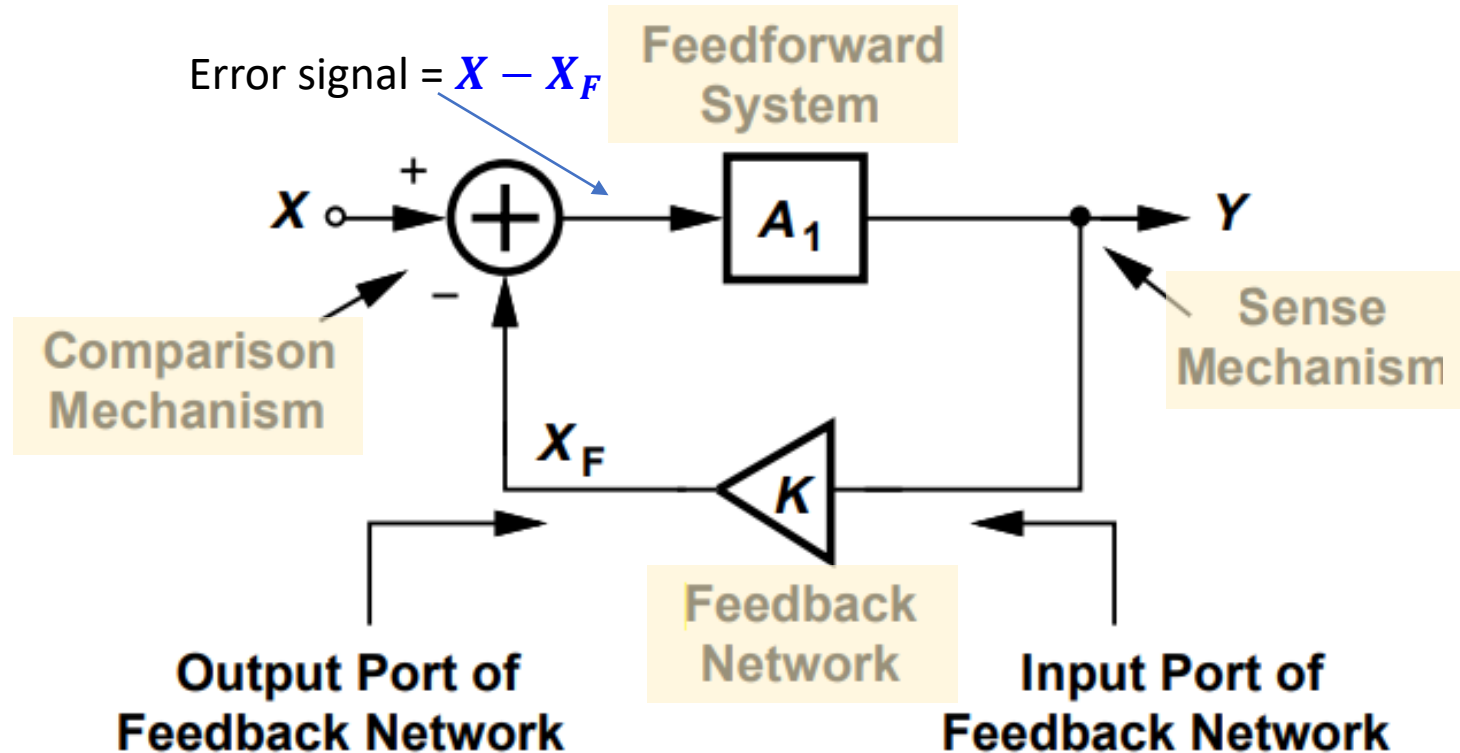


Negative feedback system:

- $X$  and  $X_F$  change in the same direction;
- The error signal should be minimized;
- Open-loop system: break the feedback network,  $K = 0$
- Closed-loop system:  $K \neq 0$

# Transfer function of closed-loop system

Error signal =  $X - X_F$

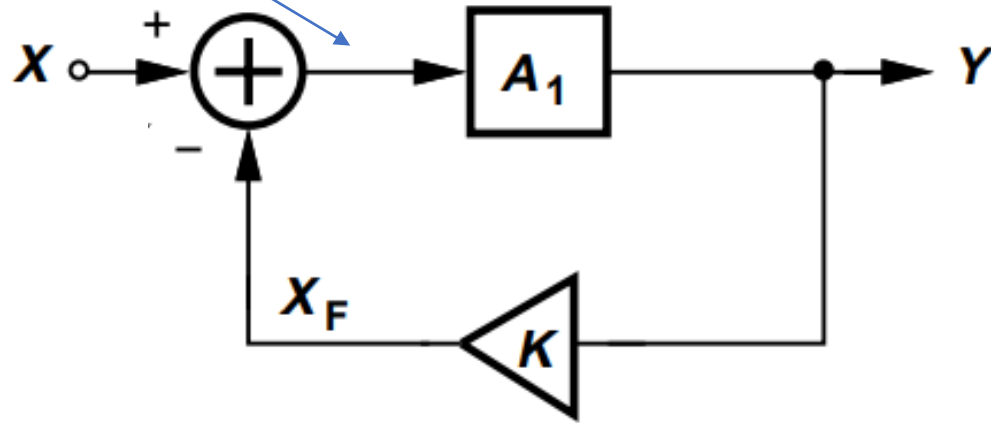

$$A_{cL} = \frac{Y}{X} = \frac{A_1}{1 + KA_1} \text{ --- closed-loop gain}$$


$A_1$  is the open-loop gain

$K$  is the feedback factor


$$KA_1 > 0 \Rightarrow |A_{cL}| < |A_1|$$

Quiz: determine the error signal in terms of  $X$

Error signal =  $X - X_F$

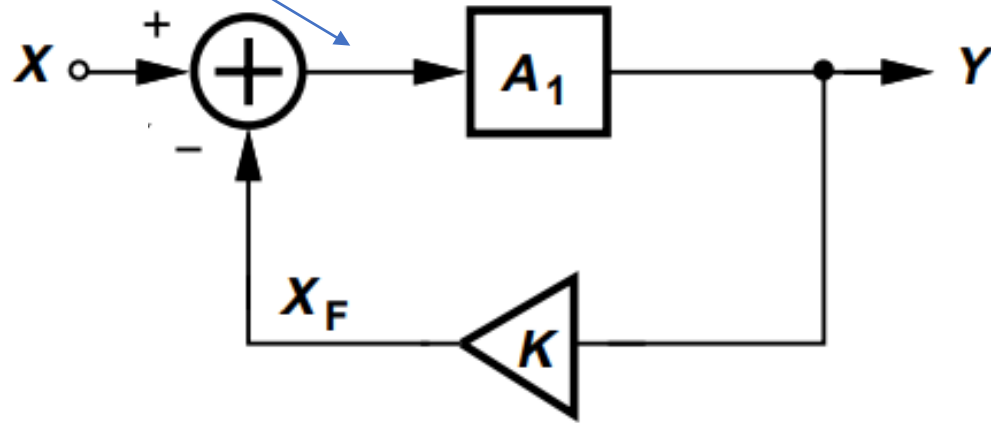

# Example

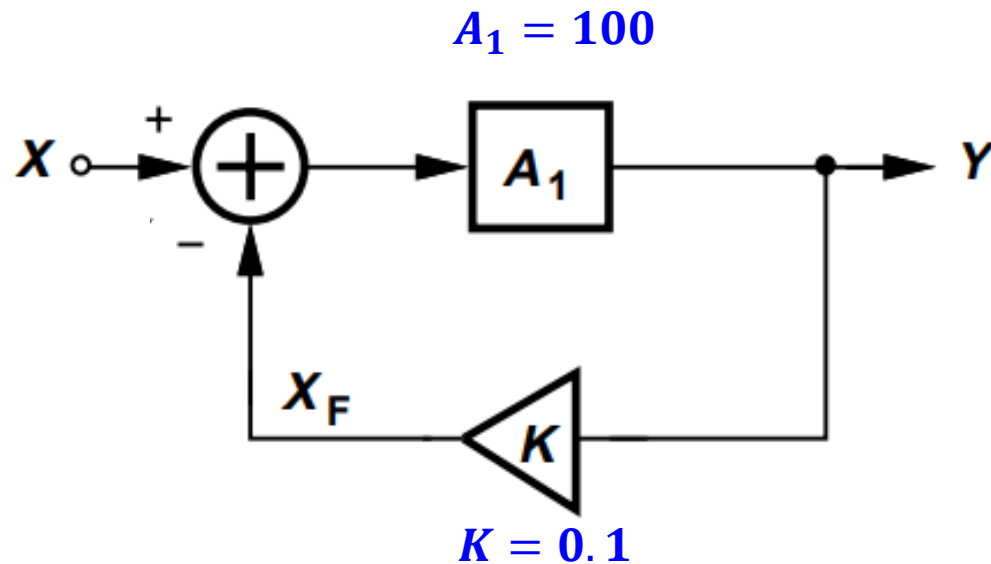

Nominal gain of an amp:  $A_1 = 100$   
Actual gain in application:  $A'_1 = 50$


How much does  $A_1$  change?  
How much does the closed-loop gain  $A_{cL}$  change?

$$A_{cL} = A_1 / (1 + K A_1) = 100 / 11 = 9.09$$

$$A'_{cL} = A'_1 / (1 + K A'_1) = 50 / 6 = 8.33$$

$A_{cL}$  change: 8.3%

# Feedback loop system

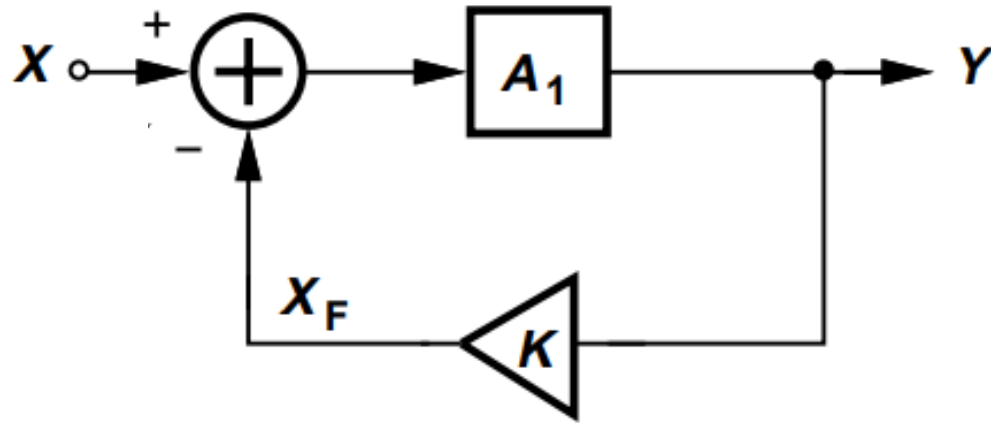


Closed-loop gain

$$A_{cL} = \frac{Y}{X} = \frac{A_1}{1 + KA_1} \approx \frac{1}{K} \text{ if } KA_1 \gg 1$$

→ Closed-loop gain  $A_{cL}$  is relatively independent of the open-loop gain  $A_1$

We still need  $A_{cL} > 1 \rightarrow 0 < K \leq 1$

# Feedback system example

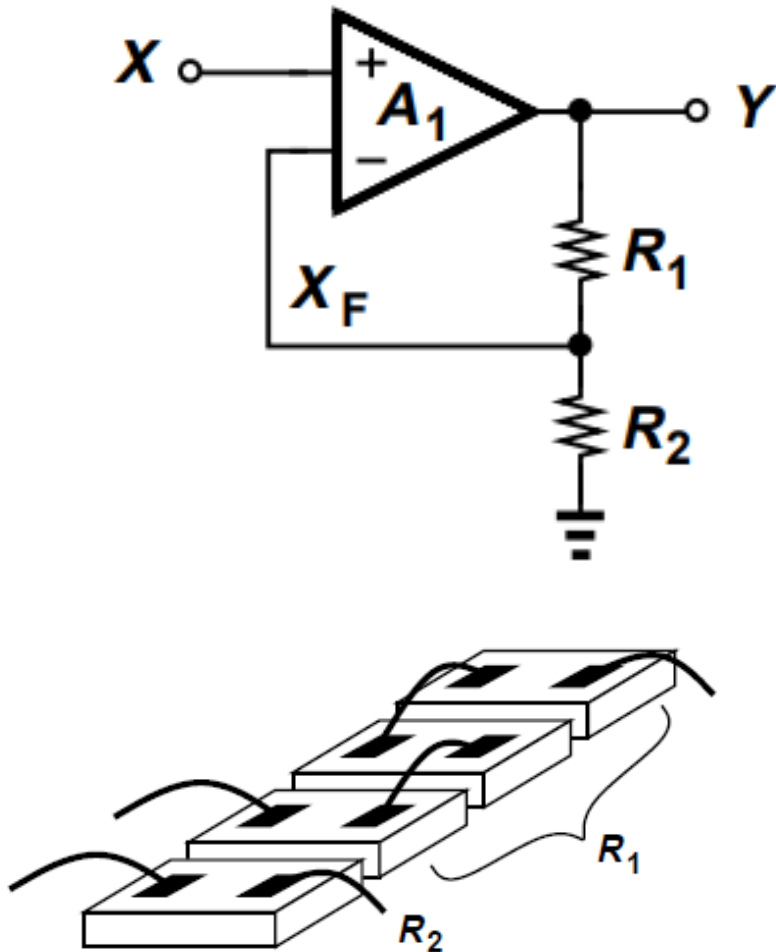

The op amp  $A_1$  performs two functions:


- subtraction
- Amplification

What is the closed-loop gain?

$$A_{cL} = \frac{Y}{X} = \frac{A_1}{1 + K A_1} = \frac{A_1}{1 + \frac{R_2}{R_1 + R_2} A_1}$$
$$A_{cL} \approx \frac{R_1 + R_2}{R_2} = 1 + \frac{R_1}{R_2}, \text{ if } \frac{R_2}{R_1 + R_2} A_1 \gg 1$$

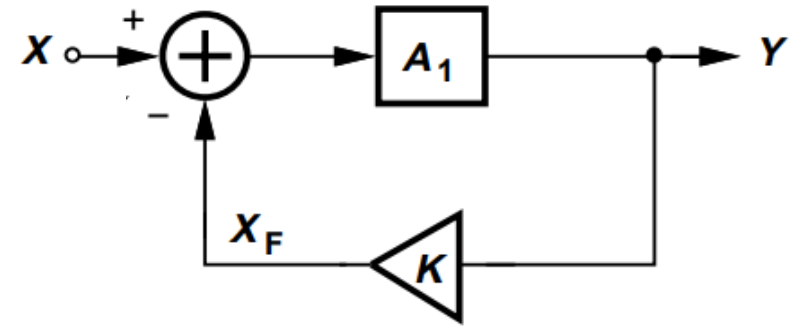
# Loop-gain

- Open-loop gain:  $A_1$
- Closed-loop gain:  $A_{cL} = \frac{Y}{X} = \frac{A_1}{1+KA_1}$
- Loop-gain:  $KA_1$ 
  - Procedure to measure loop-gain
    - Set the input  $X$  to zero (  $X$  is voltage  $\rightarrow$  AC ground; if  $X$  is current  $\rightarrow$  open)
    - Break the loop at an arbitrary point
    - Apply a test signal  $V_{test}$  at one terminal and measure the signal  $V_F$  at the other terminal
    - Calculate the loop-gain  $-\frac{V_F}{V_{test}} = KA_1$ 
      - $\frac{V_F}{V_{test}} < 0 \rightarrow$  negative feedback
      - $\frac{V_F}{V_{test}} > 0 \rightarrow$  positive feedback







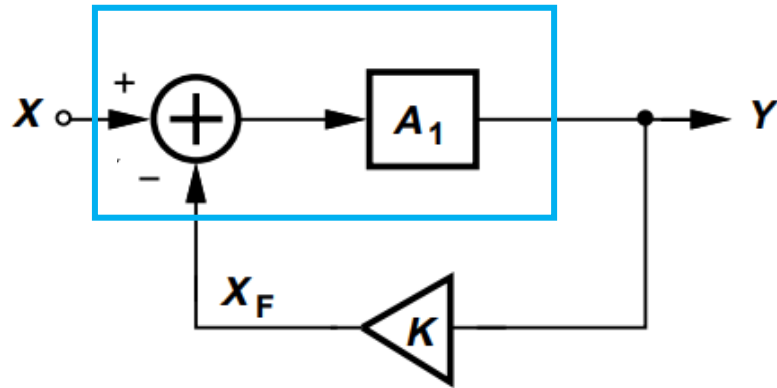
# Apply feedback to transistor amplifiers



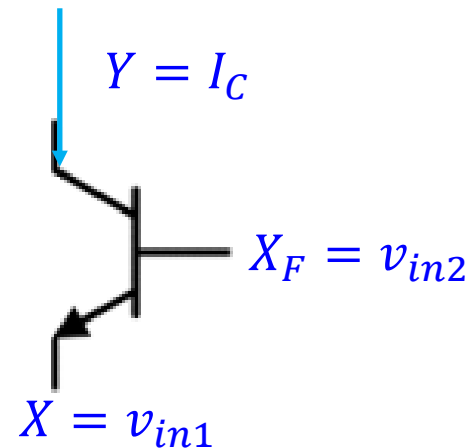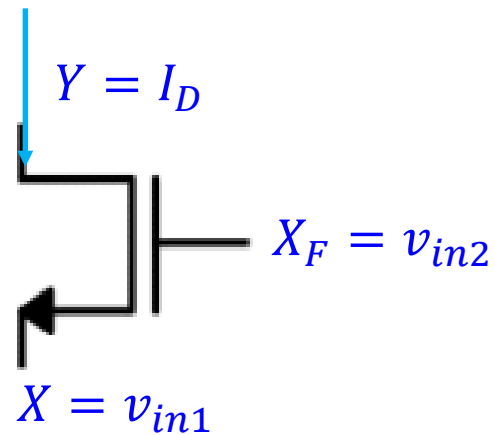- Two input, one output
- Generates the output that proportional to the deviation of the two inputs.



Quiz:  $\frac{Y}{X} = ?$

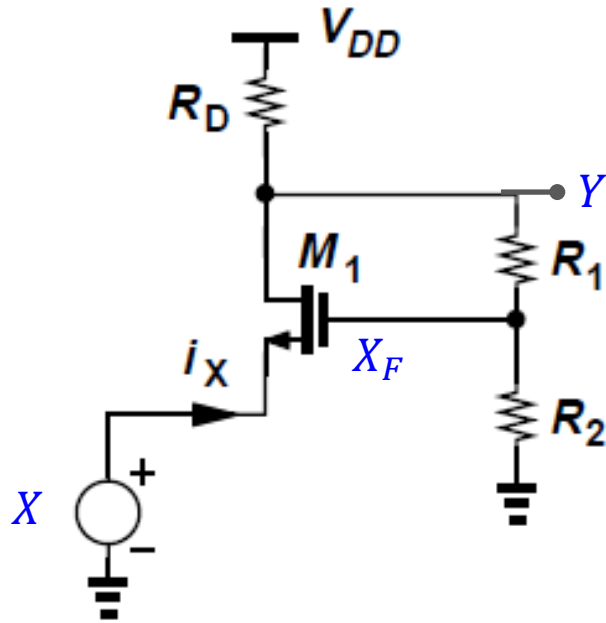

Assume  $R_1$  and  $R_2$  are very large

$$\Rightarrow A_1 = g_m R_D$$



# Summary of negative feedback concept

- Sacrifice the open-loop gain  $A_1$  to benefit from negative feedback
- The feedback signal  $X_F$  is a good copy of input signal  $X$
- The feedback factor  $K$  is normally independent to frequency
  - Make  $Y$  a good (scaled by  $1/K$ ) copy of  $X$ 
    - Wider frequency band
    - Better linearity
- If loop-gain  $KA_1 \gg 1 \Rightarrow A_{cL} \approx \frac{1}{K}$ , relatively independent of  $A_1$ 
  - Factors that cause  $A_1$  to vary have less impact on the closed-loop gain
  - Factors: temperature, supply voltage, frequency, load impedance

# Properties of negative feedback

- Gain desensitization
- Bandwidth extension
- Linearity improvement
- Modification of input and output impedance

# Gain desensitization example

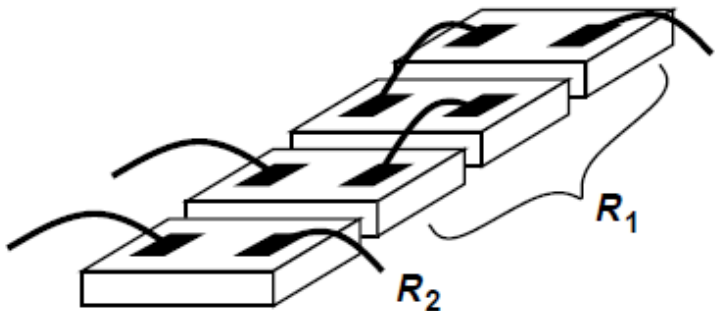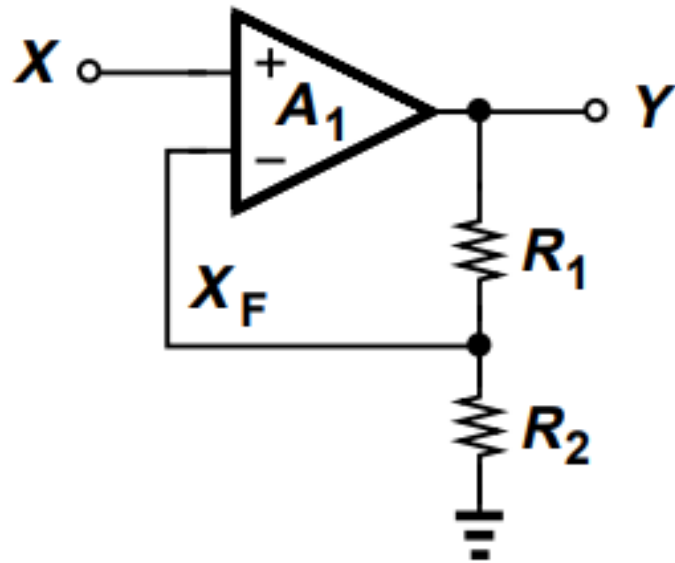


Assume the nominal gain of  $A_1=100$  and  $\frac{R_1}{R_2} = 3$ . Due to e.g., temperature, supply voltage, frequency and loading impedance,  $A_1$  drops to 50.

- How does the closed-loop gain  $A_{cL}$  change?


$$A_{cL} = \frac{Y}{X} = \frac{A_1}{1 + K A_1} = \frac{A_1}{1 + \frac{R_2}{R_1 + R_2} A_1}$$

# Bandwidth extension

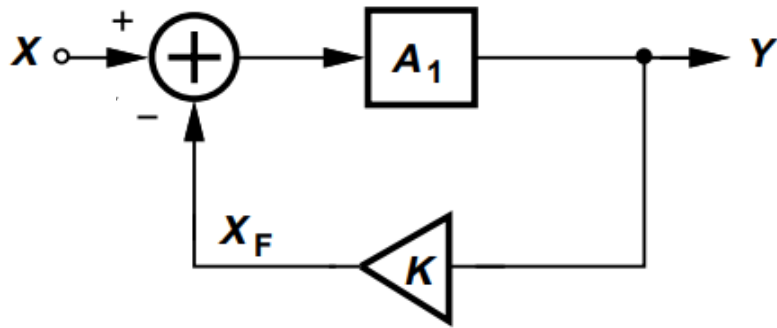

$$A_1(s) = \frac{A_0}{1 + s/\omega_0}$$
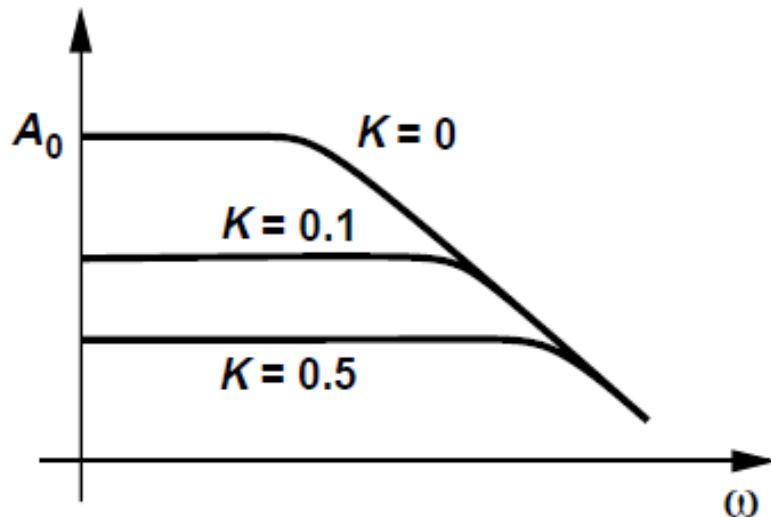
$$A_{cL}(s) = \frac{A_1(s)}{1 + KA_1(s)}$$




Closed-loop gain = ?

Closed-loop bandwidth = ?

Gain x Bandwidth is constant!


# Linearity improvement

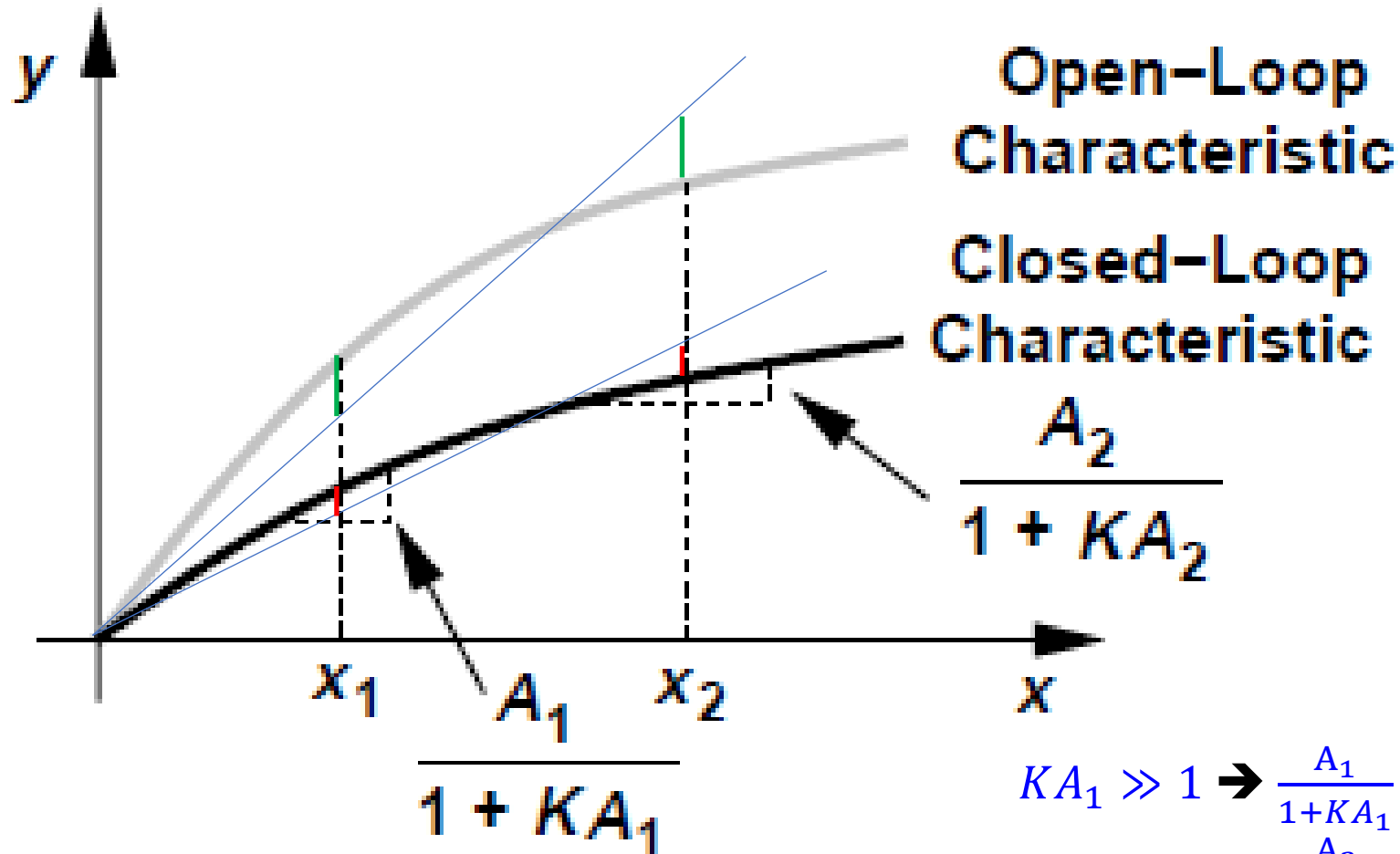


$$KA_1 \gg 1 \rightarrow \frac{A_1}{1 + KA_1} \approx K, \text{ when } KA_1 \gg 1$$

$$KA_2 \gg 1 \rightarrow \frac{A_2}{1 + KA_2} \approx K, \text{ when } KA_2 \gg 1$$


# Ideal Vs. real sources

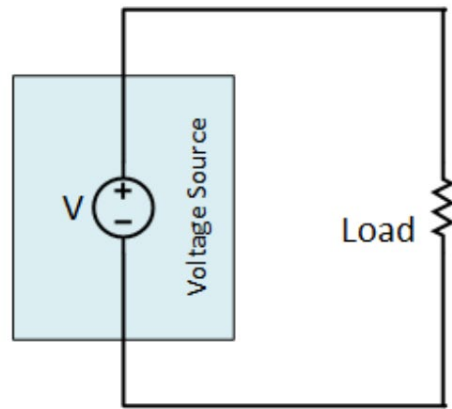


Ideal Voltage  
Source

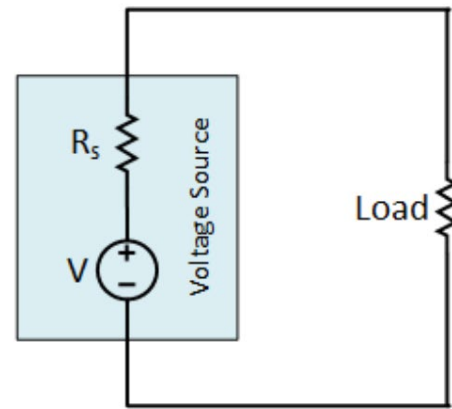

Practical Voltage  
Source

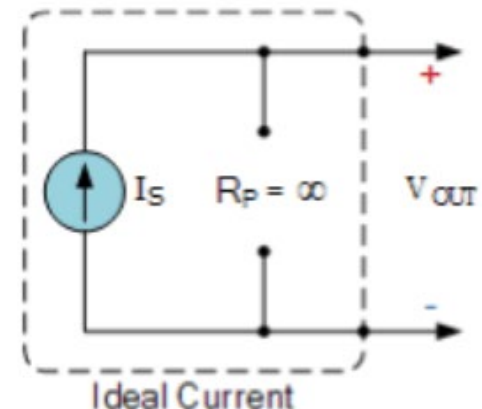




Ideal Current  
Source

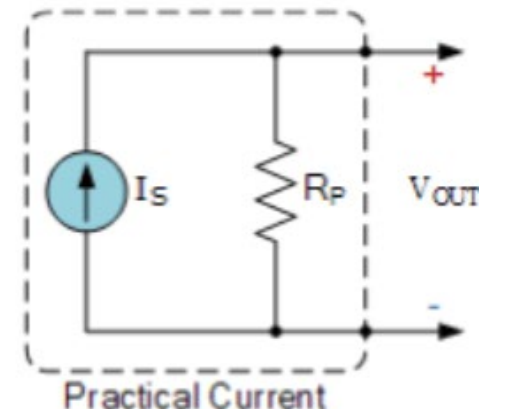

Practical Current  
Source




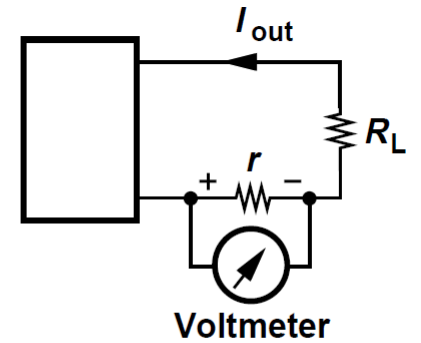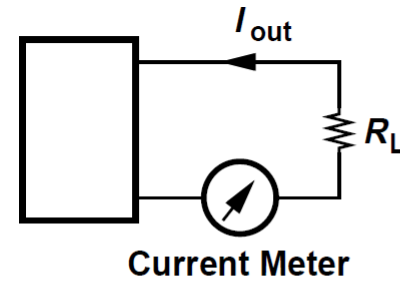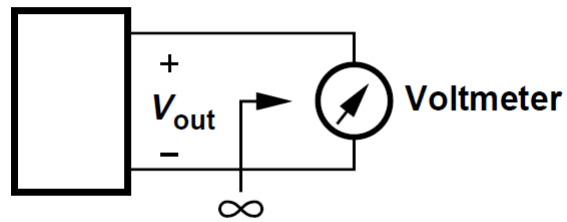
# How to sense/measure voltage or current




(a)

(b)

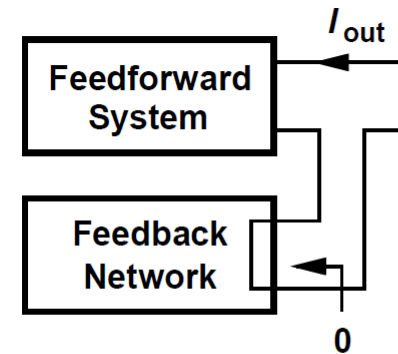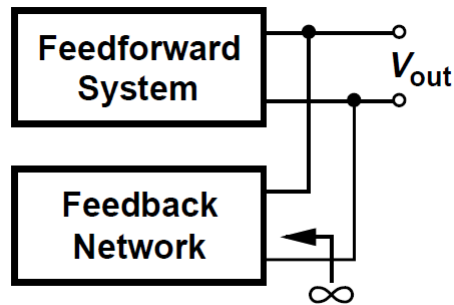


(c)

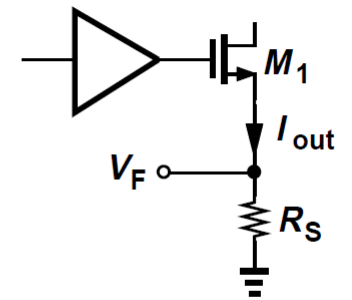

(d)

# Modification of input and output impedance

## Voltage-voltage FB

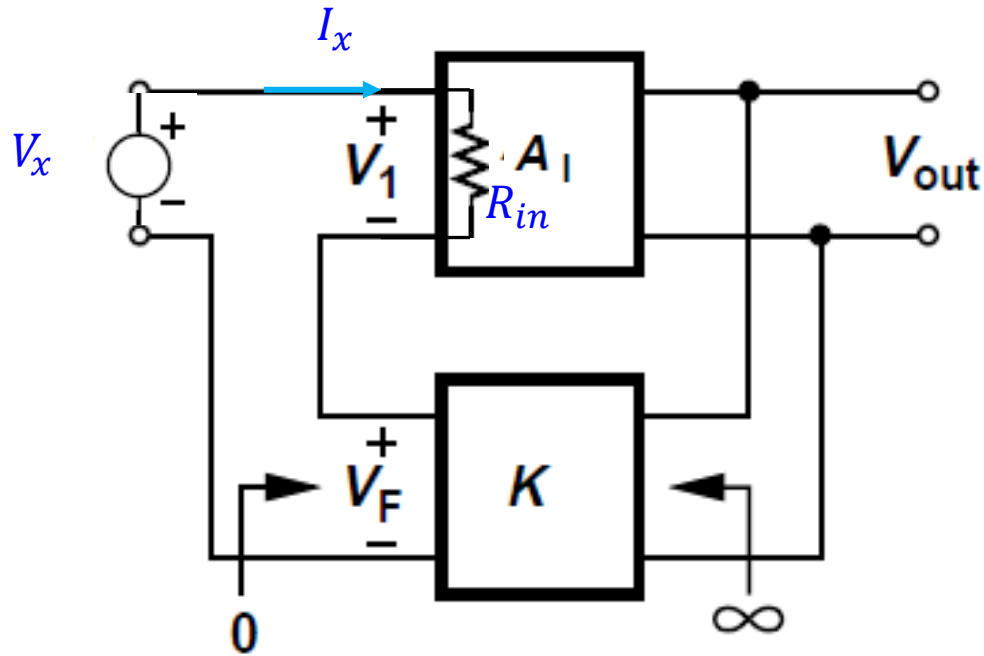

$$V_1 = I_x R_{in}$$


$$V_{out} = A_1 I_x R_{in}$$

$$V_F = K A_1 I_x R_{in}$$

$$V_x = V_1 + V_F$$

$$\Rightarrow R_{in,CL} = V_x / I_x = R_{in} (1 + K A_1)$$

*A better voltage sensor*

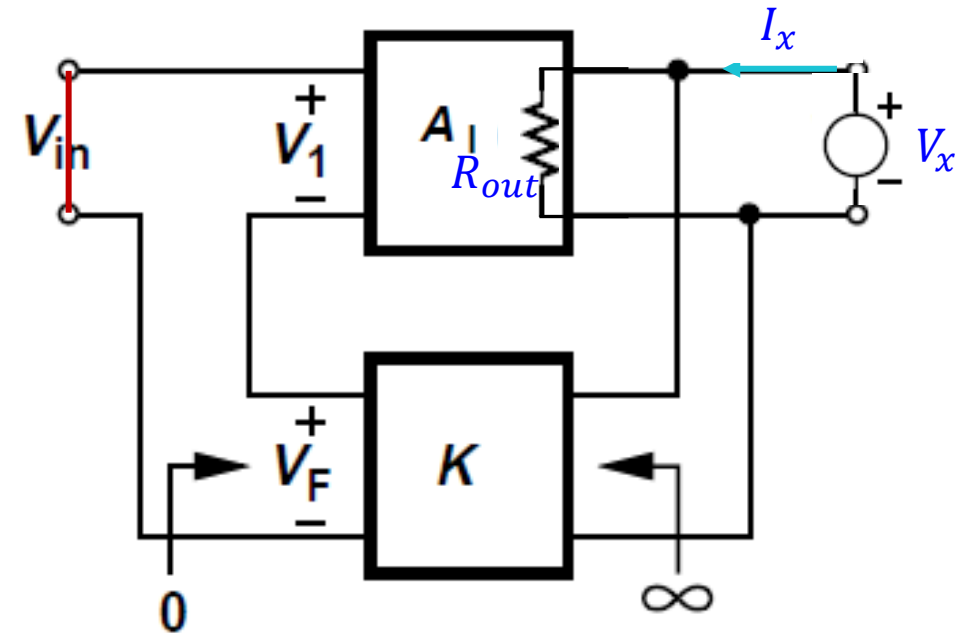


$$V_x = I_x R_{out}$$

$$V_1 = -V_F = -K V_x$$

$$\Rightarrow R_{out,CL} = V_x / I_x = R_{out} / (1 + K A_1)$$

*A better voltage source*
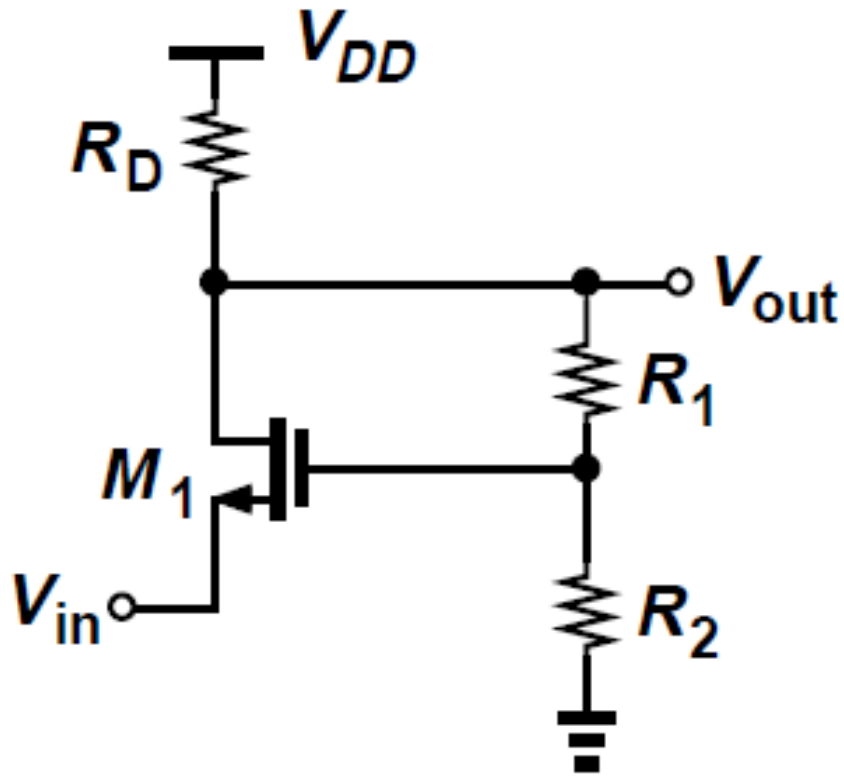
# Modification of input and output impedance



Assume  $R_1 + R_2 \gg R_D$

$$A_1 = g_m R_D$$

$$K = \frac{R_2}{R_1 + R_2}$$

$$A_{CL} = \frac{A_1}{1 + KA_1}$$


$$R_{in} = 1/g_m$$

$$R_{out} = R_D$$

$$R_{in,CL} = R_{in}(1 + KA_1)$$


$$R_{out,CL} = R_{out}/(1 + KA_1)$$

# Feedback topologies

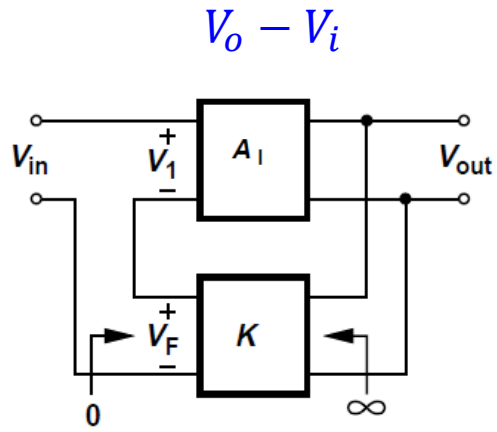


$$R_{in,CL} = R_{in}(1 + KA_1)$$

$$R_{out,CL} = R_{out}/(1 + KA_1)$$

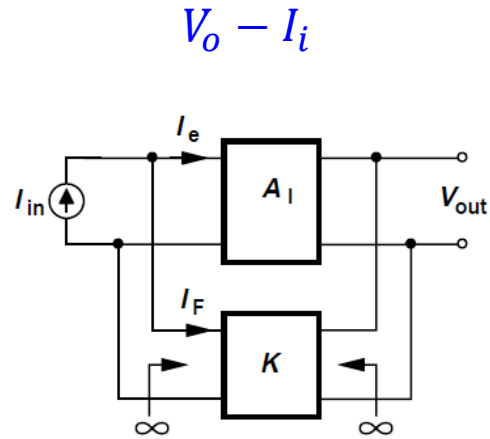


$$R_{in,CL} = R_{in}/(1 + KA_1)$$

$$R_{out,CL} = R_{out}/(1 + KA_1)$$

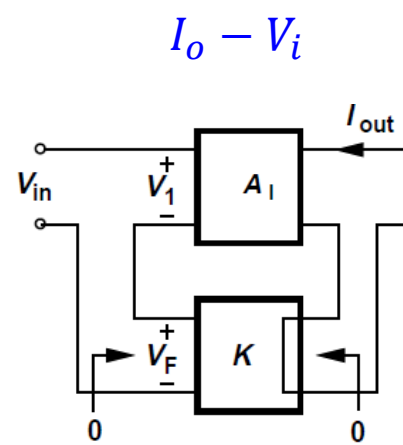

$$R_{in,CL} = R_{in}(1 + KA_1)$$





$$R_{out,CL} = R_{out}(1 + KA_1)$$

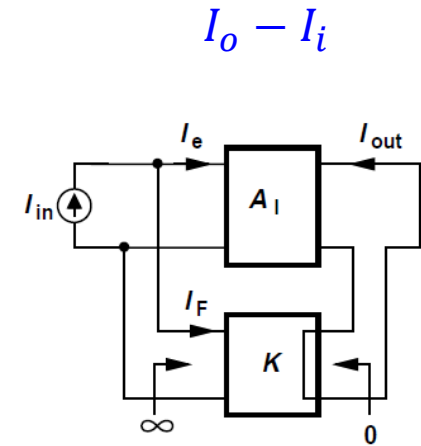




$$R_{in,CL} = R_{in}/(1 + KA_1)$$

$$R_{out,CL} = R_{out}(1 + KA_1)$$
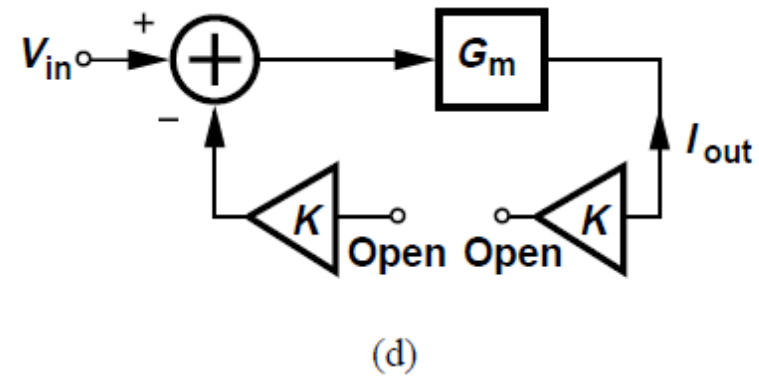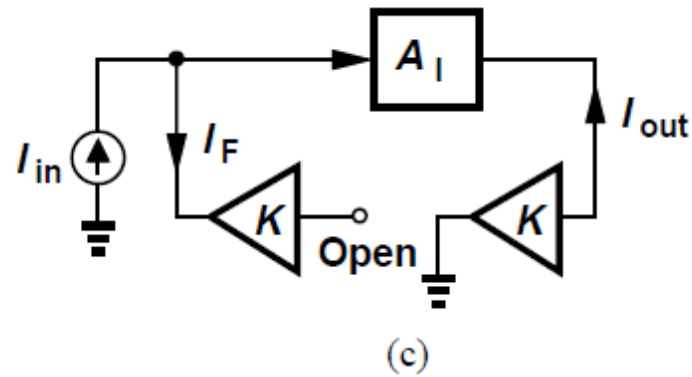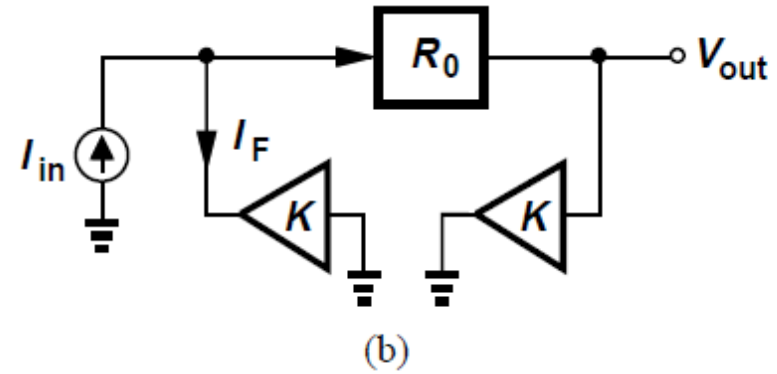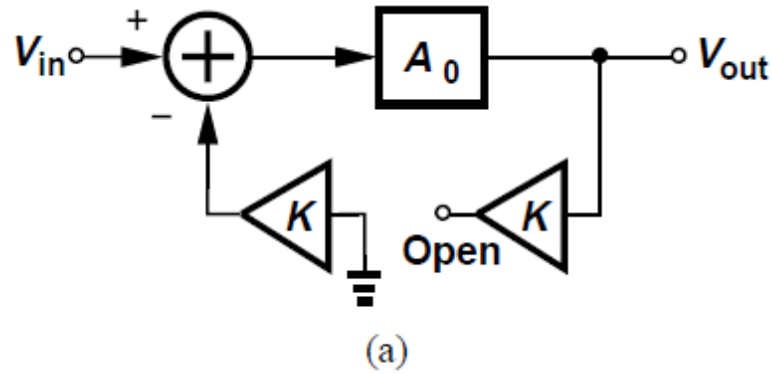
# Rules for breaking the feedback network(self-study)


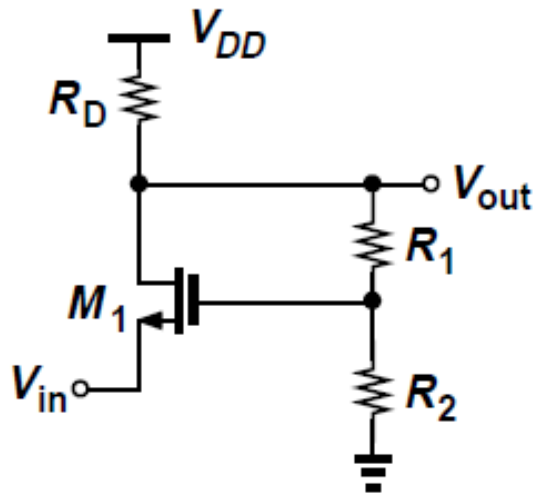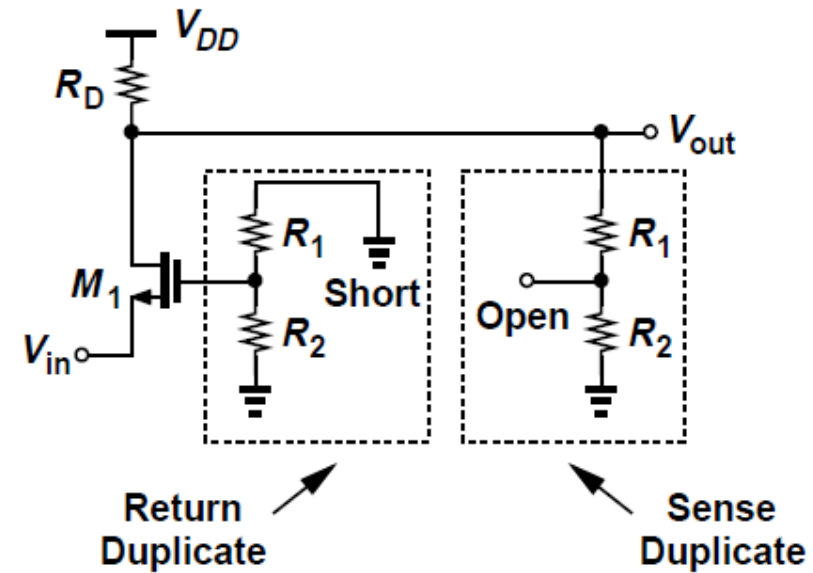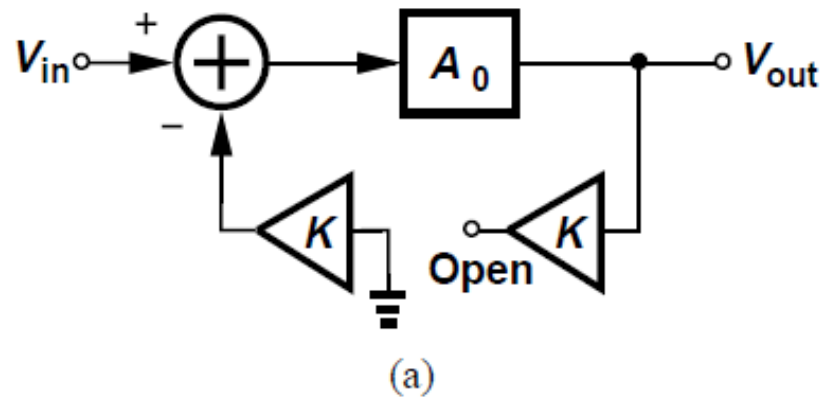
# Rules for breaking the feedback network




$$K = \frac{R_2}{R_1 + R_2}$$

$$A_1 = g_m [R_D || (R_1 + R_2)]$$

$$R_{in} = 1/g_m$$

$$R_{out} = R_D || (R_1 + R_2)$$

# Instability in FB system

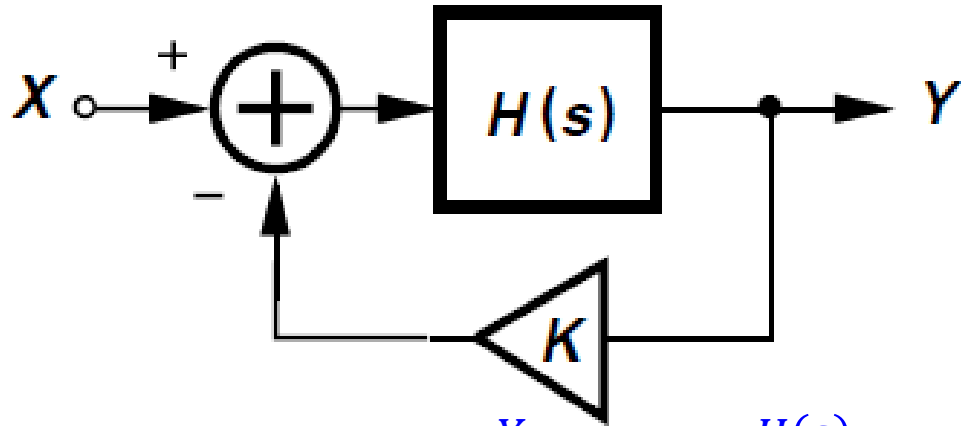

Loop transmission:  $\frac{Y}{X}(s) = \frac{H(s)}{1+KH(s)}$


For a certain input frequency  $\omega_1$ ,

$$KH(j\omega_1) = -1$$

$$\Rightarrow \frac{Y}{X}(j\omega_1) = \infty$$

Even  $X$  is very small,  $Y$  can be extremely large.

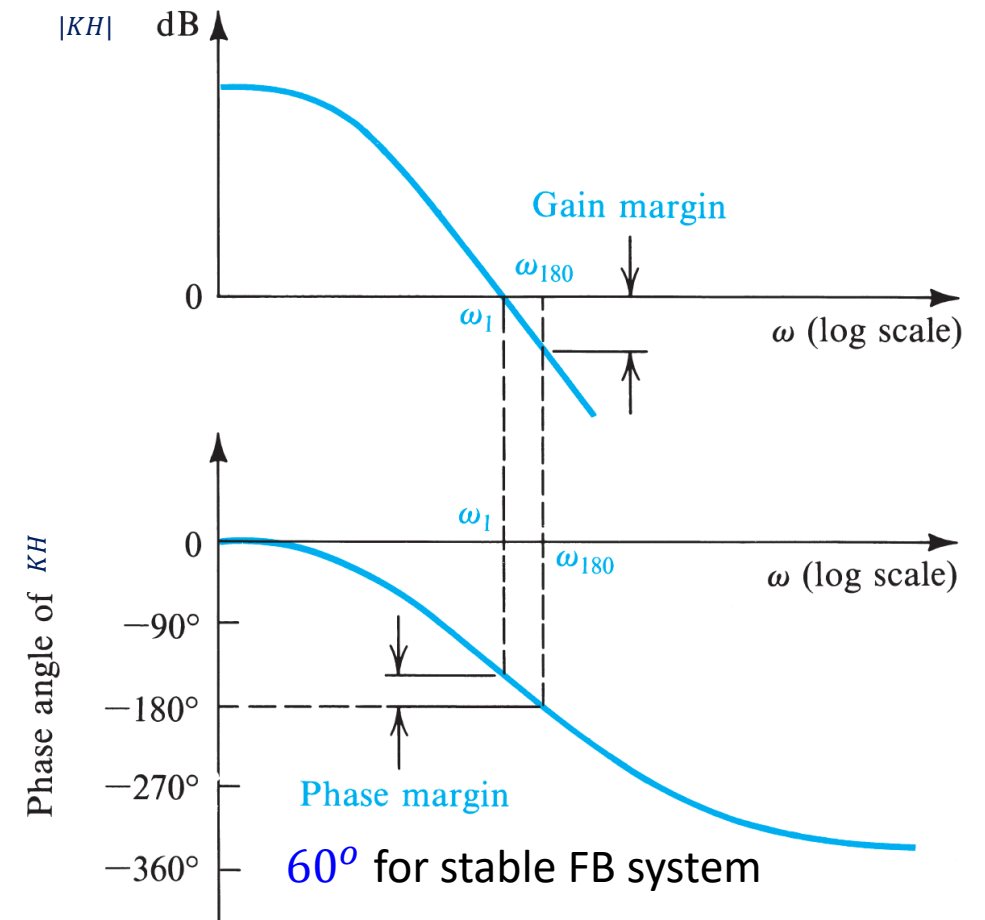- Acting like an oscillator
- Bad for building amplifiers



Unstable system:

$$|KH(j\omega_1)| \geq 1$$

$$\angle KH(j\omega_1) = 180^\circ$$

# Stability/compensation

- Reduce  $K \rightarrow \omega_1$  smaller  $\rightarrow$  more stable system but less control over the system
- Change the phase of  $H(s)$