

Bipolar Junction Transistors

Peng Mei

Department of Electronic Systems

Email: mei@es.aau.dk




AALBORG UNIVERSITY
DENMARK



Learning objectives:

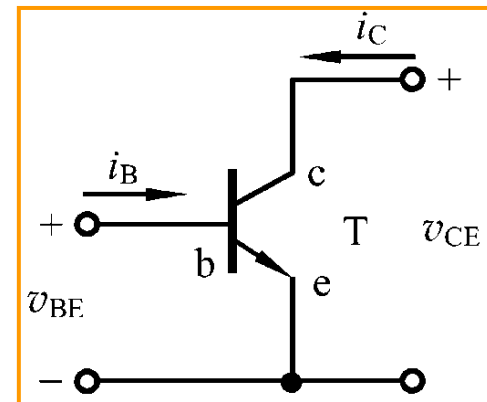- Simple NPN transistor model
- Concept of transconductance
- Large-signal and small-signal model






$$i_C = I_S \left(e^{(v_{BE}/V_T)} - 1 \right) = \frac{A_E q D_n n_i^2}{N_B W_B} \left(e^{(v_{BE}/V_T)} - 1 \right)$$

$$\approx \frac{A_E q D_n n_i^2}{N_B W_B} e^{(v_{BE}/V_T)}$$

$$i_B = \left(\frac{A_E q D_p n_i^2}{N_D L_p} + \frac{A_E q W n_i^2}{2\tau_b N_A} \right) \left(e^{(v_{BE}/V_T)} - 1 \right)$$
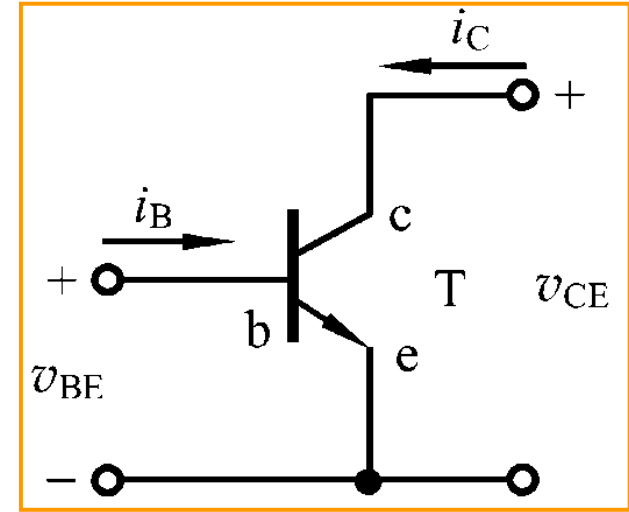
$$\approx \left(\frac{A_E q D_p n_i^2}{N_D L_p} + \frac{A_E q W n_i^2}{2\tau_b N_A} \right) e^{(v_{BE}/V_T)}$$




Current gain

$$\beta = \frac{i_C}{i_B}$$

$$i_B = \frac{i_C}{\beta} = \frac{I_S \left(e^{(v_{BE}/V_T)} - 1 \right)}{\beta} = \left(\frac{I_S}{\beta} \right) \left(e^{(v_{BE}/V_T)} - 1 \right)$$




According to KCL:

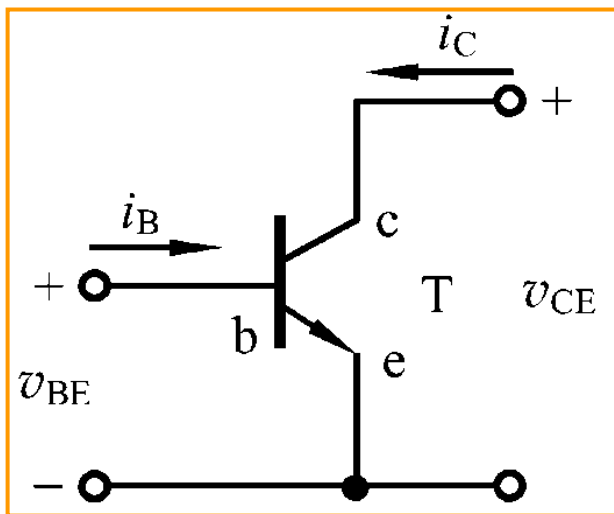

$$\begin{aligned} i_E &= i_B + i_C = \frac{i_C}{\beta} + i_C \\ &= \frac{\beta + 1}{\beta} i_C \\ &= \frac{\beta + 1}{\beta} I_S \left(e^{(v_{BE}/V_T)} - 1 \right) \end{aligned}$$

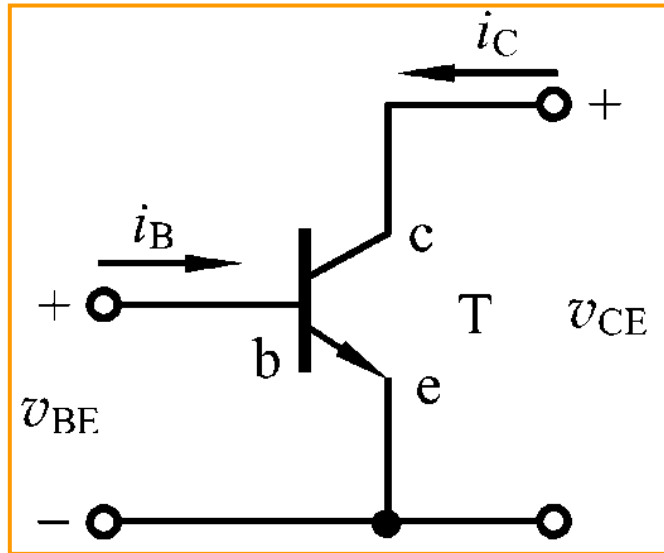
$$\alpha = \frac{i_C}{i_E} \quad \longrightarrow \quad \alpha = \frac{\beta}{\beta + 1} \quad \text{or} \quad \beta = \frac{\alpha}{1 - \alpha}$$




Can we simplify this circuit model?



Simple bipolar transistor model

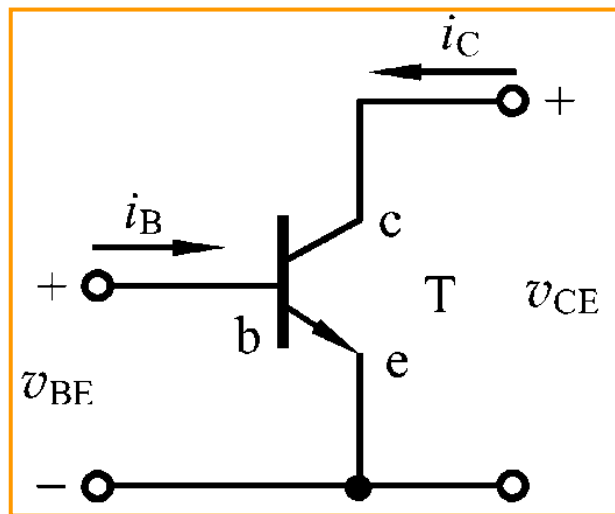

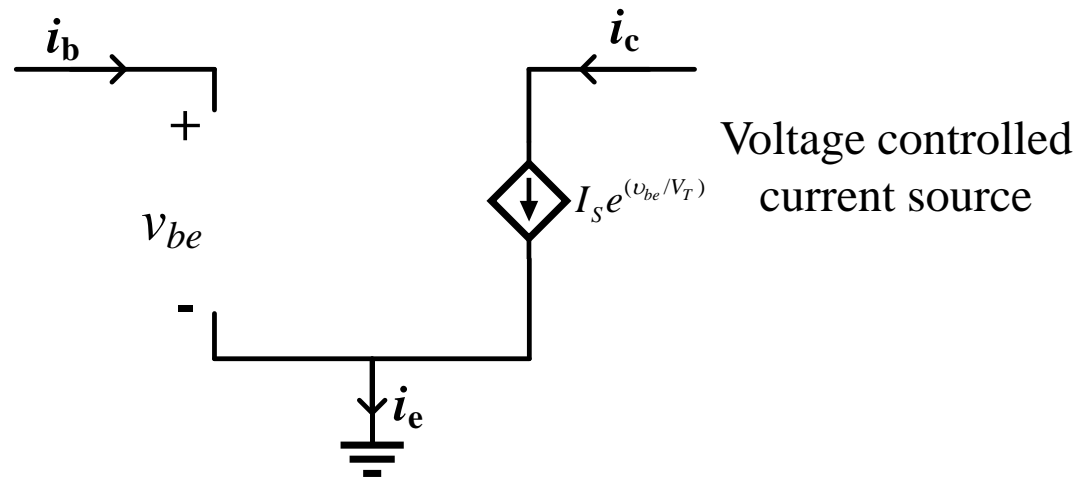
$$i_c = I_S \left(e^{(v_{be}/V_T)} - 1 \right) \approx I_S e^{(v_{be}/V_T)}$$







Simple bipolar transistor model

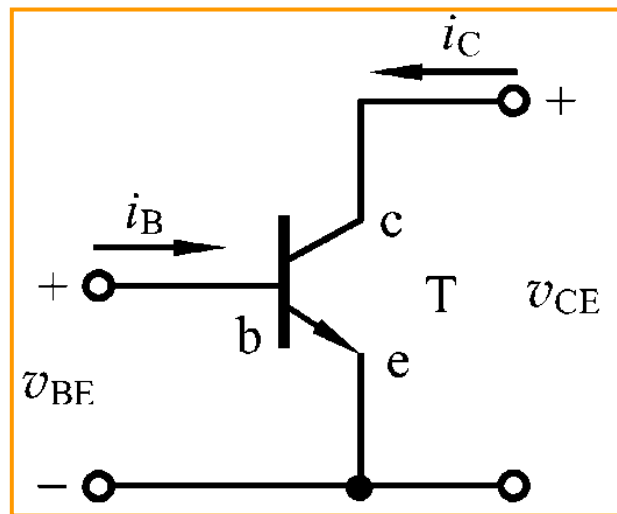

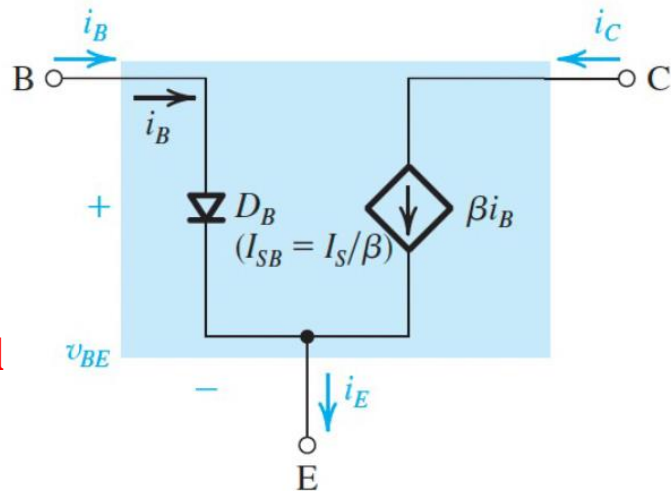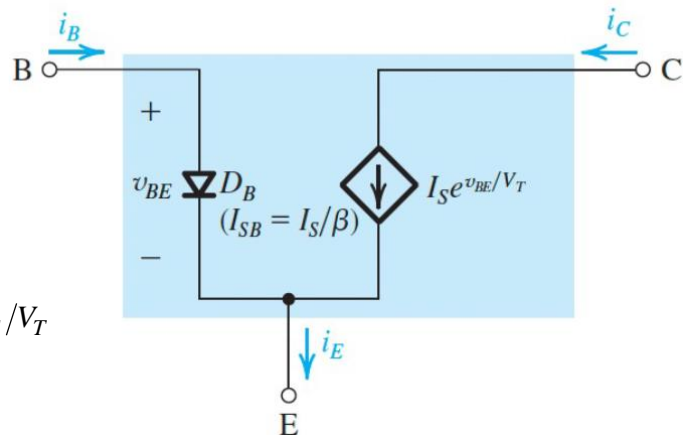
$$i_B = \frac{i_C}{\beta} = \frac{i_S}{\beta} e^{v_{BE}/V_T}$$



Application of a simple bipolar transistor model



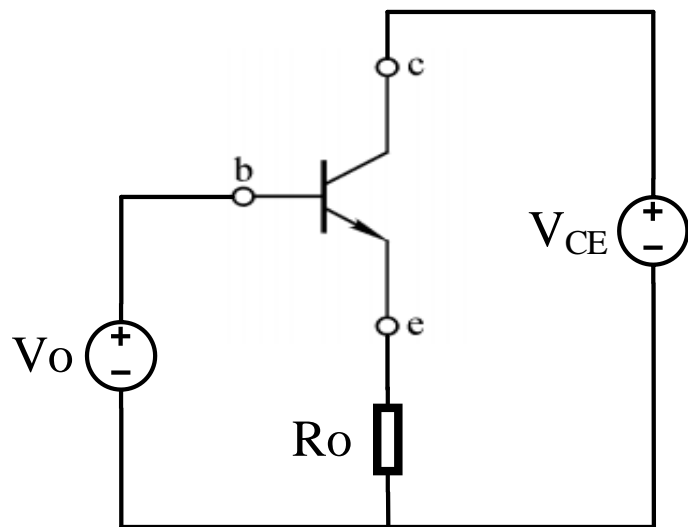Application of a simple bipolar transistor model




Calculate i_c ?

$$V_O = 5V, V_{CE} = 12V, R_O = 100 \Omega$$

$$I_S = 5 \times 10^{-16} A$$




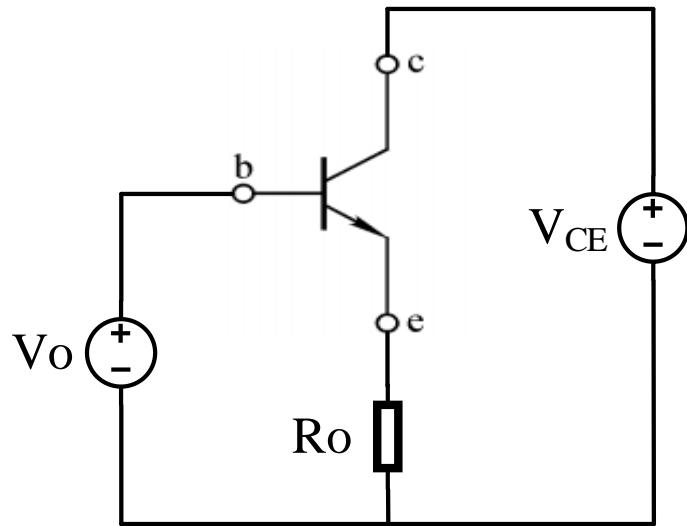Application of a simple bipolar transistor model



$$V_o = 5\text{V}, V_{CE} = 12\text{V}, R_o = 100\ \Omega$$


$$I_s = 5 \times 10^{-16}\text{ A}$$

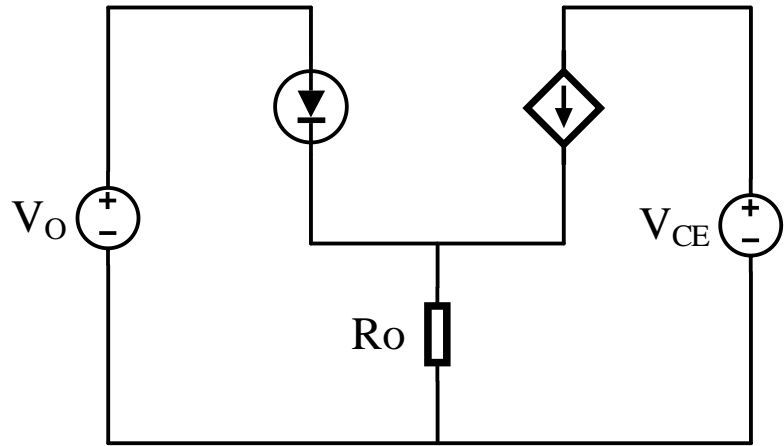

$$V_o = V_{BE} + R_o \cdot I_E \approx V_T \ln \frac{I_C}{I_s} + R_o \cdot I_C$$




Concept of transconductance:

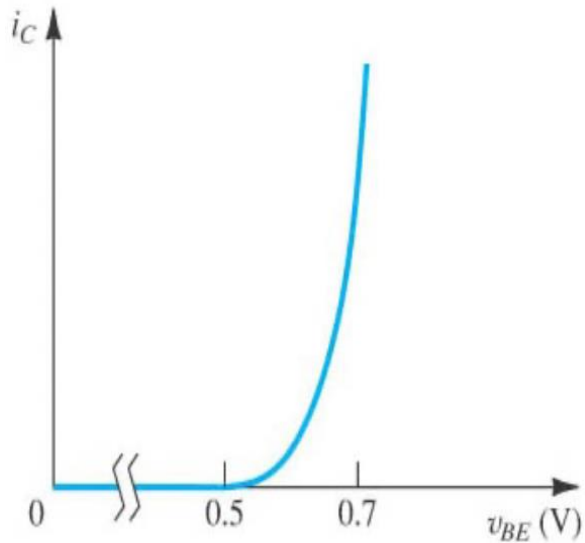

When v_{BE} has a fluctuation, how will it affect i_C ?



Concept of transconductance:

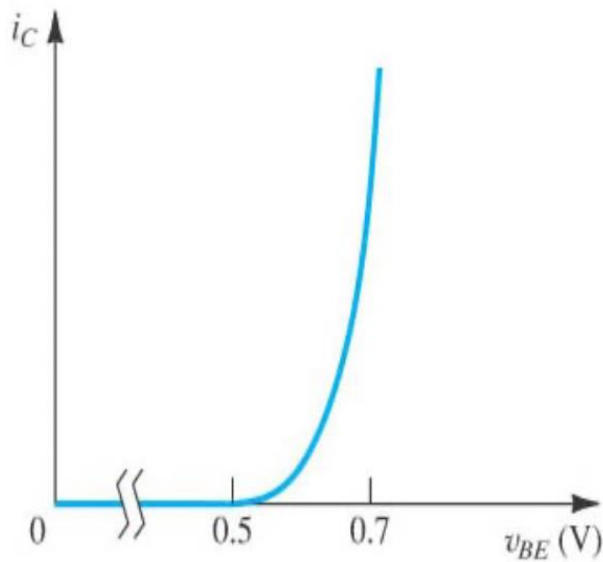

$$g_m = \frac{\Delta i_c}{\Delta v_{BE}} = \frac{di_c}{dv_{BE}}$$

$$i_c = I_S e^{v_{BE}/V_T}$$


$$g_m = \frac{d}{dv_{BE}} \left(I_S e^{v_{BE}/V_T} \right) = \frac{I_S}{V_T} e^{v_{BE}/V_T} = \frac{i_c}{V_T}$$



Large-signal and small-signal model:


Large-signal: the signal is arbitrarily large

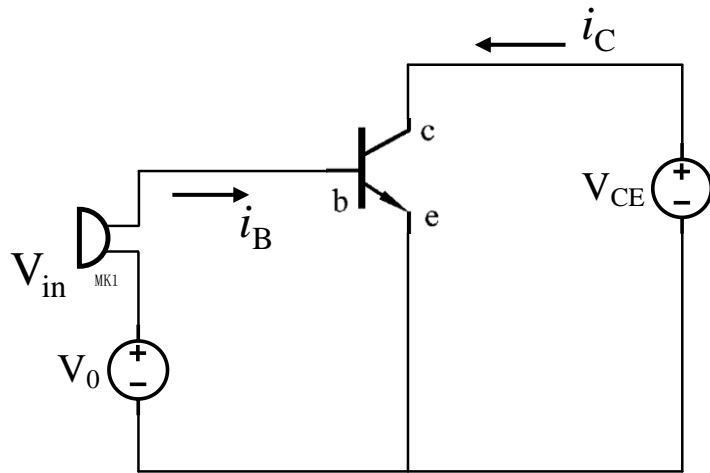Small-signal: the signal perturbs the bias point by only a small amount
(small compared to V_T)






$$V_{in} = V_m \sin \omega t$$

$$\begin{aligned} i_C &= I_s e^{\left(\frac{V_0 + V_{in}}{V_T}\right)} = I_s e^{\left(\frac{V_0}{V_T}\right)} \cdot e^{\left(\frac{V_m \sin \omega t}{V_T}\right)} \\ &= I_{CO} \cdot e^{\left(\frac{V_m \sin \omega t}{V_T}\right)} \approx I_{CO} \cdot \left(1 + \frac{V_m \sin \omega t}{V_T}\right) \\ &= I_{CO} + \frac{I_{CO}}{V_T} V_m \sin \omega t \\ &= I_{CO} + g_m V_m \sin \omega t \end{aligned}$$

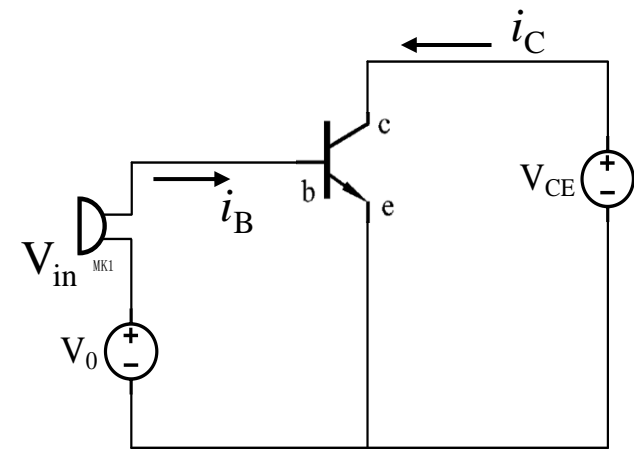


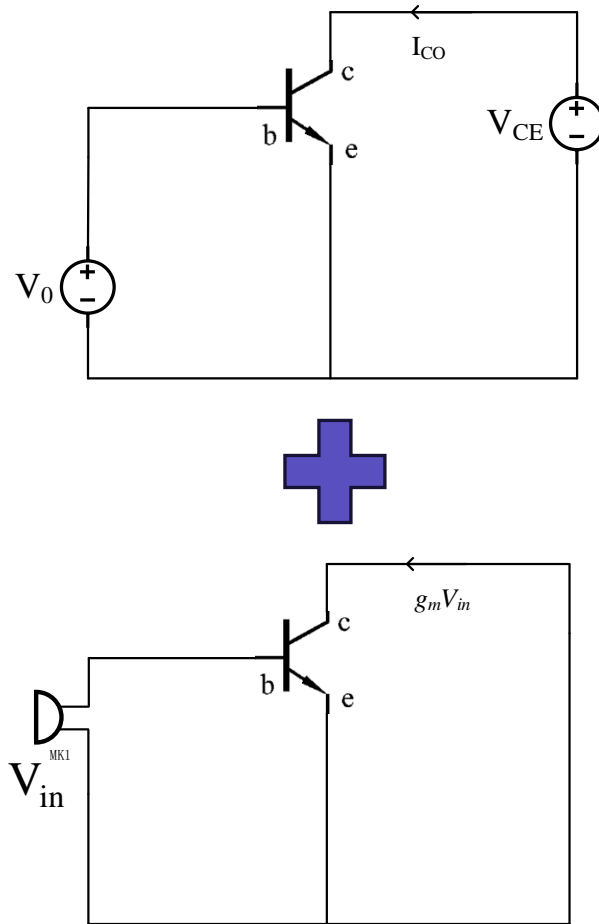
In small-signal model:
DC sources are short.



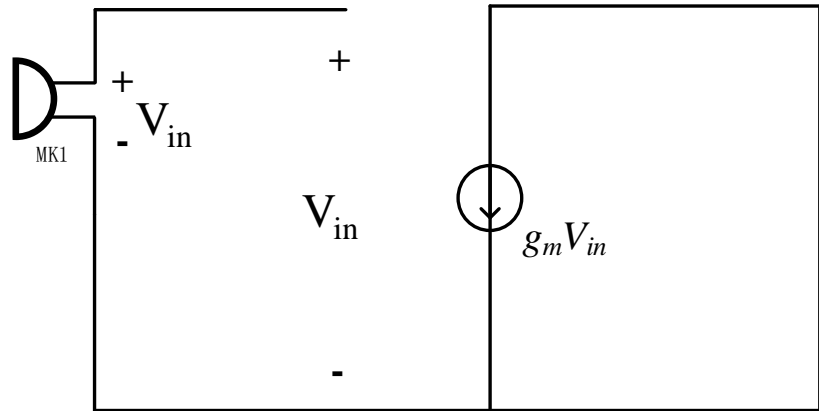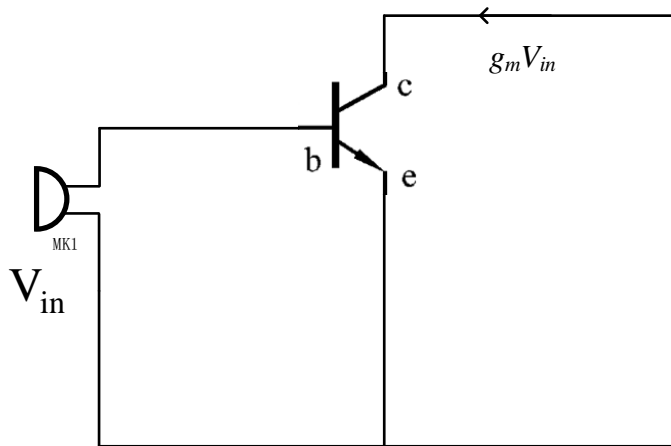

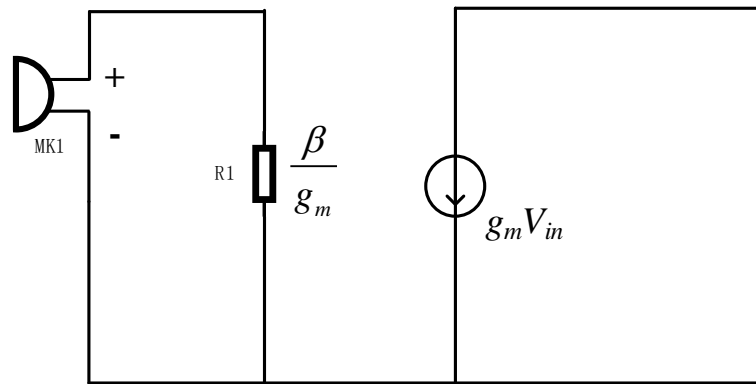
$$i_B = \frac{i_C}{\beta} = \frac{i_{CO}}{\beta} + \frac{g_m V_{in}}{\beta}$$



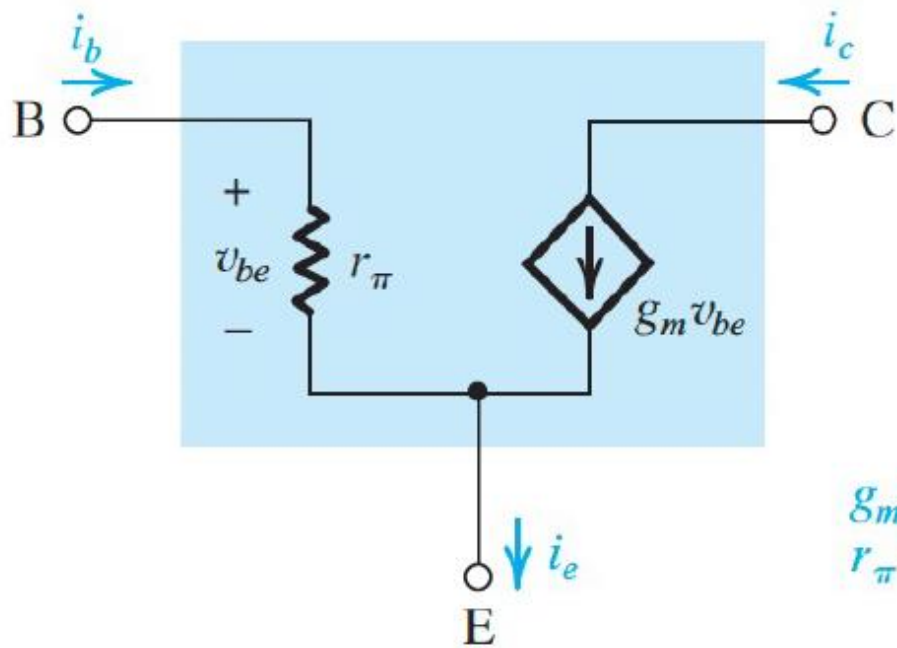
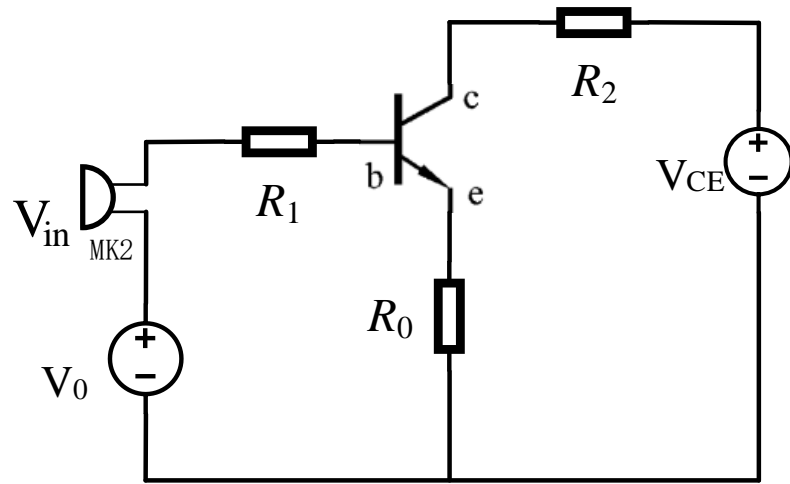
$$g_m = I_C / V_T$$
$$r_\pi = \beta / g_m$$



Draw the large-signal and small-signal models?



Thanks