

Analog Electronics


Fengchun Zhang

fz@es.aau.dk

Agenda

- Recap MOSFET and Frequency response
- Computation of frequency response
- Nonlinear system
 - General nonlinear system and harmonic distortion
 - Nonlinear system example—BJT
 - Nonlinear system example--MOSFET

Operation regions of MOSFET

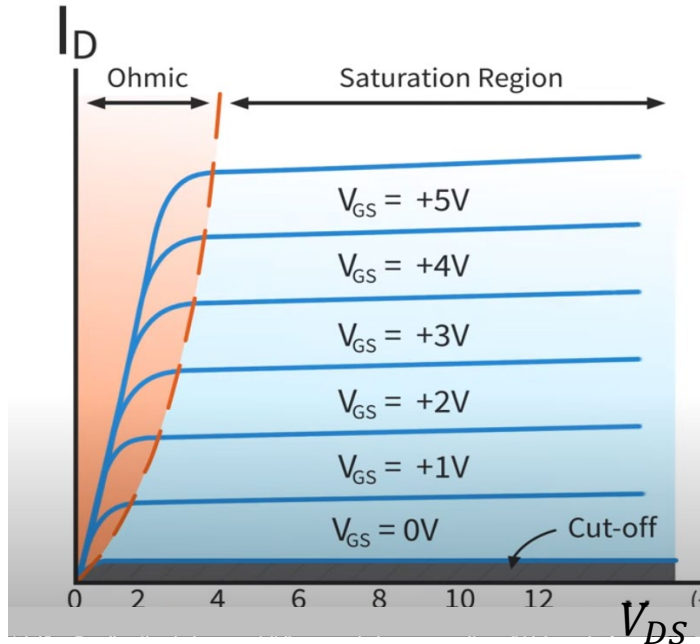

MOSFET transconductance parameter:

$$k_n = \mu_n C_{ox} W / L$$

- μ_n : mobility of the electrons at the surface of the channel
- C_{ox} : oxide capacitance
- W & L : width & length of the channel

Overdrive voltage: $V_{ov} = V_{GS} - V_{TH}$

Threshold voltage: V_{TH} ---- 0.3 V ~ 1V

$$I_D = \begin{cases} 0, & \text{cut-off} \\ k_n [(V_{GS} - V_{TH})V_{DS} - \frac{1}{2}V_{DS}^2], & \text{triode} \\ \frac{1}{2}k_n (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}), & \text{saturation} \end{cases}$$

cut-off: $V_{GS} < V_{TH}$

Triode and cut-off region: switching devices


triode: $V_{GD} > V_{TH}$

saturation: $V_{GD} < V_{TH}$

Saturation region: amplifier


Three basic configurations: MOSFET **VS.** BJT

MOSFET

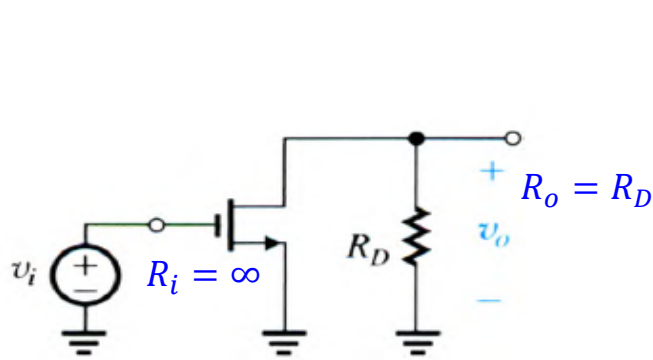


(a) Common-Source (CS)

$$A_v = -g_m R_D$$

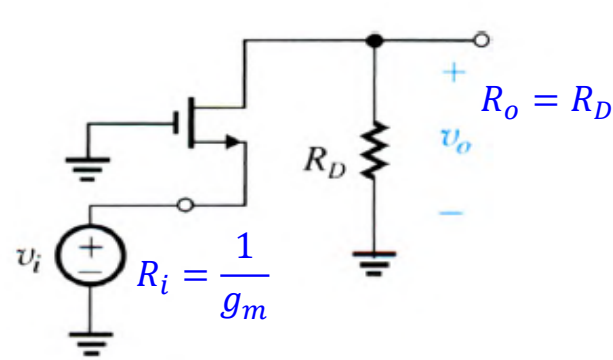

(b) Common-Gate (CG)


$$A_v = g_m R_D$$

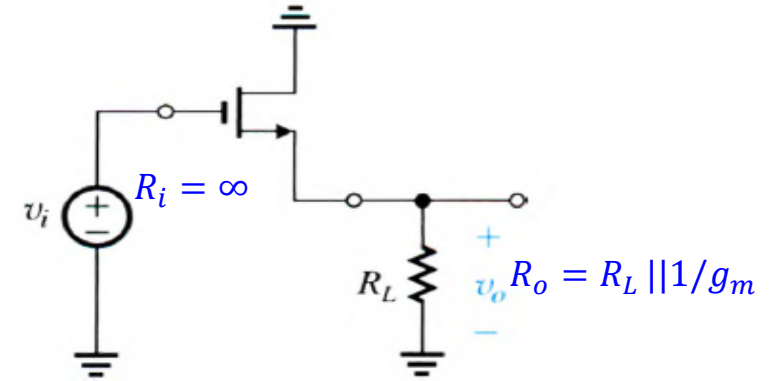

(c) Common-Drain (CD)
or Source Follower


$$A_v = \frac{R_L}{R_L + 1/g_m}$$

BJT

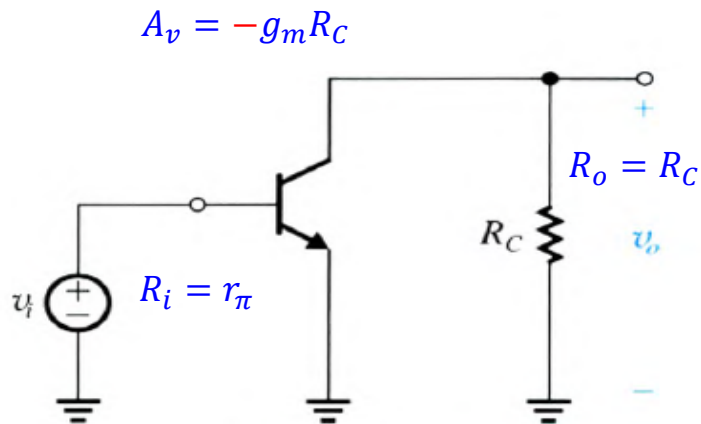


(d) Common-Emitter (CE)

$$A_v = -g_m R_C$$

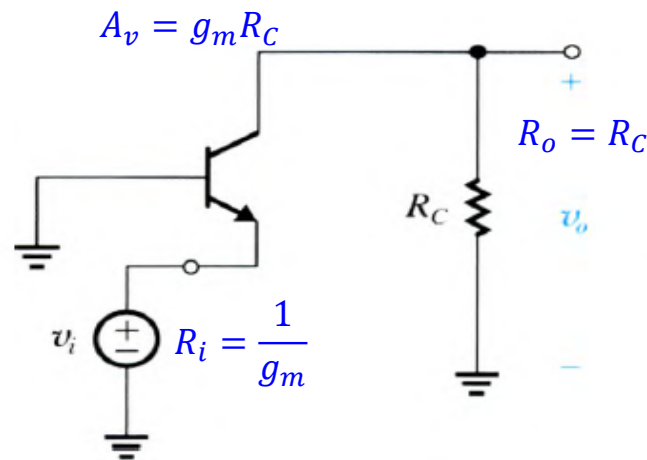

(e) Common-Base (CB)

$$A_v = g_m R_C$$

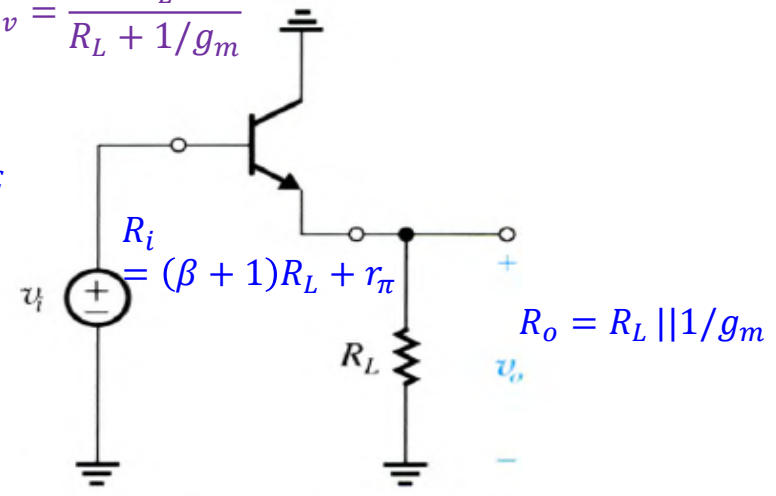

(f) Common-Collector (CC)
or Emitter Follower

$$R_o = R_L || \frac{1}{g_m}$$

Transfer function and frequency response

- The transfer function of a circuit:

$$H(s) = \frac{Y(s)}{X(s)} = A_0 \frac{(s - z_1)(s - z_2) \dots (s - z_M)}{(s - p_1)(s - p_2) \dots (s - p_N)}$$


$$A(\omega) = |H(j\omega)| = |A_0 \frac{(j\omega - z_1)(j\omega - z_2) \dots (j\omega - z_M)}{(j\omega - p_1)(j\omega - p_2) \dots (j\omega - p_N)}|$$

$$\omega = 2\pi f$$



z_m and p_n are zeros and poles

Bode's rules to fast construct $A(\omega)$ plot approximately:

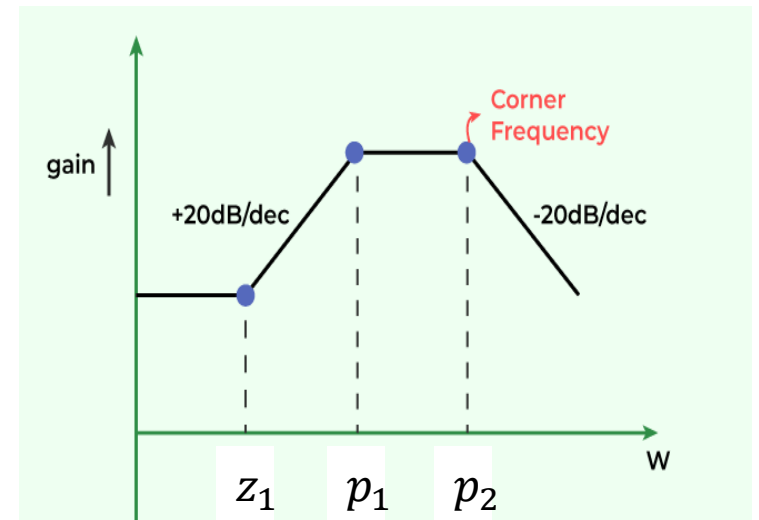As ω passes a **pole** / **zero**, the slope $A(\omega)$ **decreases** / **increases** by 20 dB/dec.




Miller's theorem

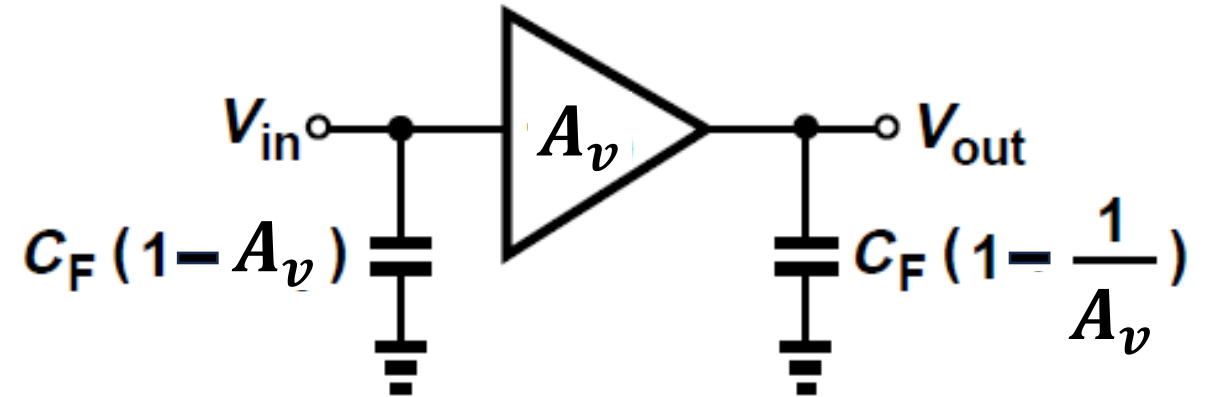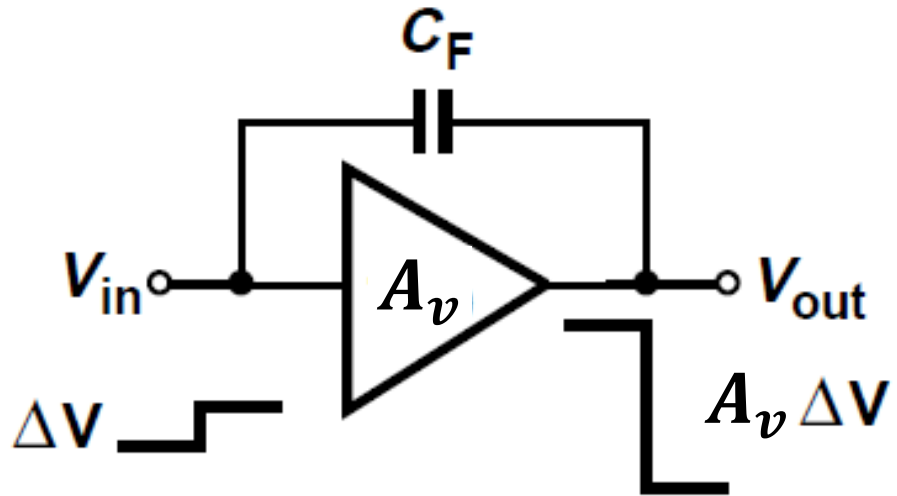


$$A_v = V_{out}/V_{in}$$

Decompose a floating capacitor into two grounded capacitors.


High-frequency models of BJT and MOSFET

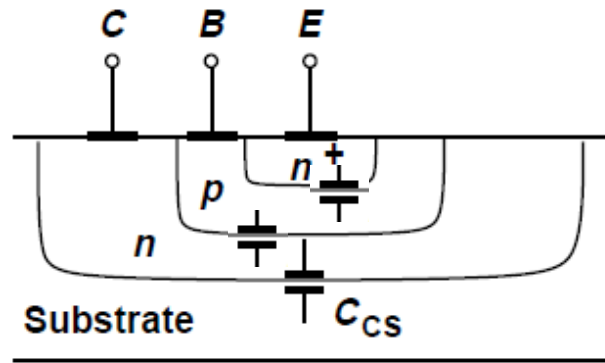




(a)

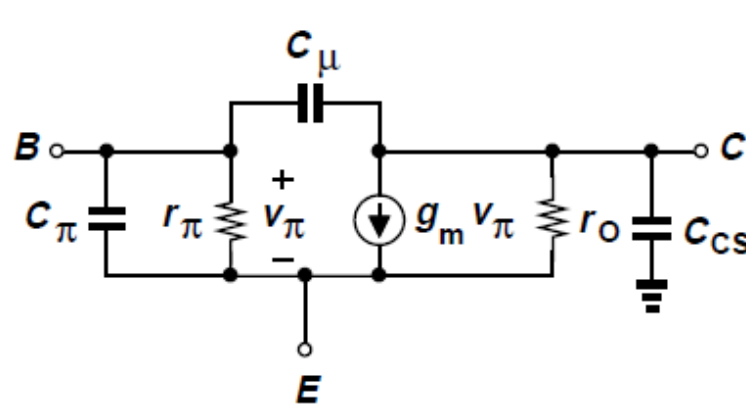

(b)

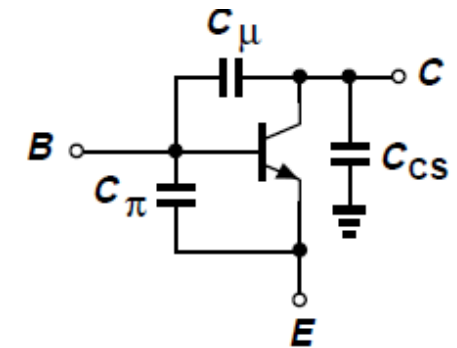

(c)

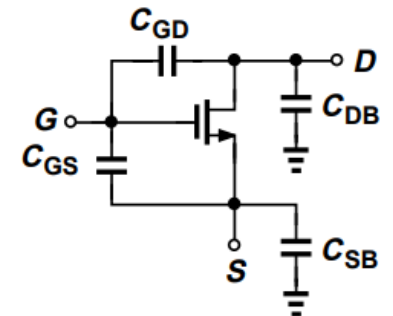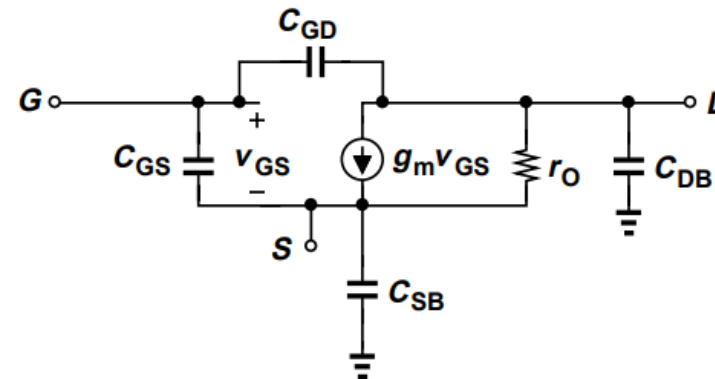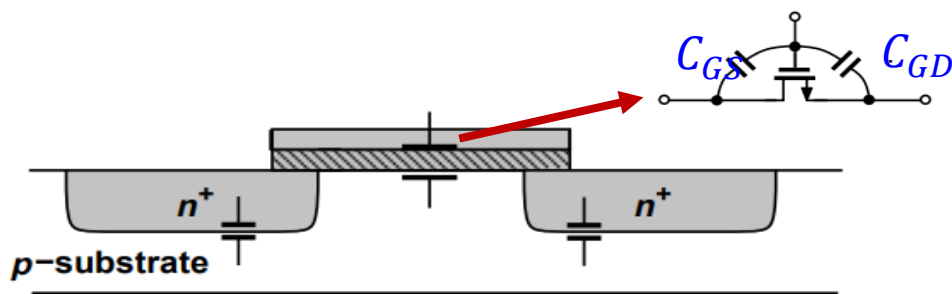

Agenda

- Recap MOSFET and Frequency response
- **Computation of frequency response**
- Nonlinear system
 - General nonlinear system and harmonic distortion
 - Nonlinear system example—BJT
 - Nonlinear system example--MOSFET

Computation of frequency response




- General procedure:

- Draw the circuit;
- Draw all of the device internal capacitors;
- Remove or merge capacitors;
- Write the transfer function $H(s)$;
- Plot the frequency response $|H(s = j\omega)|$.





Or approximation: find the poles by inspection

CE/CS frequency response

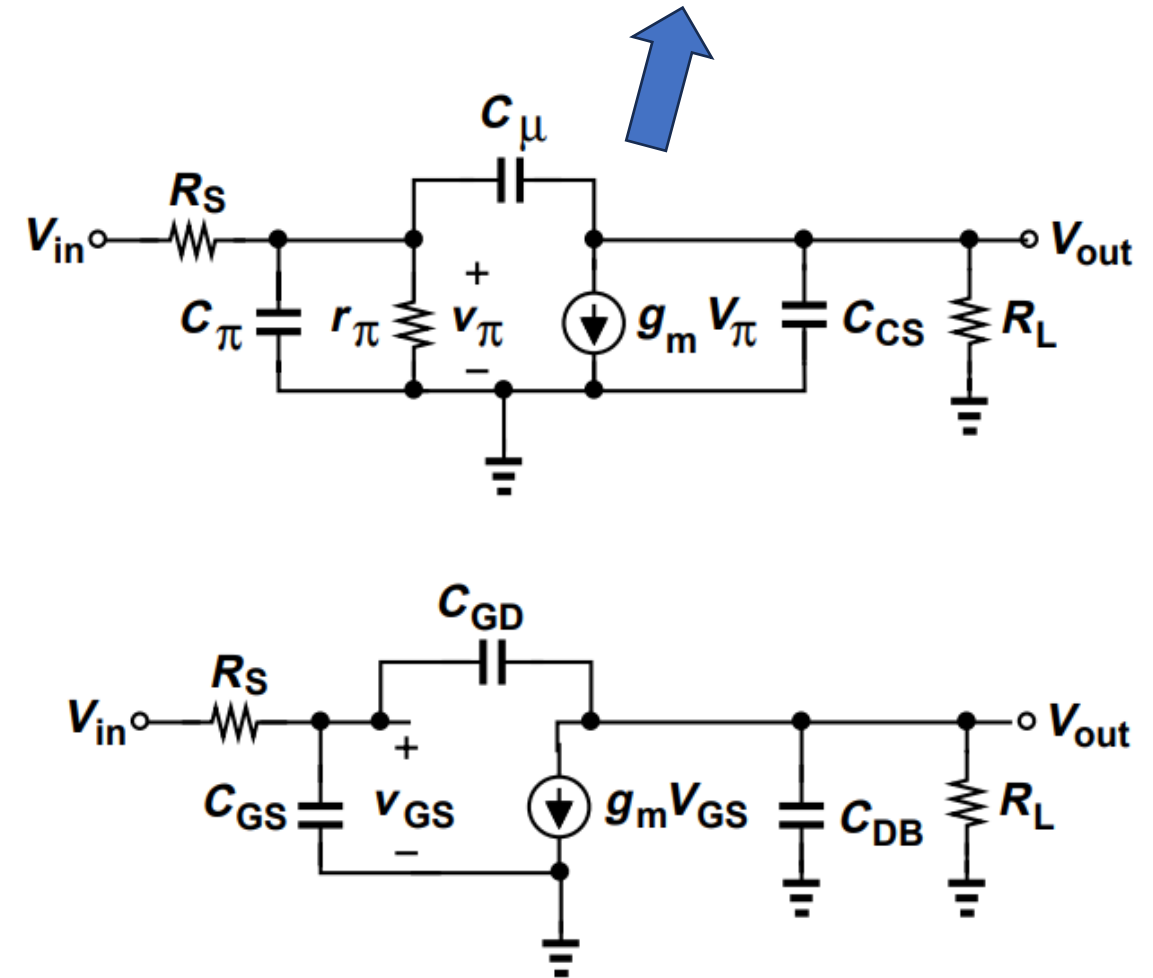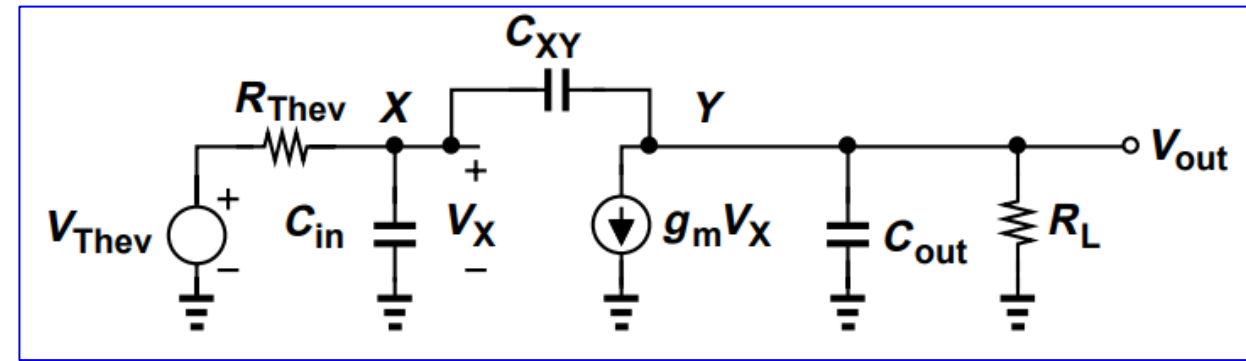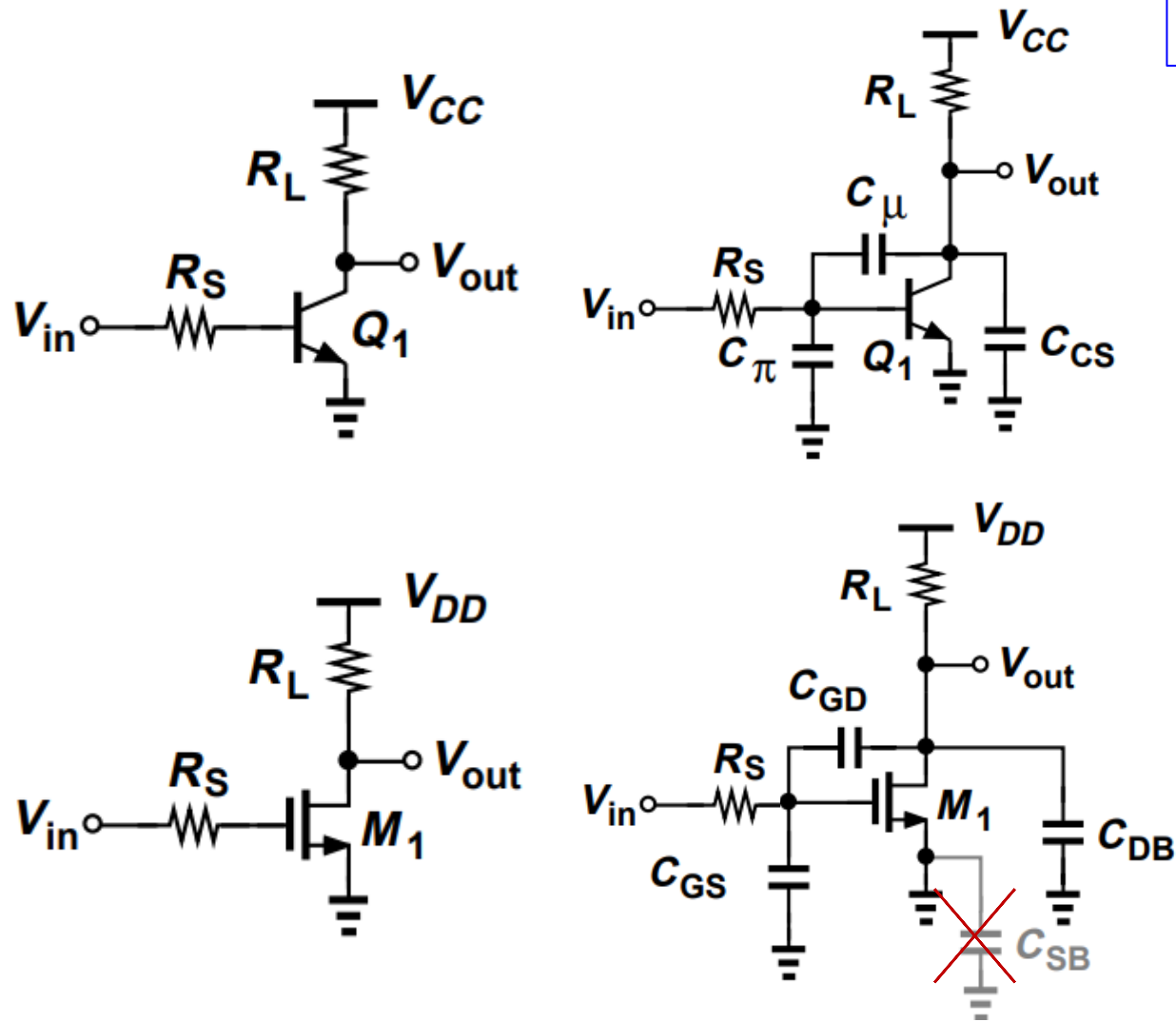

Approach I: finding poles by inspection

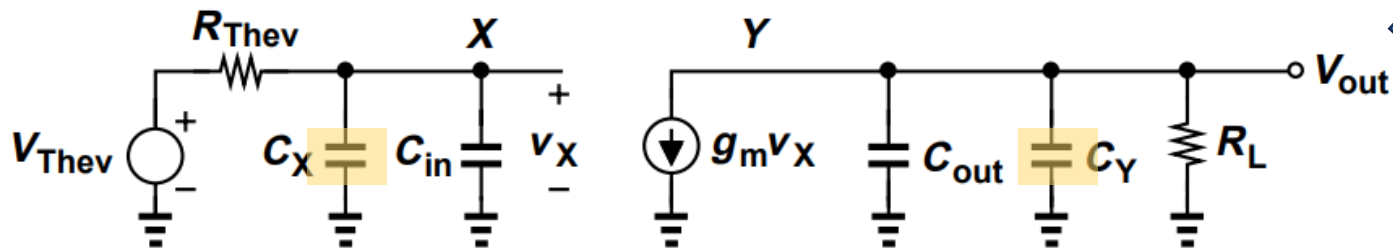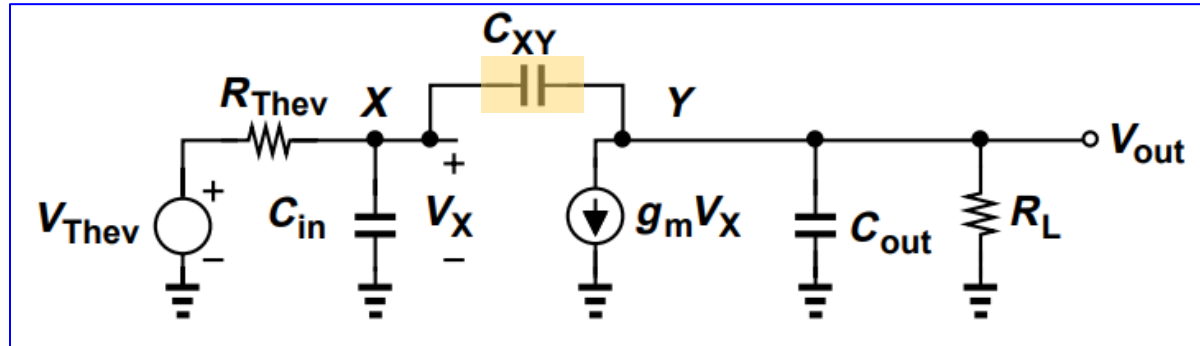

CE Stage

$$V_{\text{Thev}} = V_{\text{in}} \frac{r_{\pi}}{r_{\pi} + R_S}$$

$$R_{\text{Thev}} = R_S \parallel r_{\pi}$$

$$C_X = C_{\mu} (1 + g_m R_L)$$

$$C_Y = C_{\mu} \left(1 + \frac{1}{g_m R_L}\right)$$

CS Stage

$$V_{\text{Thev}} = V_{\text{in}}$$

$$R_{\text{Thev}} = R_S$$


$$C_X = C_{\text{GD}} (1 + g_m R_L)$$

$$C_Y = C_{\text{GD}} \left(1 + \frac{1}{g_m R_L}\right)$$


Apply Miller's theorem to C_{XY}

$$|\omega_{p,\text{in}}| = \frac{1}{R_{\text{Thev}} [C_{\text{in}} + C_{XY} (1 + g_m R_L)]}$$

$$|\omega_{p,\text{out}}| = \frac{1}{R_L [C_{\text{out}} + C_{XY} (1 + \frac{1}{g_m R_L})]}$$

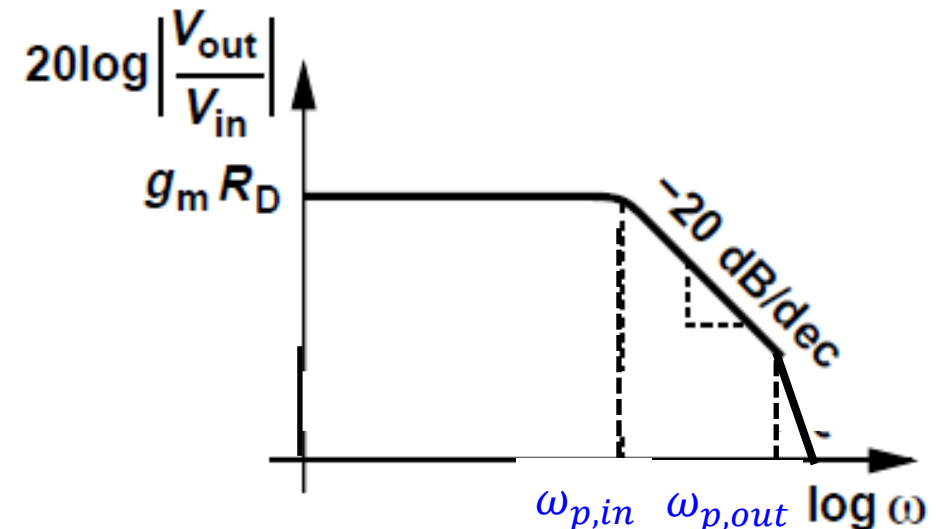

Ltspice simulation example

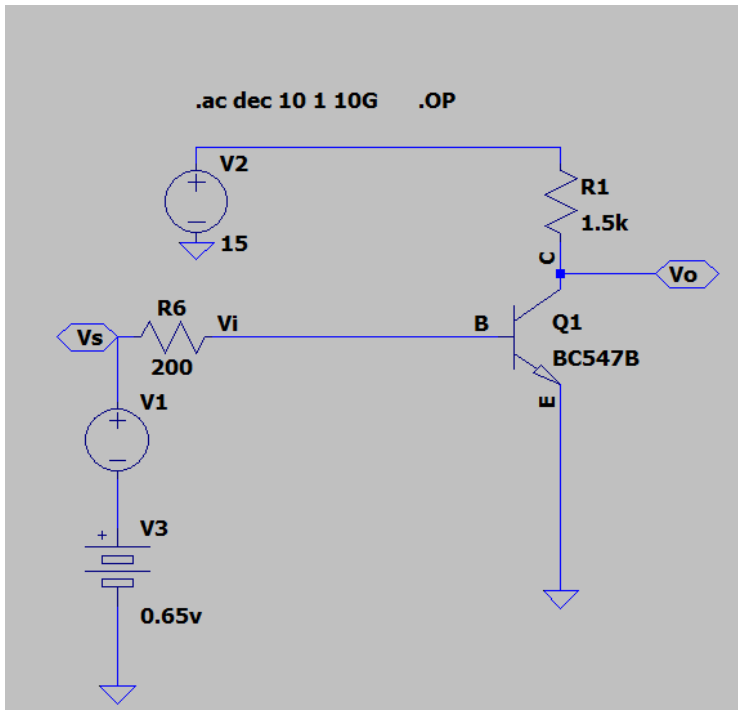

Name: q1
Model: bc547b
Ib: 5.13e-06
Ic: 1.72e-03
Vbe: 6.49e-01
Vbc: -1.18e+01
Vce: 1.24e+01
BetaDC: 3.35e+02
Gm: 6.52e-02
Rpi: 5.10e+03
Rx: 1.00e+00
Ro: 4.27e+04
Cbe: 7.87e-11
Cbc: 8.41e-13
Cjs: 0.00e+00
BetaAC: 3.32e+02
Cbx: 5.17e-13
Ft: 1.29e+08


$$|\omega_{p,in}| = \frac{1}{R_{Thev}[C_{in} + C_{XY}(1 + g_m R_L)]}$$

$$f_{p,in} = 5.1\text{e}6 \text{ Hz}$$

$$|\omega_{p,out}| = \frac{1}{R_L[C_{out} + C_{XY}(1 + \frac{1}{g_m R_L})]}$$

$$f_{p,out} = 1.2\text{e}8 \text{ Hz}$$

Approach II: exact analysis

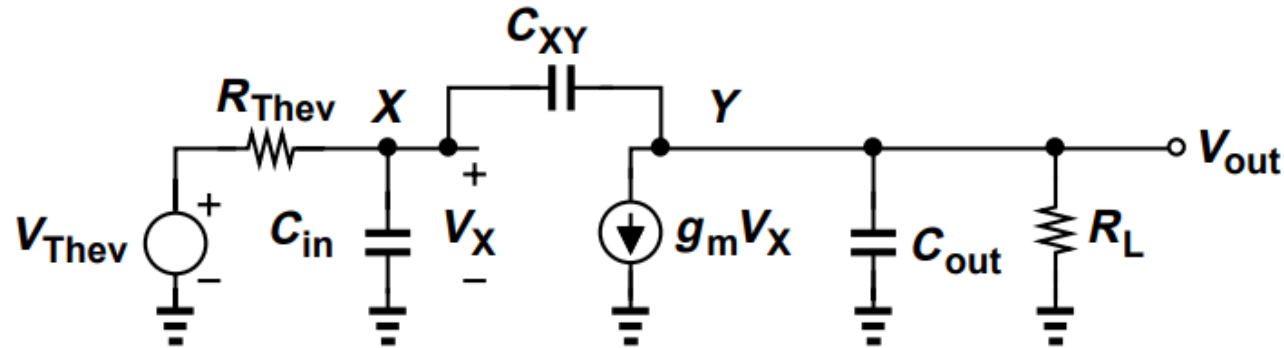


$$\frac{V_{out}}{V_{Thev}}(s)$$

$$= \frac{(C_{XY}s - g_m)R_L}{R_{Thev}R_L[C_{in}C_{XY} + C_{out}C_{XY} + C_{in}C_{out}]s^2 + [R_{Thev}C_{XY}(1 + g_mR_L) + R_{Thev}C_{in} + R_L(C_{XY} + C_{out})]s + 1}$$

- If $s = 0$, $\frac{V_{out}}{V_{Thev}}(s) = -g_mR_L$
- If $s = \infty$, $\frac{V_{out}}{V_{Thev}}(s) = 0$, C_{in} and C_{out} as short circuits $\rightarrow V_{out} = V_{Thev} = 0$
- One zero: $\omega_z = \frac{g_m}{C_{XY}}$, e.g., $g_m \sim 0.01$, $C_{XY} \sim 10^{-12} \rightarrow \omega_z \sim 100$ GHz, very high frequency, so typically not important
- Two poles: dominant pole approximation, i.e., $\omega_{p1} \ll \omega_{p2}$


$$\rightarrow \omega_{p1} = \frac{1}{[R_{Thev}C_{XY}(1+g_mR_L)+R_{Thev}C_{in}+R_L(C_{XY}+C_{out})]}$$

Low-frequency response

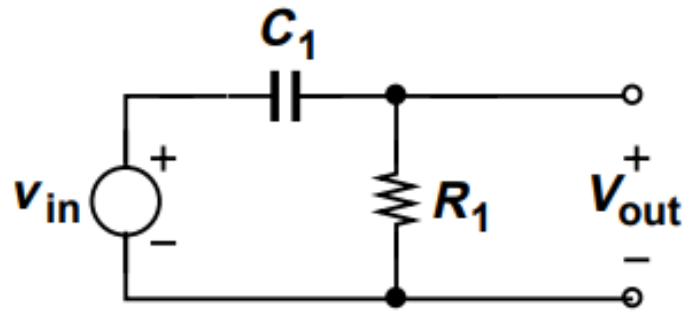

$$\begin{aligned}\frac{V_{out}}{V_{in}}(s) &= \frac{R_1}{R_1 + \frac{1}{C_1 s}} \\ &= \frac{R_1 C_1 s}{R_1 C_1 s + 1},\end{aligned}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{R_1 C_1 \omega}{\sqrt{R_1^2 C_1^2 \omega^2 + 1}}.$$

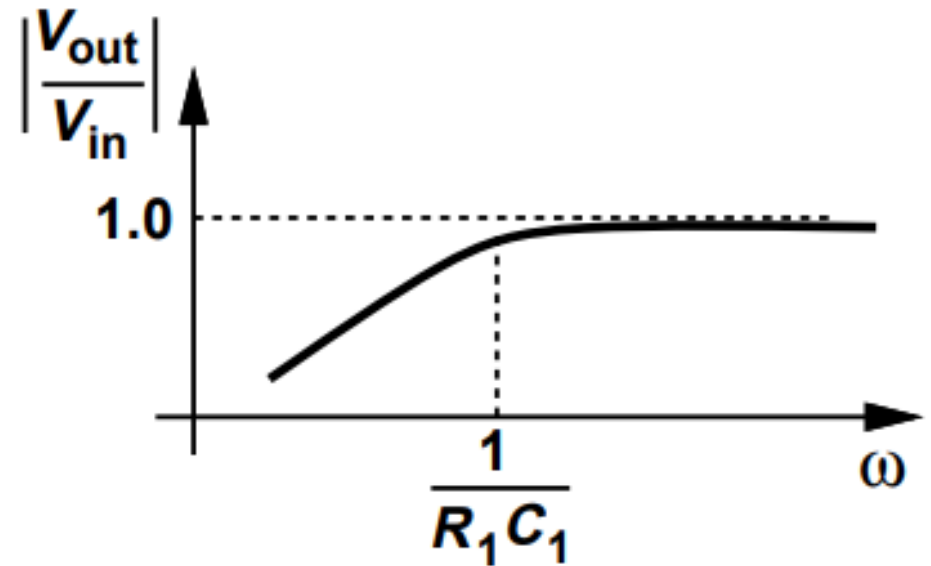

Low-frequency response-BJT

$$\frac{V_o}{V_{sig}} = A_M \frac{s}{s+\omega_{p1}} \frac{s+\omega_z}{s+\omega_{pE}} \frac{s}{s+\omega_{p2}}$$

$$\omega_{p1} = \frac{1}{\tau_{c1}} = \frac{1}{C_{C1}(R_B || r_{\pi} + R_{sig})}$$

$$\omega_{pE} = \frac{1}{\tau_{cE}} = \frac{1}{C_E [R_E || (\frac{1}{g_m} + \frac{R_B || R_{sig}}{\beta + 1})]} \quad \text{Dominant pole}$$




$$\omega_{p2} = \frac{1}{\tau_{c2}} = \frac{1}{C_{C2}(R_D + R_L)}$$

$$\omega_z = \frac{1}{C_E R_E}$$


$$R_B = R_{B1} || R_{B2} \quad r_{\pi} = \frac{\beta}{g_m} = \beta r_e$$

Short-circuit time constant method:

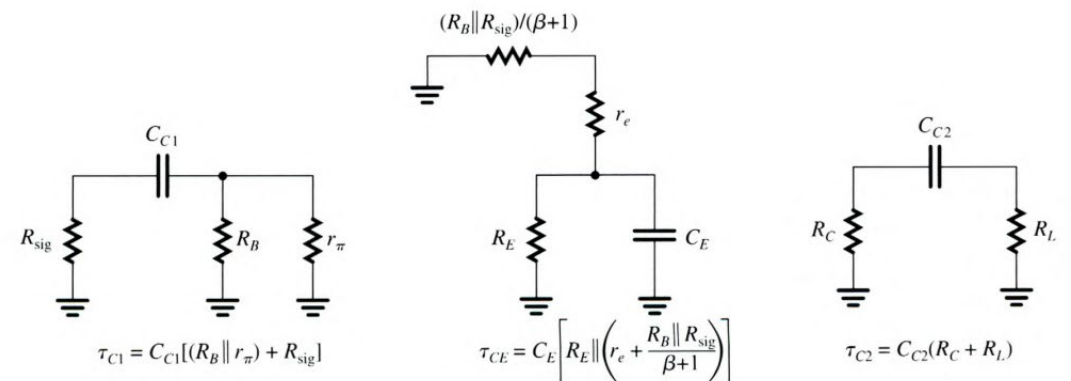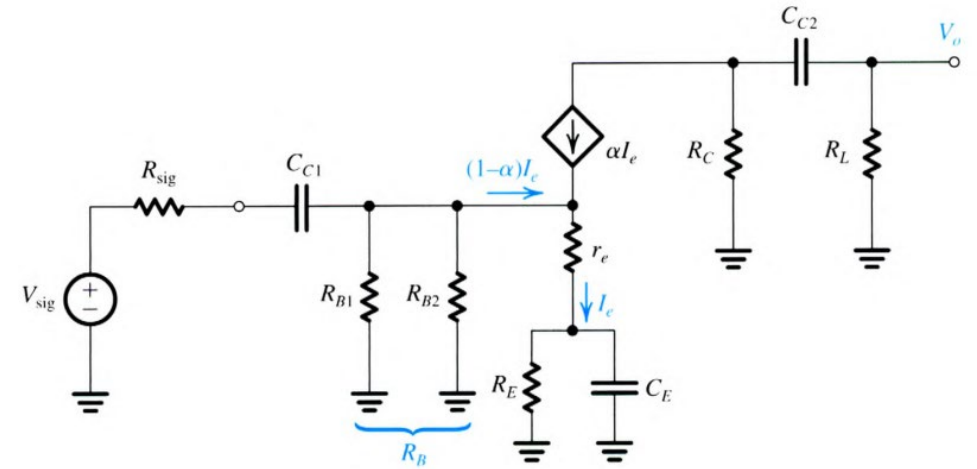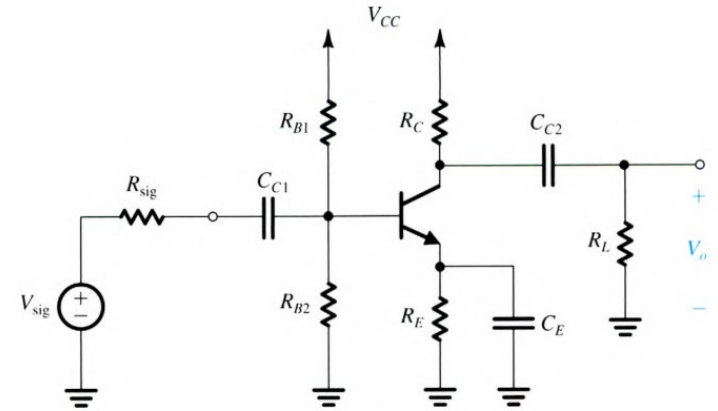- Short other capacitors
- turn off sources:
 - Voltage source \rightarrow short circuit
 - Current source \rightarrow open circuit



Low-frequency response--MOSFET

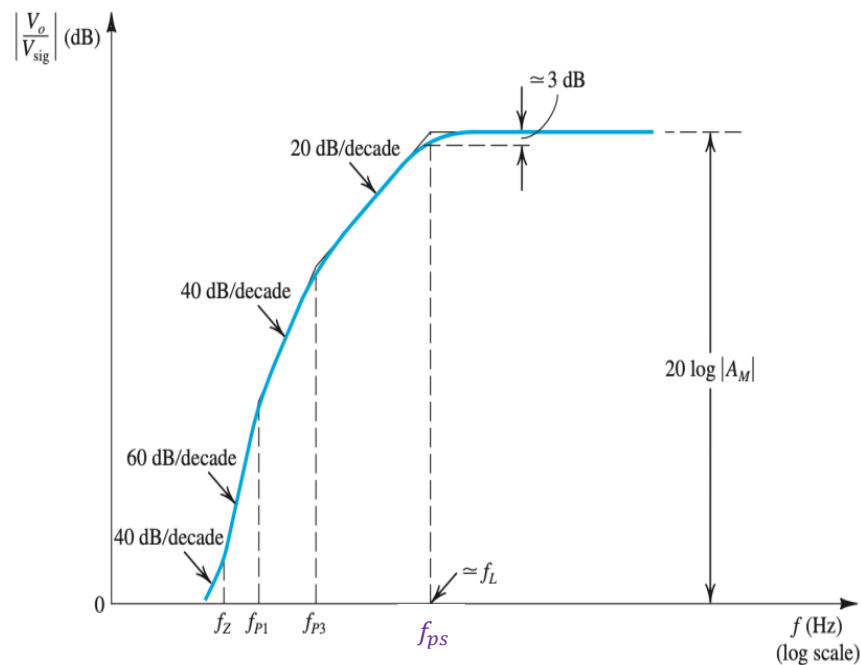

Dominant pole

$$\frac{V_o}{V_{sig}} = A_M \frac{s}{s + \omega_{p1}} \frac{s + \omega_z}{s + \omega_{ps}} \frac{s}{s + \omega_{p2}}$$




$$\omega_{p1} = \frac{1}{\tau_{c1}} = \frac{1}{C_{C1}(R_G + R_{sig})}$$

$$\omega_{ps} = \frac{1}{\tau_{cs}} = \frac{1}{C_S(R_S \parallel \frac{1}{g_m})}$$

$$\omega_{p2} = \frac{1}{\tau_{c2}} = \frac{1}{C_{C2}(R_D + R_L)}$$

$$\omega_z = \frac{1}{C_S R_S}$$

$$R_G = R_{G1} \parallel R_{G2}$$

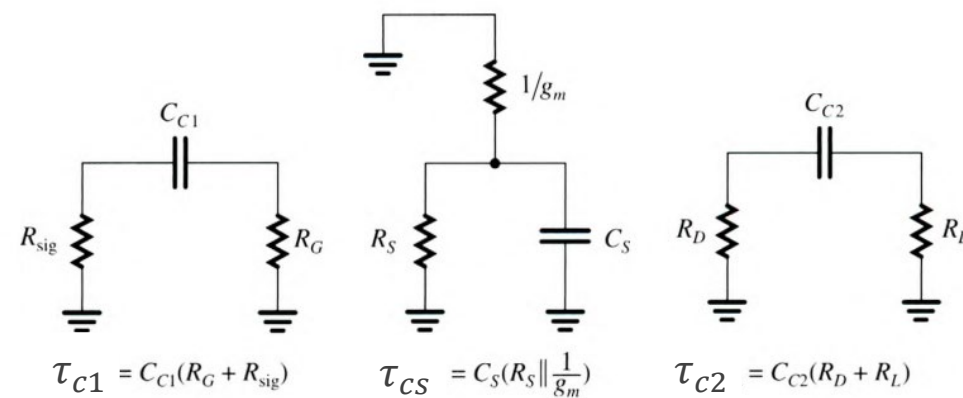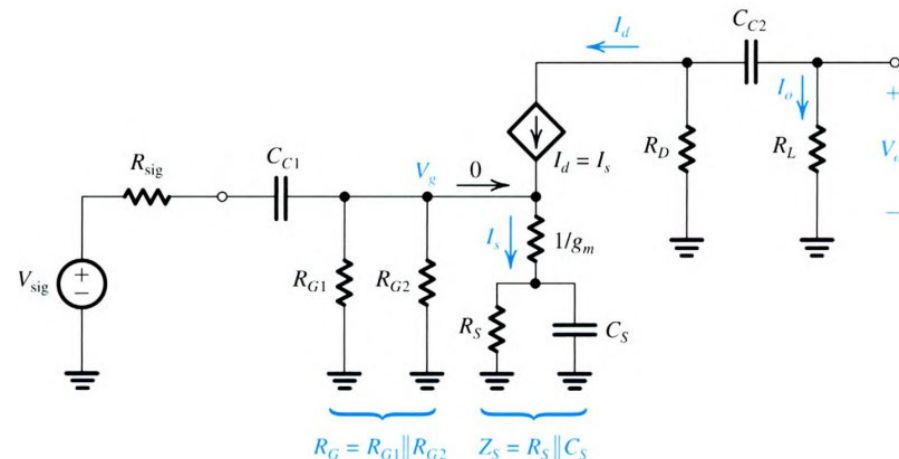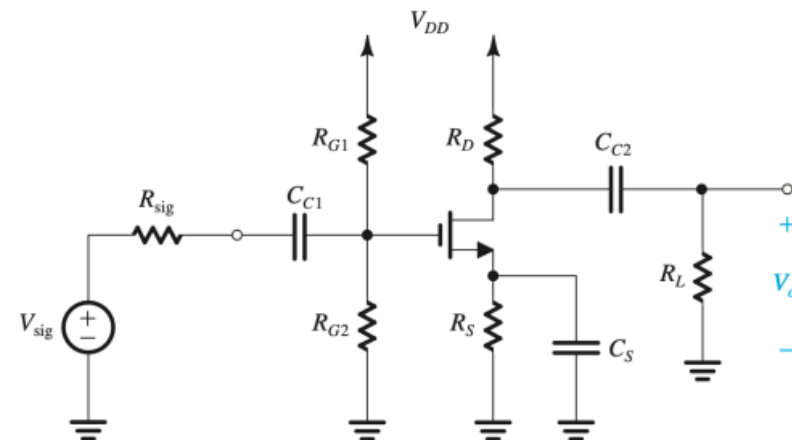


Low frequency design

- Design the C_{C1} , C_{CE} and C_{C2} to achieve a given f_L

$$f_{C1} = f_{C2} = 0.1f_L$$
$$f_{CE} = 0.8f_L$$







- $\omega_{p1} = 2\pi f_{C1} = \frac{1}{C_{C1}(R_B || r_\pi + R_{sig})}$
- $\omega_{pE} = 2\pi f_{CE} = \frac{1}{C_E[R_E || (\frac{1}{g_m} + \frac{R_B || R_{sig}}{\beta + 1})]}$
- $\omega_{p2} = 2\pi f_{C2} = \frac{1}{C_{C2}(R_D + R_L)}$

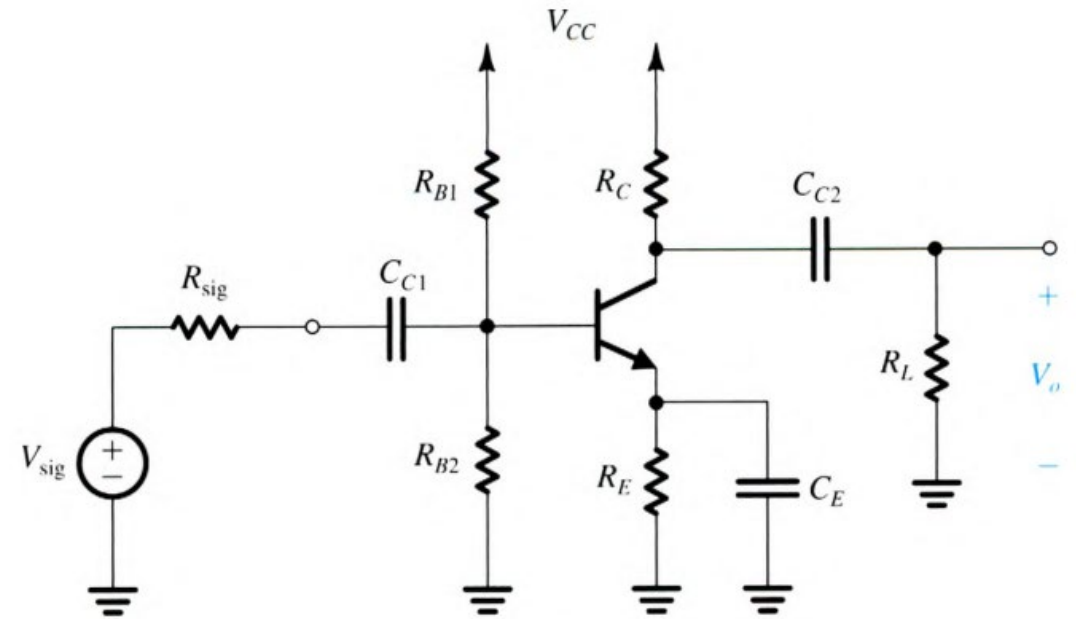

Agenda

- Recap MOSFET and Frequency response
- Computation of frequency response
- Nonlinear system
 - General nonlinear system and harmonic distortion
 - Nonlinear system example—BJT
 - Nonlinear system example--MOSFET


Linear system

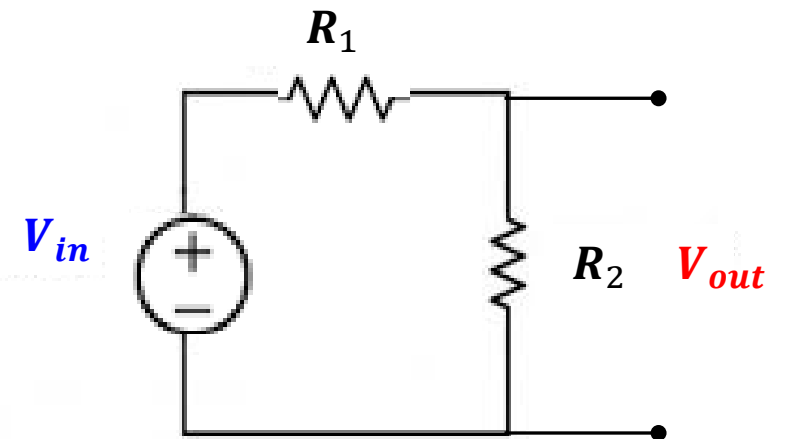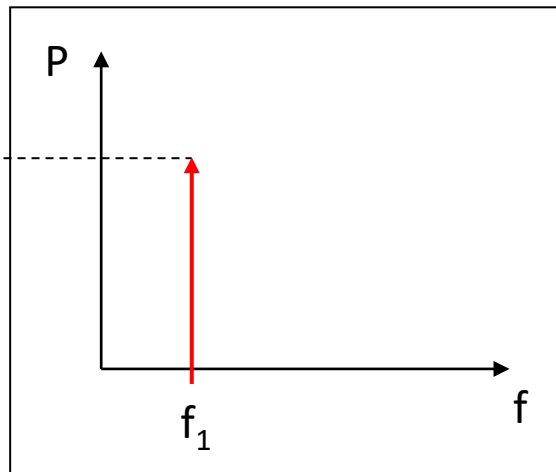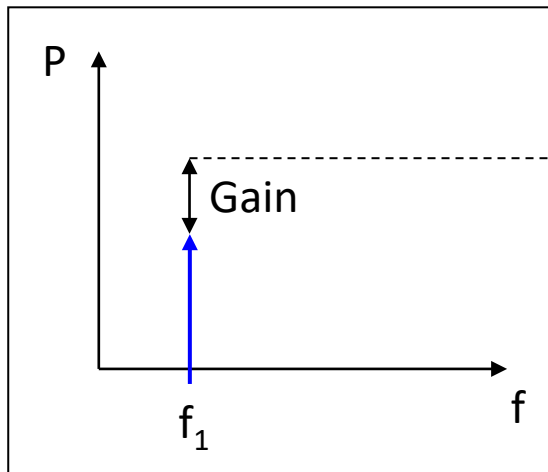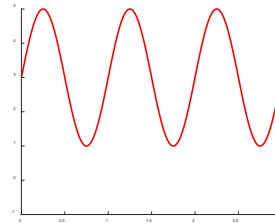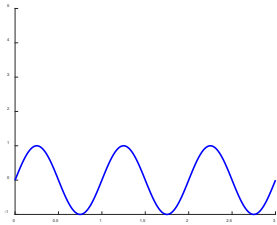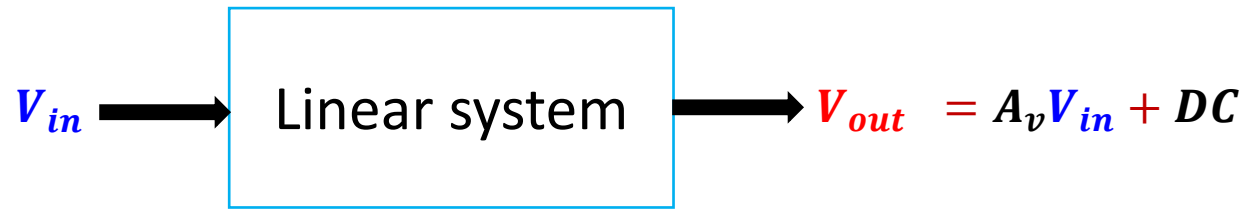


$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$

Nonlinear system

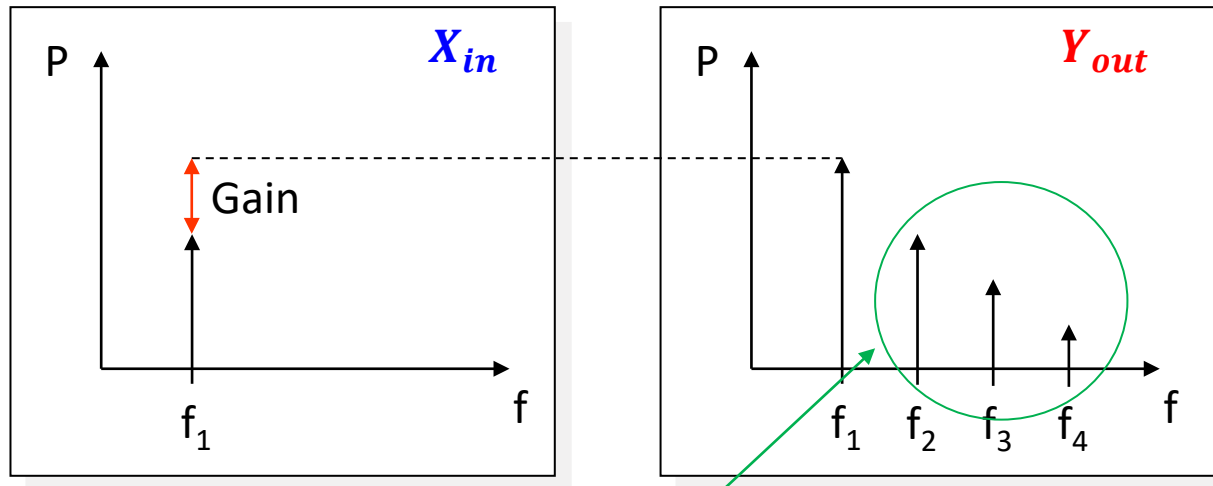- $Y_{out} = f(X_{in})$: nonlinear function
 - X and Y could be V or I
 - $Y_{out} = \alpha_1 X_{in} + \alpha_2 X_{in}^2$, $Y_{out} = e^{\frac{X_{in}}{a}}$...
 - Capacitors, diodes, transistor



Undesirable frequency components

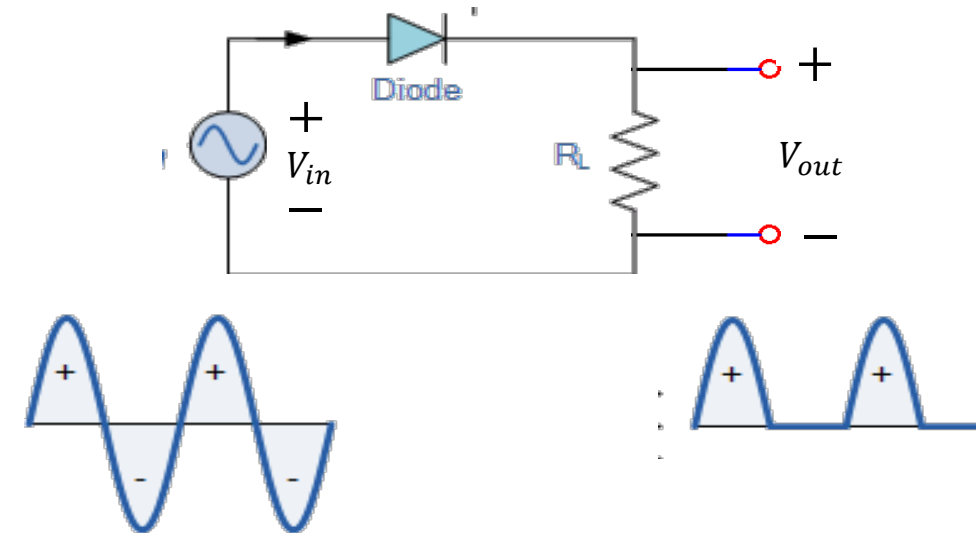

General nonlinear system

$$Y_{out} = f(X_{in}) = f(a) + f'(a)(X_{in} - a) + \frac{f''(a)}{2!}(X_{in} - a)^2 + \dots$$

$$X_{in} = X_{in,Q} + x_{in}$$

In small-signal model, assume x_{in} is a sin wave centered at $a = 0$

$$\begin{aligned} Y_{out} &= f(0) + f'(0)x_{in} + \frac{f''(0)}{2!}x_{in}^2 + \frac{f'''(0)}{3!}x_{in}^3 + \dots \\ &= \alpha_0 + \alpha_1 x_{in} + \alpha_2 x_{in}^2 + \alpha_3 x_{in}^3 + \dots \end{aligned}$$

General nonlinear system

$$Y_{out} = \alpha_0 + \alpha_1 x_{in} + \alpha_2 x_{in}^2 + \alpha_3 x_{in}^3 + \dots$$

- $x_{in} = A \cos(\omega t)$
- $x_{in}^2 = A^2 \cos^2(\omega t) = A^2 \frac{1 + \cos(2\omega t)}{2}$
- $x_{in}^3 = A^3 \cos^3(\omega t) = A^3 \frac{3\cos(\omega t) + \cos(3\omega t)}{4}$

DC:

$$\beta_0 = \alpha_0 + \alpha_2 \frac{A^2}{2}$$

2nd Harmonic:

$$\beta_2 = \alpha_2 \frac{A^2}{2}$$

Fundamental:

$$\beta_1 = \alpha_1 A + \alpha_3 \frac{3A^3}{4} \approx \alpha_1 A$$

3rd Harmonic:

$$\beta_3 = \alpha_3 \frac{A^3}{4}$$

Total harmonic distortion (THD):

$$THD = \sqrt{HD_2^2 + HD_3^2 + HD_4^2 + \dots}$$

Harmonic distortion (HD):


2nd Harmonic:

$$HD_2 = \frac{\beta_2}{\beta_1} \approx \frac{\alpha_2}{2\alpha_1} A$$

3rd Harmonic:

$$HD_3 = \frac{\beta_3}{\beta_1} \approx \frac{\alpha_3}{4\alpha_1} A^2$$

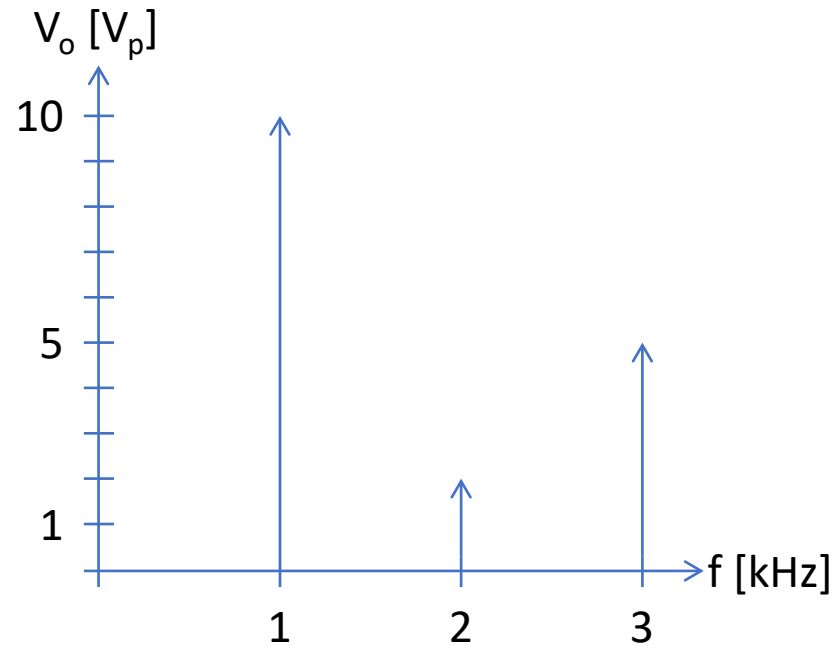Example for harmonic distortion calculation




$$HD_2 = \frac{\beta_2}{\beta_1} = \frac{2}{10} = 0.2 \rightarrow 20\%$$

$$HD_3 = \frac{\beta_3}{\beta_1} = \frac{5}{10} = 0.5 \rightarrow 50\%$$

$$THD = \sqrt{HD_2^2 + HD_3^2} = \sqrt{0.2^2 + 0.5^2} = 0.54 \rightarrow 54\%$$

Nonlinear system example--BJT

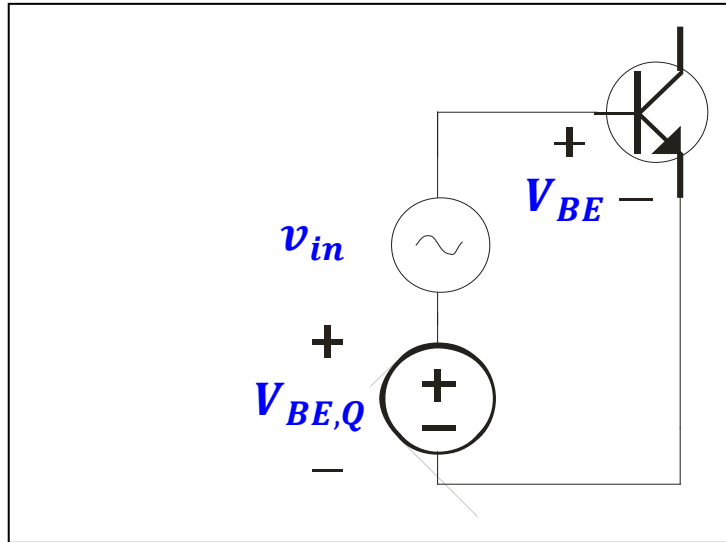

Taylor series expansion:

$$e^{x/a} = 1 + \frac{1}{a}x + \frac{1}{2! \cdot a^2}x^2 + \dots + \frac{1}{n! \cdot a^n}x^n + \dots$$

$$\begin{aligned} I_C &= I_S e^{V_{BE}/V_T} = I_S e^{(V_{BE,Q} + v_{in})/V_T} = I_S e^{V_{BE,Q}/V_T} e^{v_{in}/V_T} = I_{CQ} e^{v_{in}/V_T} \\ &= I_{CQ} \left(1 + \frac{1}{V_T} v_{in} + \frac{1}{2! \cdot V_T^2} v_{in}^2 + \frac{1}{3! \cdot V_T^3} v_{in}^3 + \dots \right) \\ &= I_{CQ} + \frac{I_{CQ}}{V_T} v_{in} + \frac{I_{CQ}}{2! \cdot V_T^2} v_{in}^2 + \frac{I_{CQ}}{3! \cdot V_T^3} v_{in}^3 + \dots \\ &= \alpha_0 + \alpha_1 v_{in} + \alpha_2 v_{in}^2 + \alpha_3 v_{in}^3 + \dots \end{aligned}$$

DC:

$$\beta_0 = \alpha_0 + \alpha_2 \frac{A^2}{2}$$

2nd Harmonic:

$$\beta_2 = \alpha_2 \frac{A^2}{2}$$

Total harmonic distortion (THD):

$$\begin{aligned} THD &= \sqrt{HD_2^2 + HD_3^2 + HD_4^2 + \dots} \\ &= \sqrt{\left(\frac{\beta_2}{\beta_1}\right)^2 + \left(\frac{\beta_3}{\beta_1}\right)^2 + \left(\frac{\beta_4}{\beta_1}\right)^2 + \dots} \end{aligned}$$


Fundamental:

$$\beta_1 = \alpha_1 A + \alpha_3 \frac{3A^3}{4} \approx \alpha_1 A$$

3rd Harmonic:

$$\beta_3 = \alpha_3 \frac{A^3}{4}$$

Nonlinear system example--MOSFET

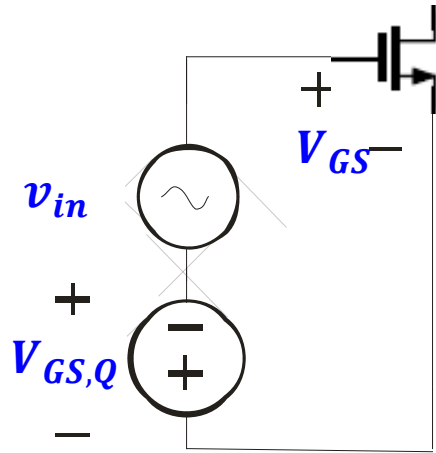

$$\begin{aligned}
 I_D &= \frac{1}{2} k_n (V_{GS} - V_{TH})^2 = \frac{1}{2} k_n (V_{GS,Q} - V_{TH} + v_{in})^2 \\
 &= \frac{1}{2} k_n (V_{GS,Q} - V_{TH})^2 \left(1 + \frac{v_{in}}{V_{GS,Q} - V_{TH}} \right)^2 \\
 &= I_{DQ} \left(1 + \frac{2}{V_{GS,Q} - V_{TH}} v_{in} + \frac{1}{(V_{GS,Q} - V_{TH})^2} v_{in}^2 \right) \\
 &= I_{DQ} + \frac{2I_{DQ}}{V_{GS,Q} - V_{TH}} v_{in} + \frac{I_{DQ}}{(V_{GS,Q} - V_{TH})^2} v_{in}^2 \\
 &= \alpha_0 + \alpha_1 v_{in} + \alpha_2 v_{in}^2
 \end{aligned}$$

DC:

$$\beta_0 = \alpha_0 + \alpha_2 \frac{A^2}{2}$$

2nd Harmonic:

$$\beta_2 = \alpha_2 \frac{A^2}{2}$$

Fundamental:

$$\beta_1 = \alpha_1 A$$

3rd Harmonic:

$$\beta_3 = 0$$

Total harmonic distortion (THD):

$$\begin{aligned}
 THD &= \sqrt{HD_2^2 + HD_3^2 + HD_4^2 + \dots} \\
 &= \frac{\beta_2}{\beta_1} = HD_2
 \end{aligned}$$

Sound samples—harmonic distortions

400 Hz



800 Hz



1200 Hz



First 400 Hz then all three tones together



Sound samples—clip




original



Zero-clip



Clip

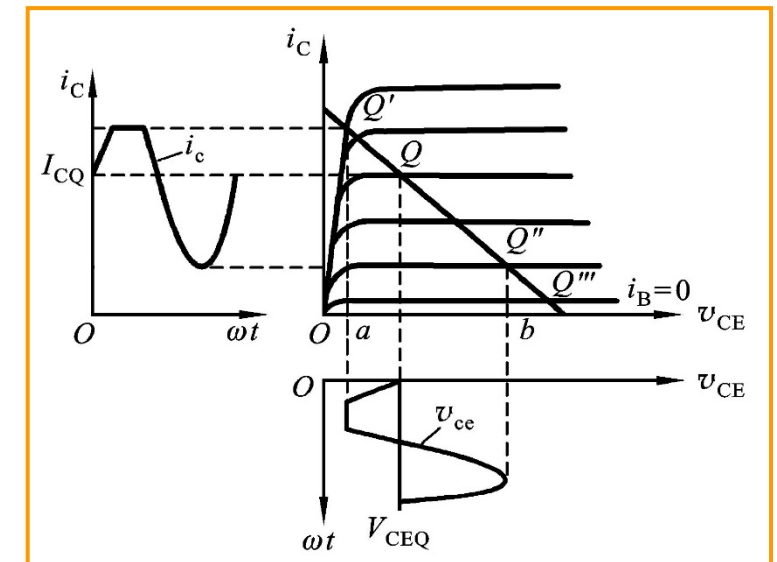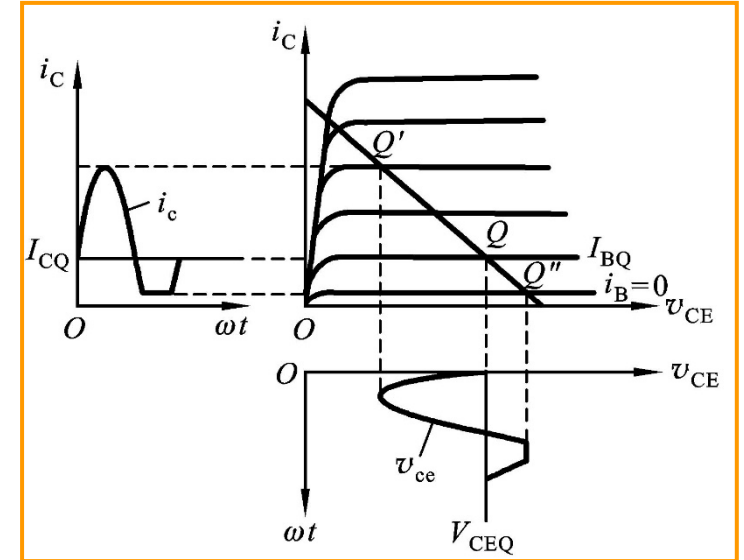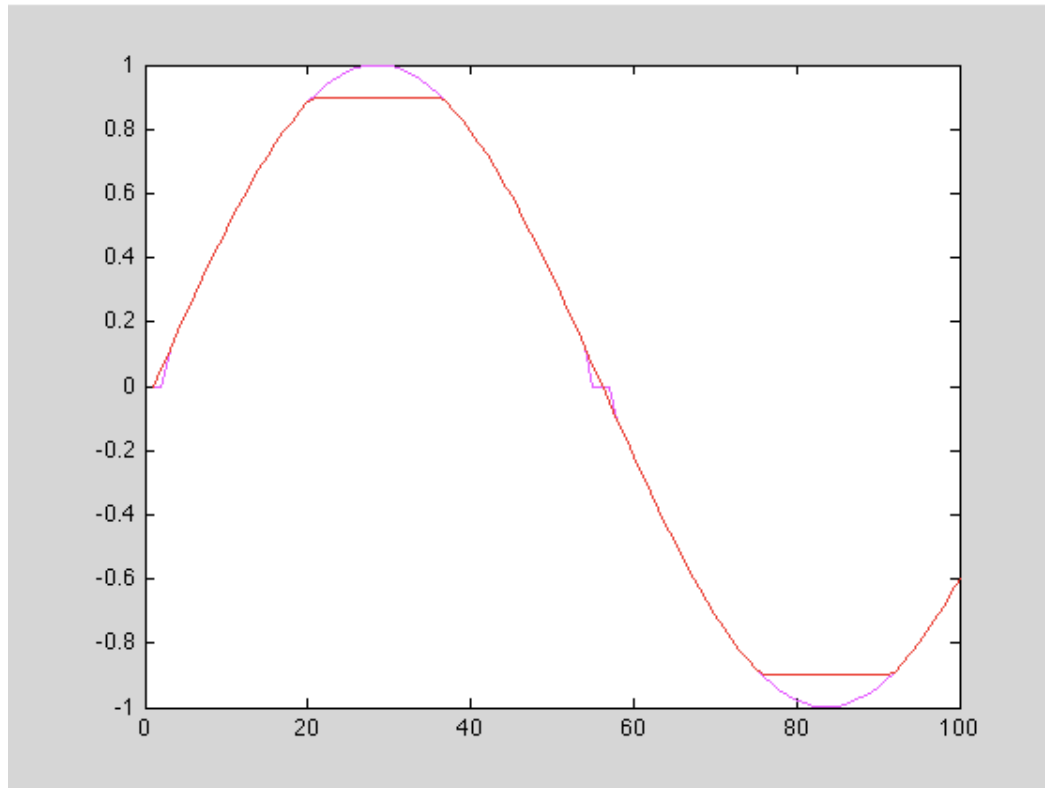

Design consideration

- Properly bias
 - BJT
 - Active forward region $\rightarrow V_{BE} \geq 0.7\text{ V}$ & $V_{CE} \geq V_{BE}$
 - MOSFET
 - Saturation $\rightarrow V_{DS} > V_{GS} - V_{TH}$
- Select suitable Q point (clip distortion)
- Small-signal assumption
 - BJT
 - Small-signal assumption $\rightarrow v_{in} < 0.2 V_T$
 - MOSFET
 - Small-signal assumption $\rightarrow v_{in} < 0.2 (V_{GS,Q} - V_{TH})$

