

# Bipolar Junction Transistors

**Peng Mei**

**Department of Electronic Systems**

**Email: [mei@es.aau.dk](mailto:mei@es.aau.dk)**



**AALBORG UNIVERSITY**  
DENMARK





## Learning objectives:

- Early effect
- Static operating point in power amplifier design



$i_C \sim v_{CE}$  curve:

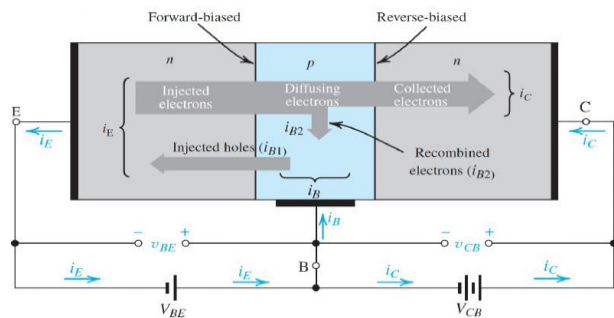
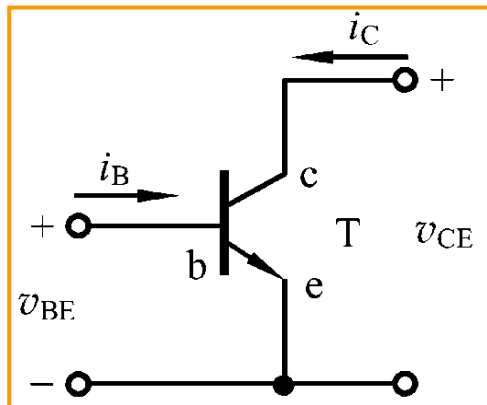


$i_C$ :

Electrons  $E \rightarrow B \rightarrow C$



$i_C \sim v_{CE}$  curve:

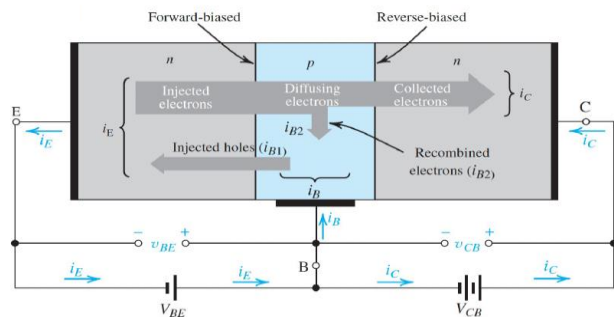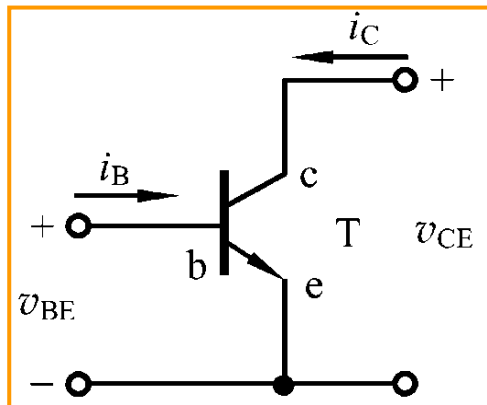

$i_C$ :


Electrons  $E \rightarrow B \rightarrow C$

Saturation

Active

Cutoff

$$i_C = f(u_{CE}) \Big|_{I_B}$$

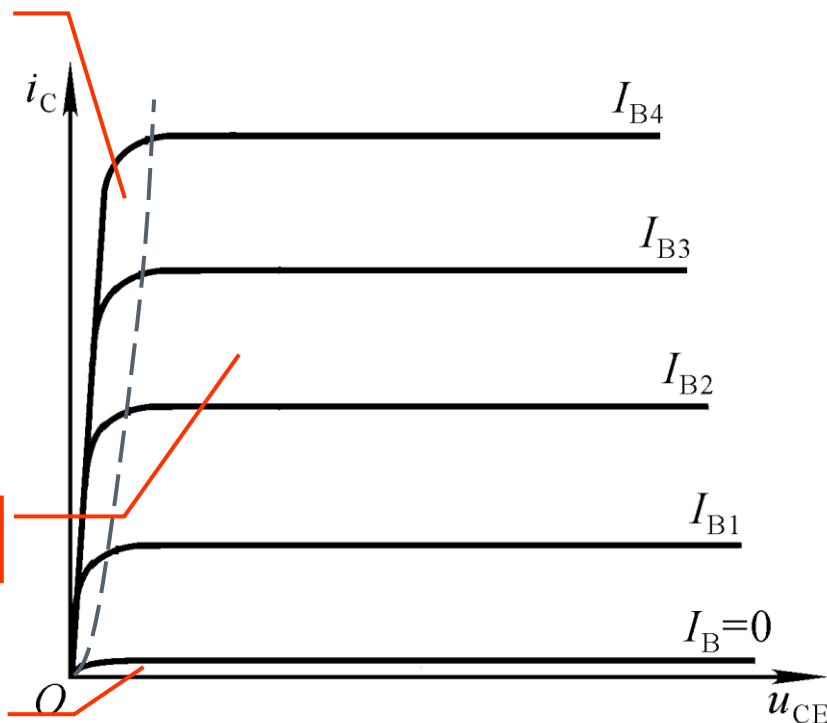

A big  $i_B$  results in a big  $i_C$ .



Mode	EBJ	CBJ
Cutoff	Reverse	Reverse
Active	Forward	Reverse
Saturation	Forward	Forward

Saturation region:  $i_c$  is mainly controlled by  $v_{ce}$ ,  $\beta i_b > i_c$




$$V_{BE} = 0.7V, V_{CE} < 1V$$

Active region:  $i_c$  is basically parallel with  $v_{ce}$ ,  $\beta i_b = i_c$

$$V_{BE} = 0.7V, V_{CE} > 1V$$




Cutoff region:  $i_c$  is approaching to 0,  $i_b \approx i_c \approx 0$

$$V_{BE} < 0.5V$$

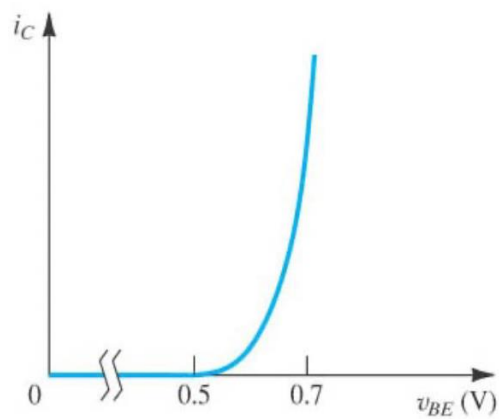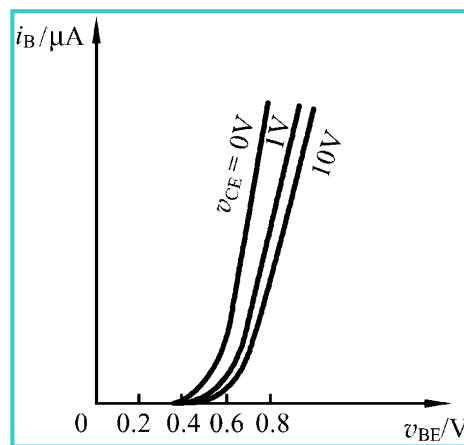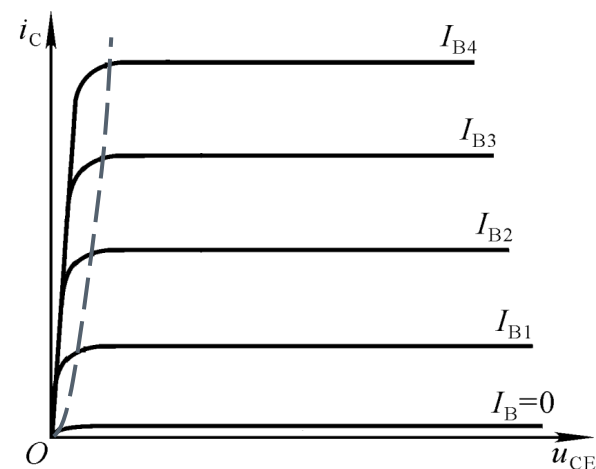 $u_{BE} - i_C$  $u_{BE} - i_B$  $u_{CE} - i_C$




## Effects of temperature:

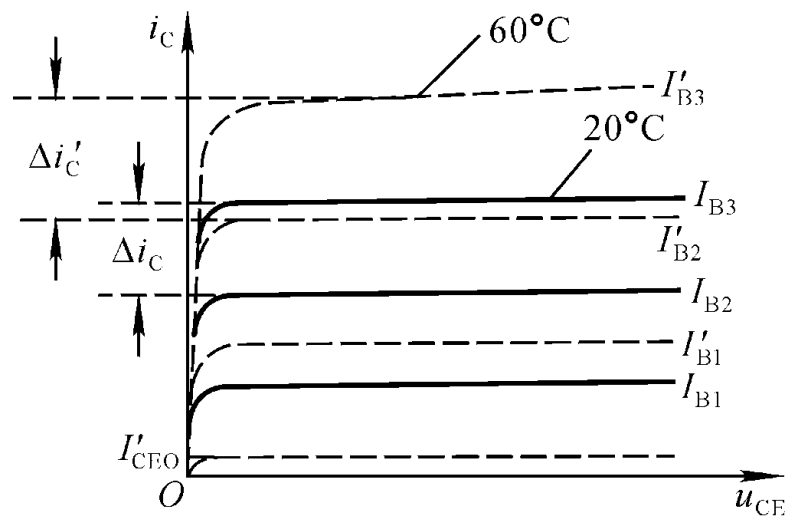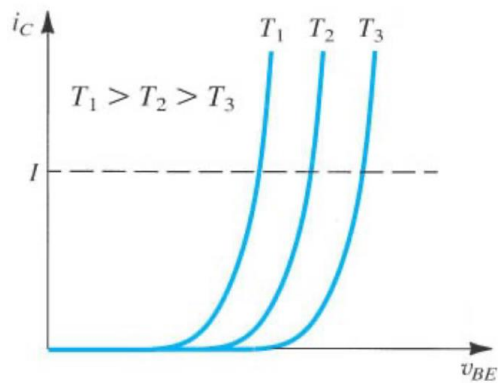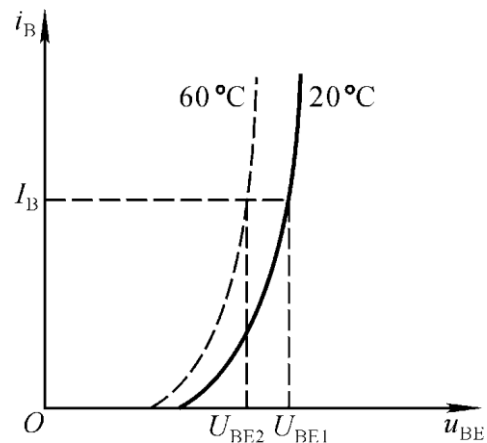



Early effects:

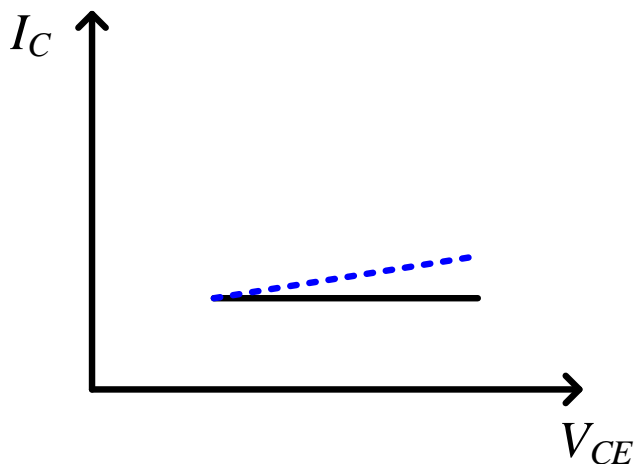

The effects of early voltage on transconductance:

$$g_m = \frac{dI_C}{dV_{BE}} = \frac{I_S}{V_T} e^{\frac{V_{BE}}{V_T}} \left( 1 + \frac{V_{CE}}{V_A} \right) = \frac{I_C}{V_T}$$



Not change

$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \left( 1 + \frac{V_{CE}}{V_A} \right) \quad V_A \text{ is early voltage}$$





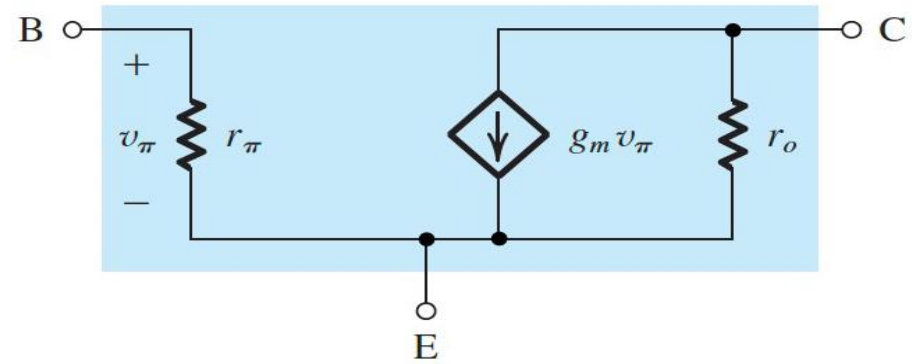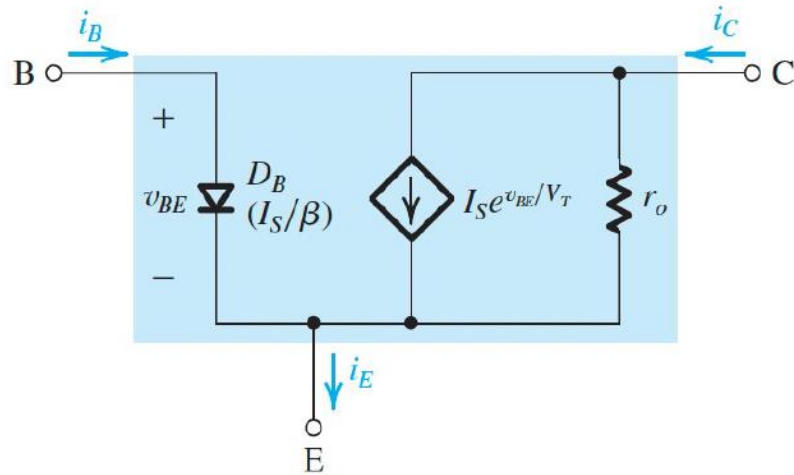
Inclusion of early effect in large-signal and small-signal models:



$$r_o = \frac{V_A}{I_S e^{\frac{v_{BE}}{V_T}}} \approx \frac{V_A}{I_C}$$



Power amplifier:

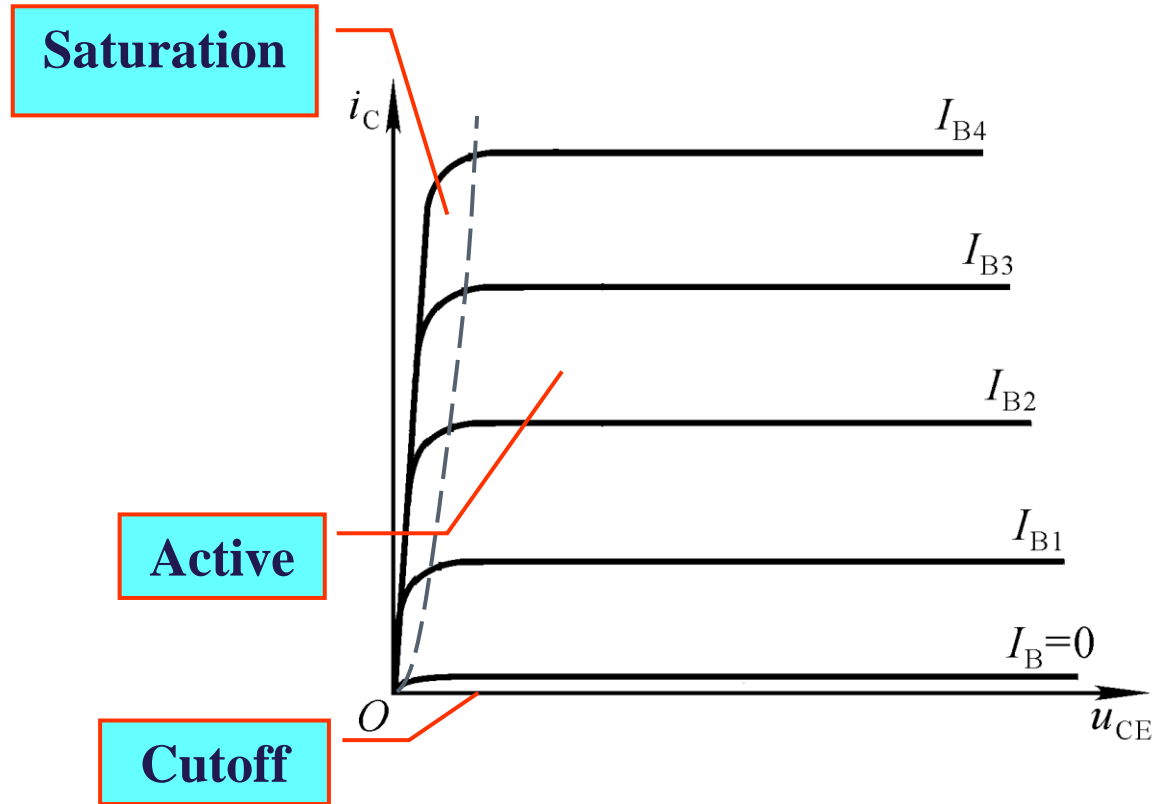







DC biasing (Static operating point (Q point)):

$$I_{BQ} = \frac{V_{BB} - V_{BEQ}}{R_b}$$

$$I_{CQ} \approx \beta \cdot I_{BQ}$$


$$V_{CEQ} = V_{CC} - I_{CQ} R_c$$

$$Q (I_{BQ}, I_{CQ}, V_{CEQ})$$

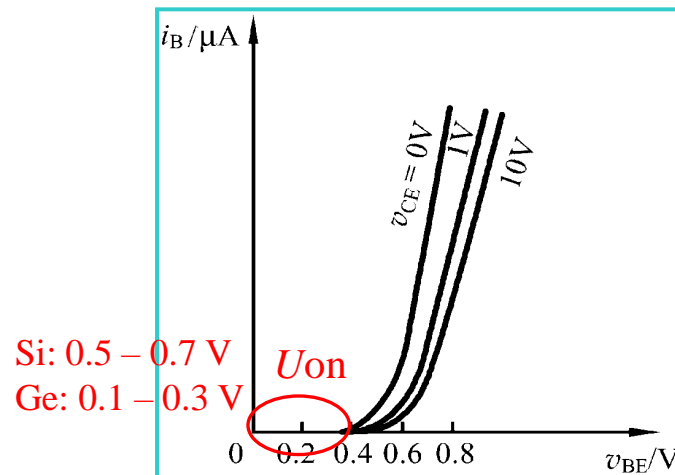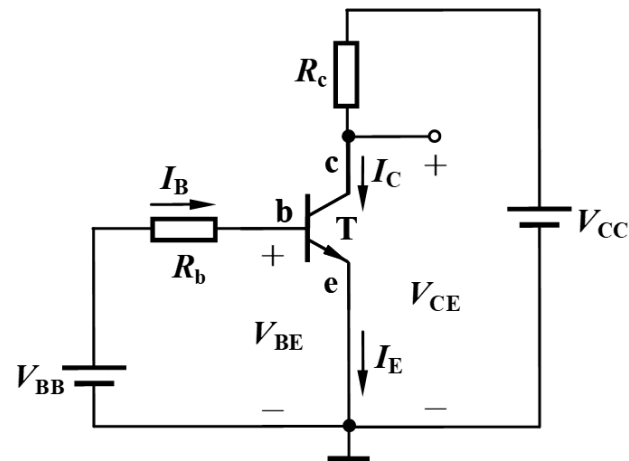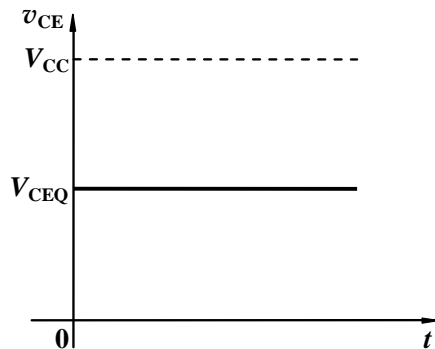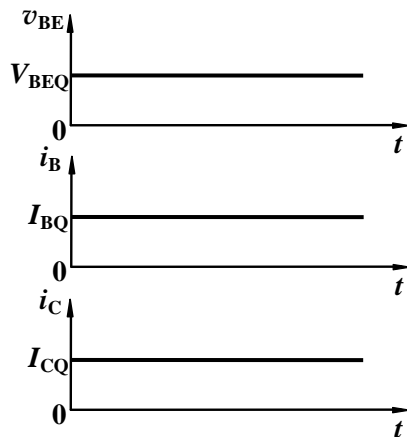



Calculate Q point:

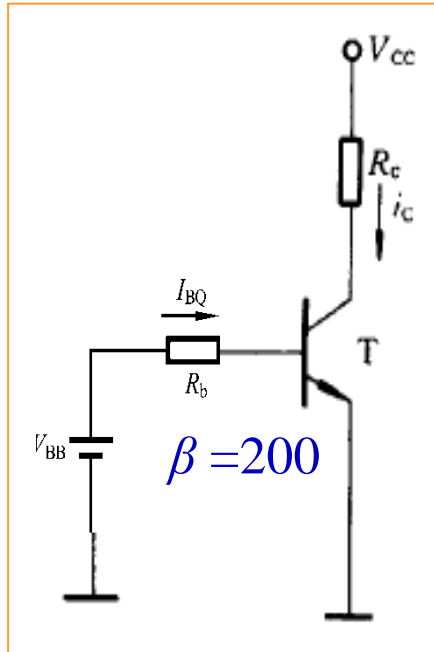

$$V_{CC}=15V, R_C=1.5k\Omega, i_B=20\mu A$$



$$Q(20\mu A, 4\text{ m A}, 9\text{ V})$$

$$V_{CC}=12V, R_C=1k\Omega, V_{BB}=2.2V, R_b=50k\Omega, V_{BEQ}=0.7V$$

$$Q(30\mu A, 6\text{ m A}, 6\text{ V})$$

$$V_{CC}=6V, R_C=200\Omega, V_{BB}=3.2V, R_b=20k\Omega, V_{BEQ}=0.7V$$
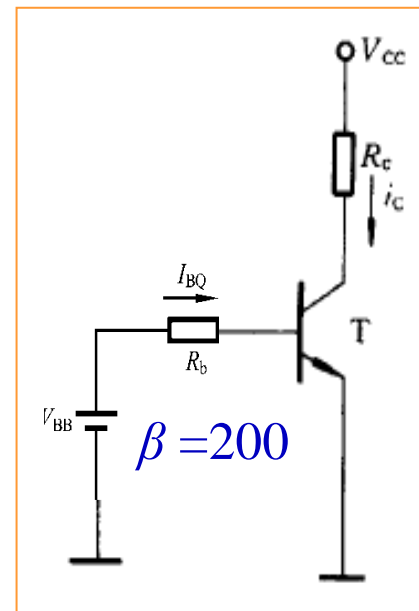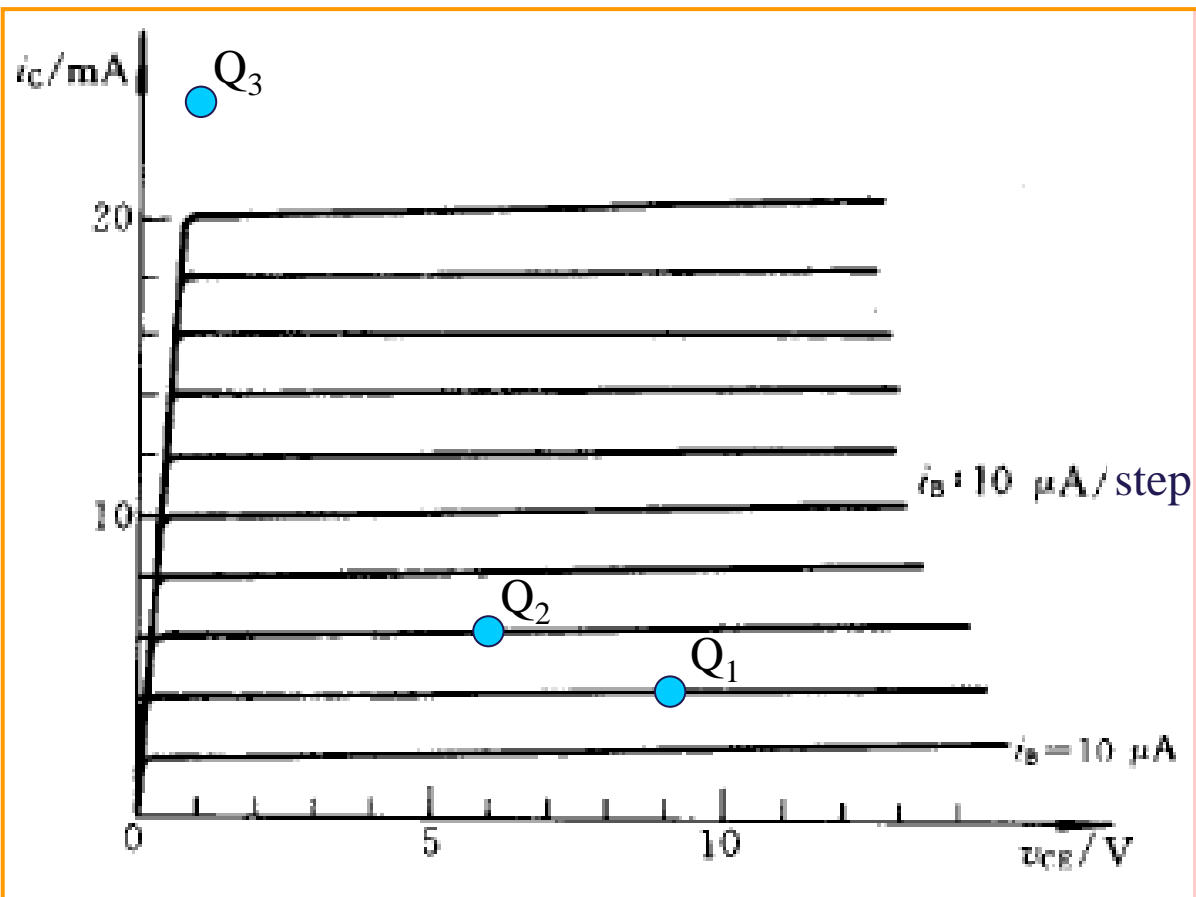
$$Q(125\mu A, 25\text{ m A}, 1\text{ V})$$



$Q_1(20\mu\text{A}, 4\text{ mA}, 9\text{ V})$

$Q_2(30\mu\text{A}, 6\text{ mA}, 6\text{ V})$

$Q_3(125\mu\text{A}, 25\text{ mA}, 1\text{ V})$








With a perturbation (a sinusoidal signal (alternating signal)):

$$i_B = \frac{V_{BB} + v_s - V_{BEQ}}{R_b}$$

$$i_C = \beta \cdot i_B$$



$$v_{CE} = V_{CC} - i_C R_c$$

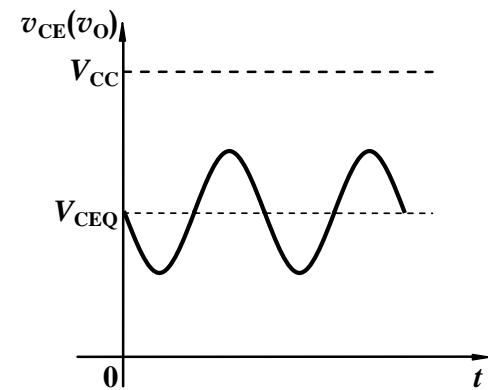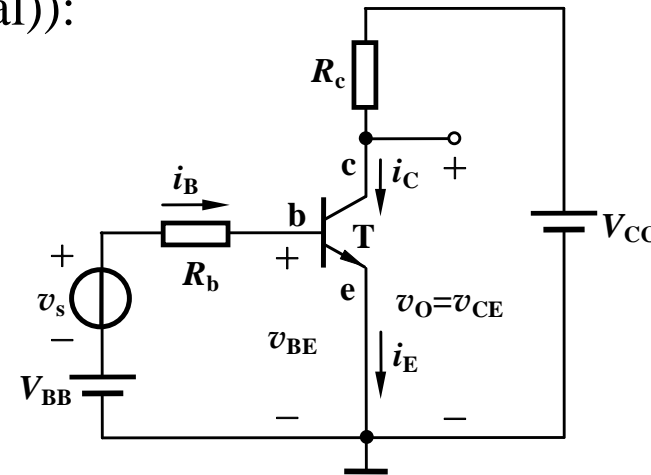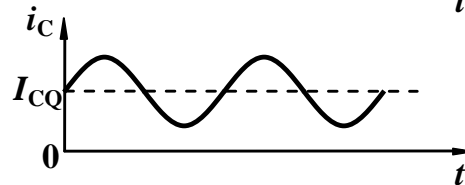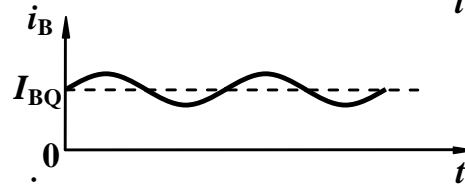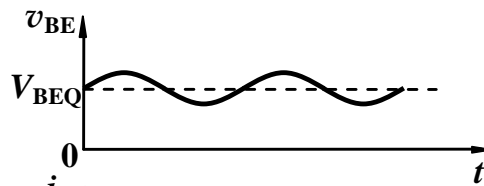


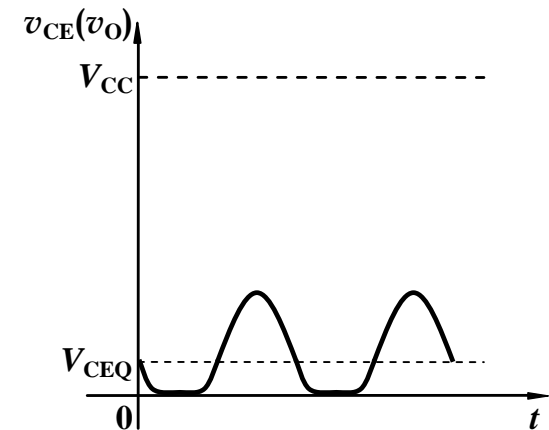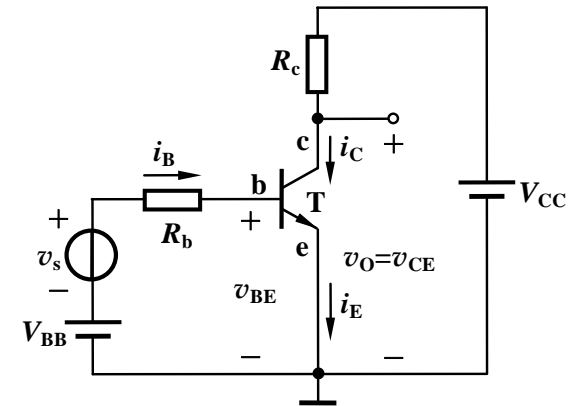
## The effects of static operating point on output voltage

- $I_{BQ} \uparrow \longrightarrow I_{CQ} \uparrow \longrightarrow \text{the voltage on } R_c \uparrow$   
 $\longrightarrow V_{CEQ} \downarrow$
- $R_c \uparrow \longrightarrow \text{the voltage on } R_c \uparrow \longrightarrow V_{CEQ} \downarrow$







## The effects of static operating point on amplification

- $I_{BQ} \downarrow \longrightarrow I_{CQ} \downarrow \longrightarrow \text{the voltage on } R_c \downarrow$   
 $\longrightarrow V_{CEQ} \uparrow$

A proper static operating point should be provided to make the transistor operate at the active mode (amplification region).

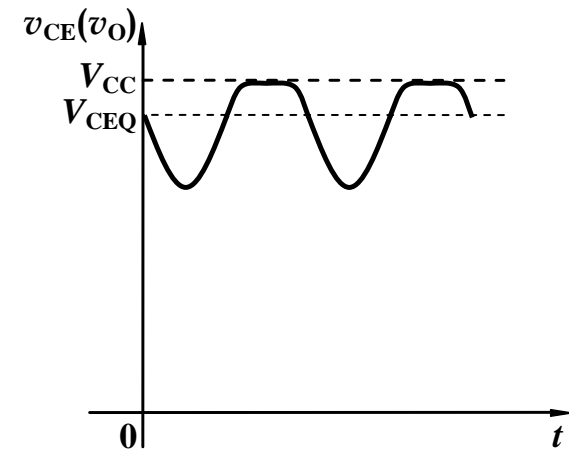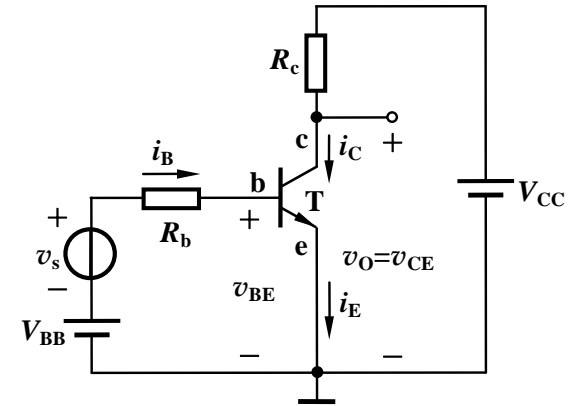
The amplitude of output signal is limited by  $V_{CC}$ .









For DC signal:

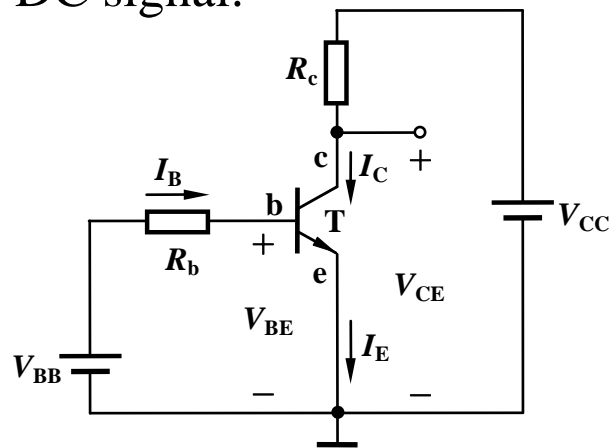

Simplified

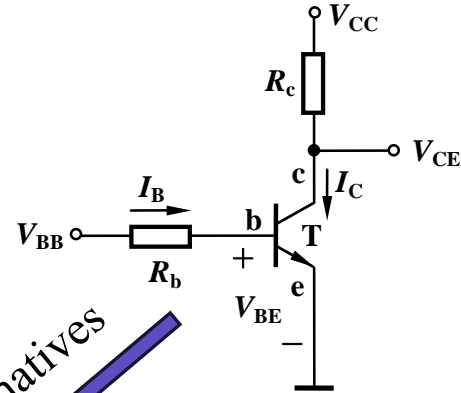

Alternatives

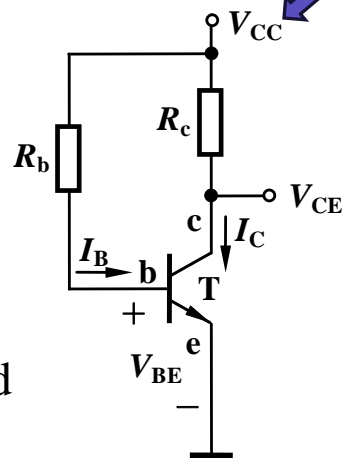

Only one DC  
power is involved

Q point:


$$I_{BQ} = \frac{V_{CC} - V_{BEQ}}{R_b}$$

$$I_{CQ} = \beta \cdot I_{BQ}$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_c$$




When AC signal is added directly:

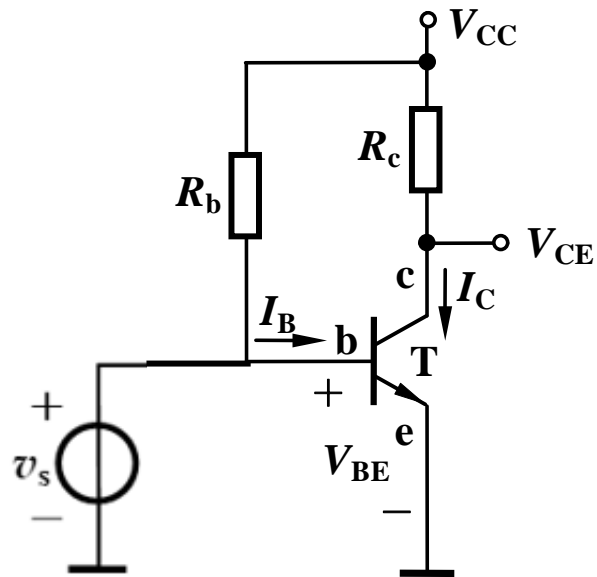

What will happen when  $v_s = 0$ ?



When AC signal is added with capacitors:

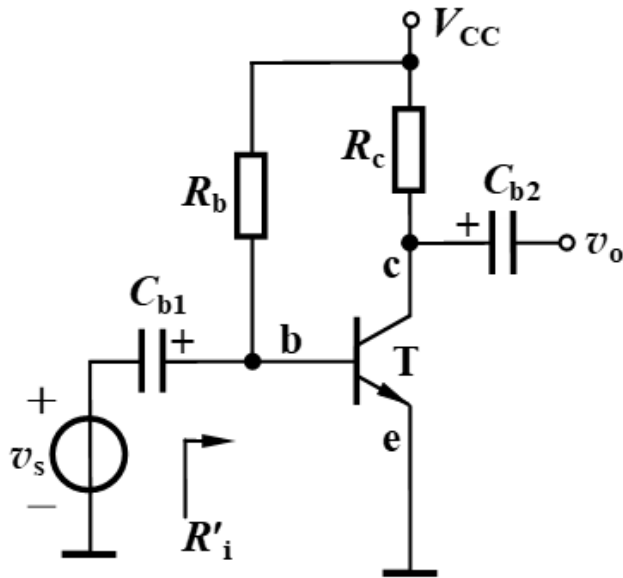



Two capacitors are added at input and output ends to isolate DC and AC signals.

The involvements of  $v_s$  and  $v_o$  do not affect the Q point of the circuit.


The frequency of  $v_s$  can not be too small.



DC circuit and AC circuit:

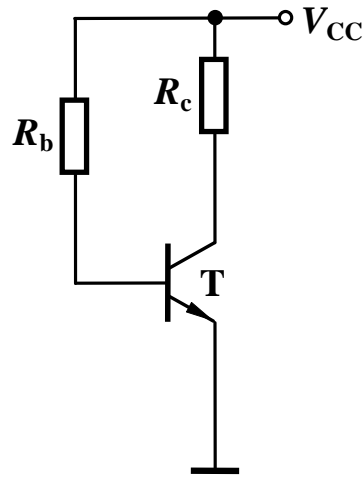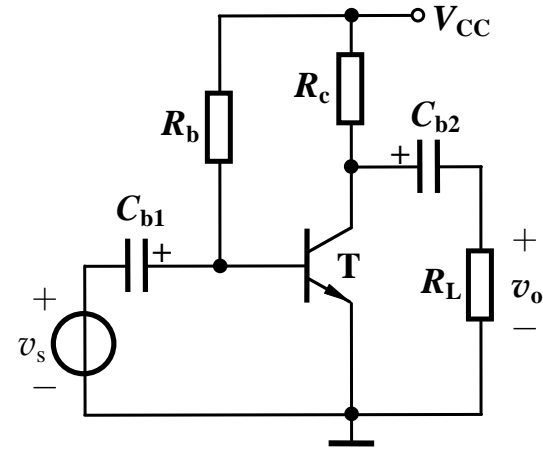


DC circuit

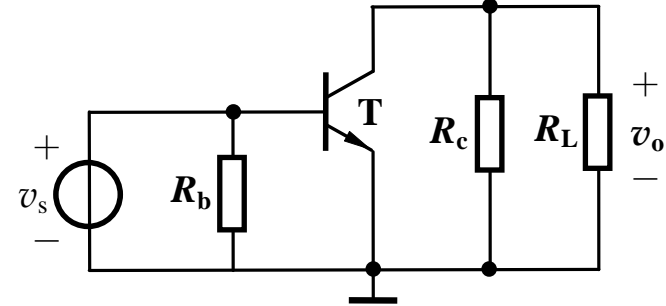

AC circuit

DC circuit: capacitor is open, AC source is open;

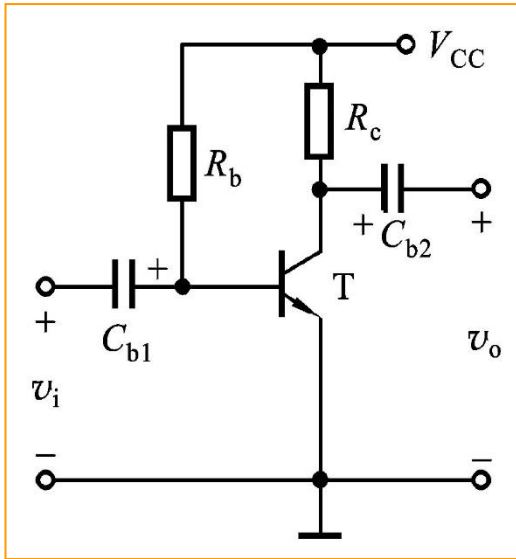AC circuit: capacitor is short, DC source is short;



$$\beta = 80, R_b = 300\text{k}\Omega, R_c = 2\text{k}\Omega, V_{CC} = +12\text{V}$$

$V_{BEQ}$  is assumed to be 0

Calculate Q point, which region does the BJT operate?


Q ( $40\mu\text{A}$ ,  $3.2\text{mA}$ ,  $5.6\text{V}$ )    Active region

If  $R_b = 100\text{k}\Omega$ ,


Q ( $120\mu\text{A}$ ,  $6.0\text{mA}$ ,  $0\text{V}$ )    Saturation region

If  $R_b = 300\text{k}\Omega$ ,  $R_c = 5\text{k}\Omega$

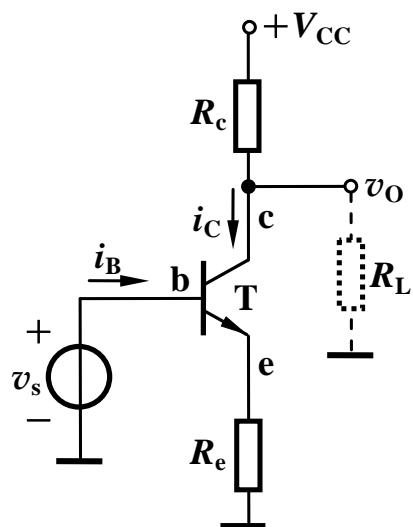
Q ( $40\mu\text{A}$ ,  $2.4\text{mA}$ ,  $0\text{V}$ )    Saturation region



Common emitter

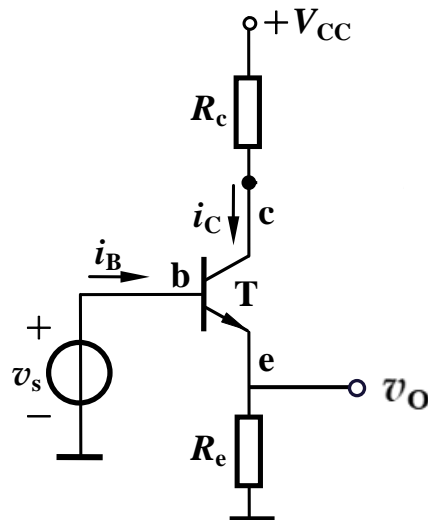

Common collector

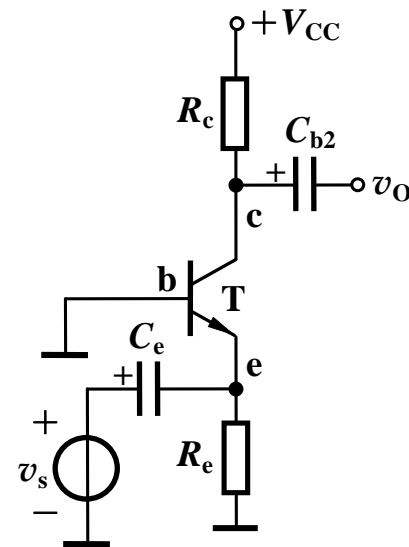

Common base

Common emitter: signal is input from the base, and output from the collector;

Common collector: signal is input from the base, and output from the emitter;

Common base: signal is input from the emitter, and output from the collector;



*Thanks*