



$$i_C = f(u_{CE}) \Big|_{I_B}$$

Saturation

Saturation region: i_c is mainly controlled by v_{ce} , $\beta i_b > i_c$

$$V_{BE} = 0.7V, V_{CE} < 1V$$

Active


Active region: i_c is basically parallel with v_{ce} , $\beta i_b = i_c$

$$V_{BE} = 0.7V, V_{CE} > 1V$$

Cutoff


Cutoff region: i_c is approaching to 0, $i_b \approx i_c \approx 0$

$$V_{BE} < 0.5V$$

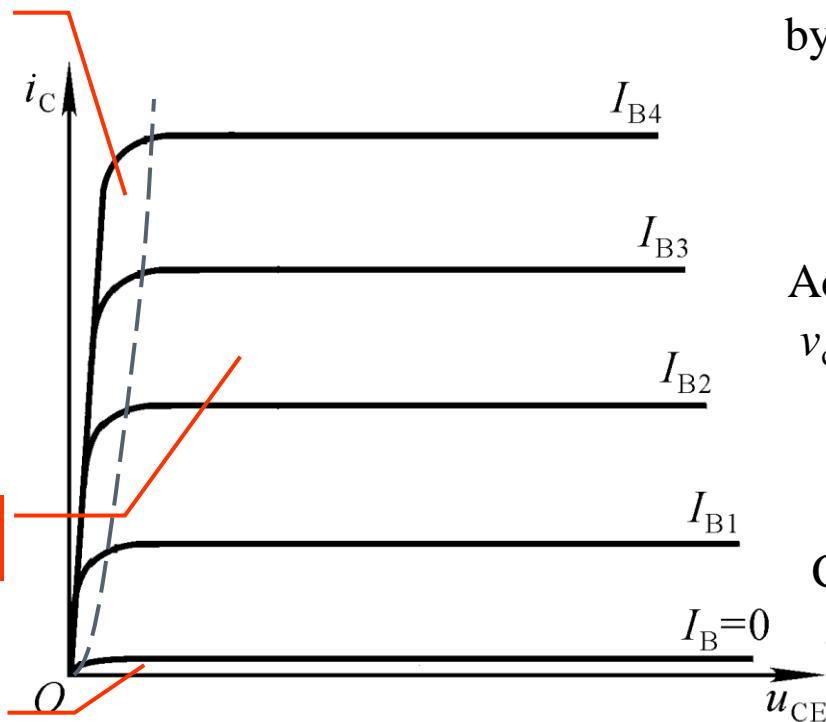




Early effect:

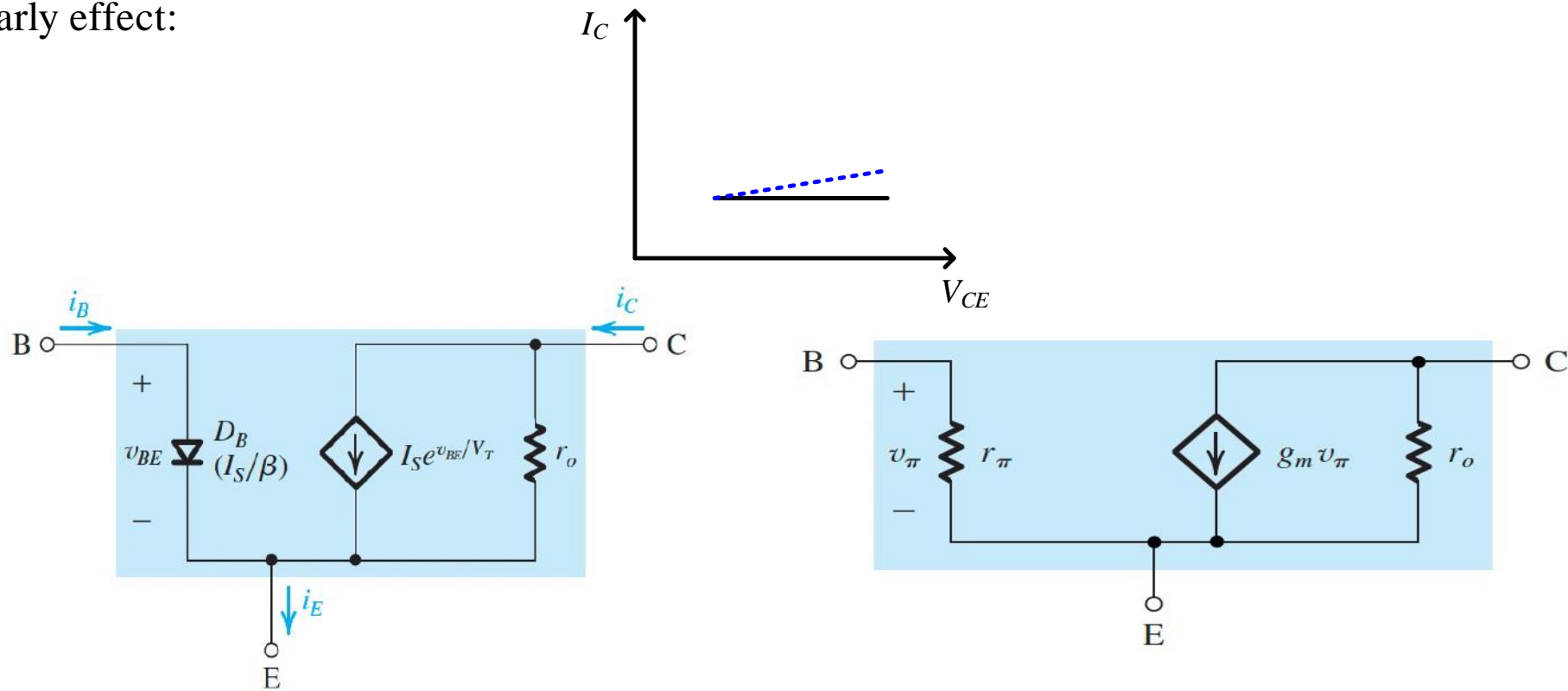


$$r_o = \frac{V_A}{I_S e^{\frac{v_{BE}}{V_T}}} \approx \frac{V_A}{I_C}$$




For DC signal:

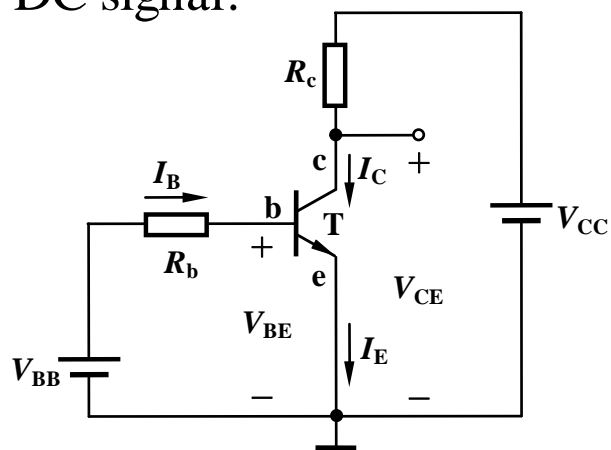

Simplified

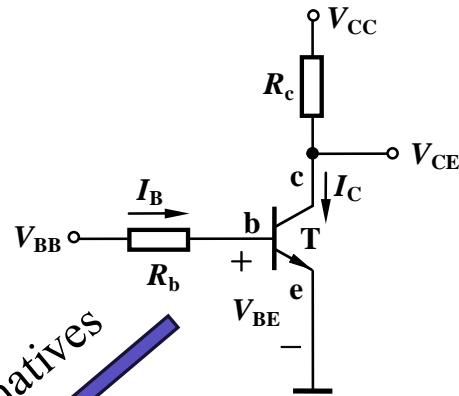

Alternatives

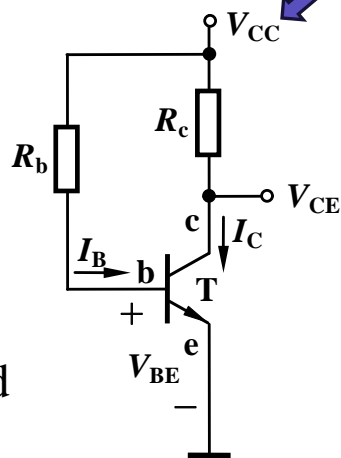

Only one DC
power is involved

Q point:

$$I_{BQ} = \frac{V_{CC} - V_{BEQ}}{R_b}$$

$$I_{CQ} = \beta \cdot I_{BQ}$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_c$$

Bipolar Junction Transistors

Peng Mei

Department of Electronic Systems

Email: mei@es.aau.dk



AALBORG UNIVERSITY
DENMARK





Learning objectives:

- Transistor-based amplifier
- Lab session



Using a diagram to analyze a BJT amplification circuit:

First step: draw the DC circuit

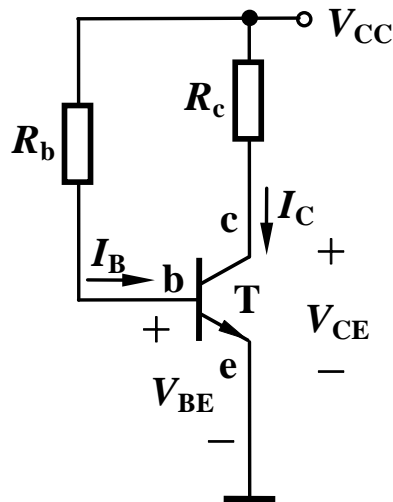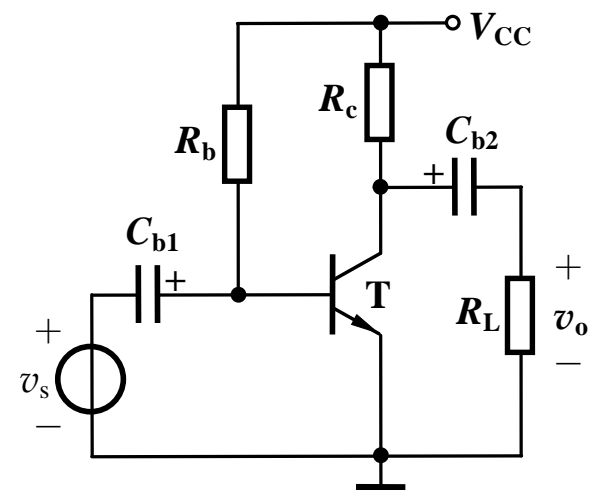

Input $i - v$ curve:

$$v_{BE} = V_{CC} - i_B R_b$$


Output $i - v$ curve:
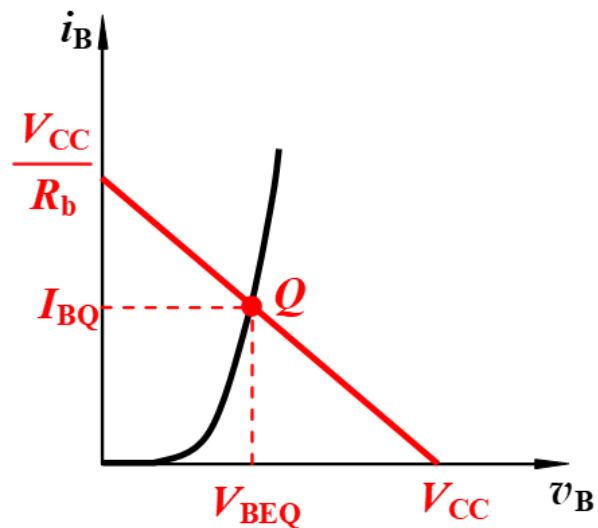
$$v_{CE} = V_{CC} - i_C R_c$$

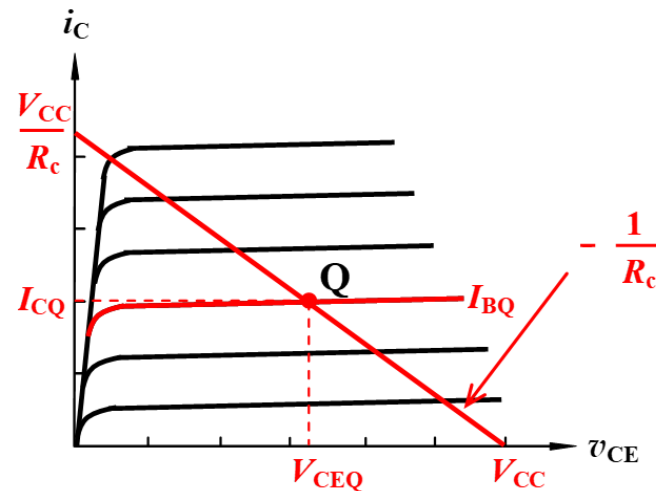


Diagram analysis of static operating point :

$$v_{BE} = V_{CC} - i_B R_b$$





$$v_{CE} = V_{CC} - i_C R_c$$







Effects of temperature on Q point :

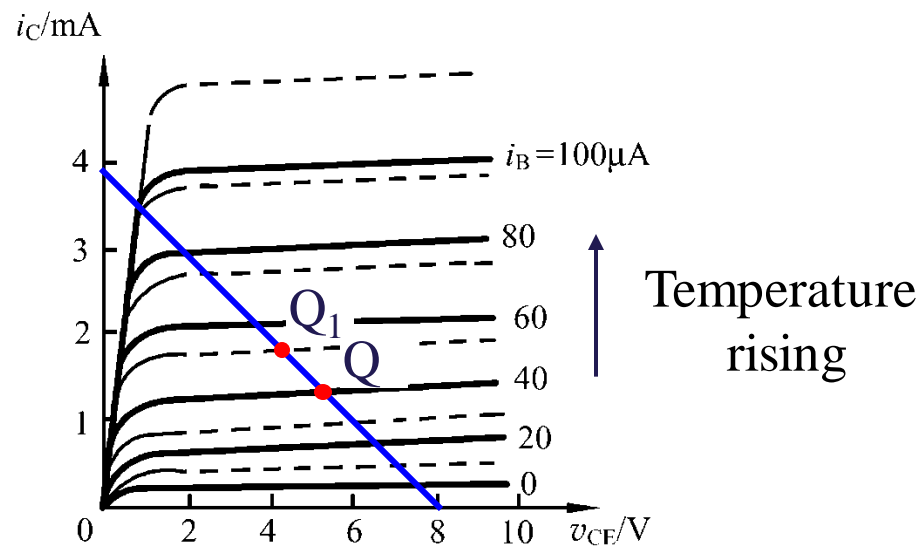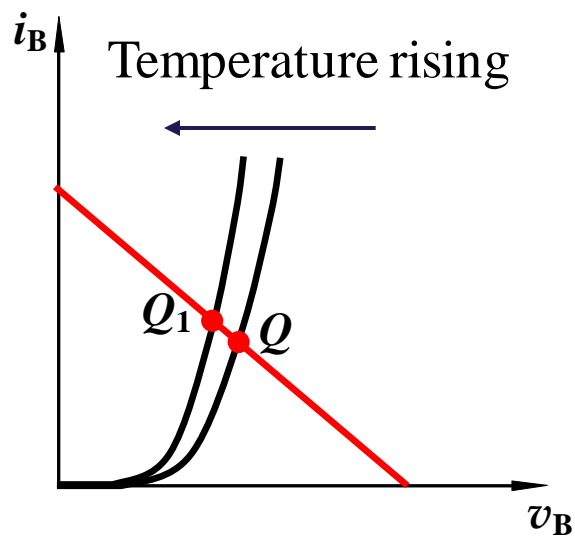




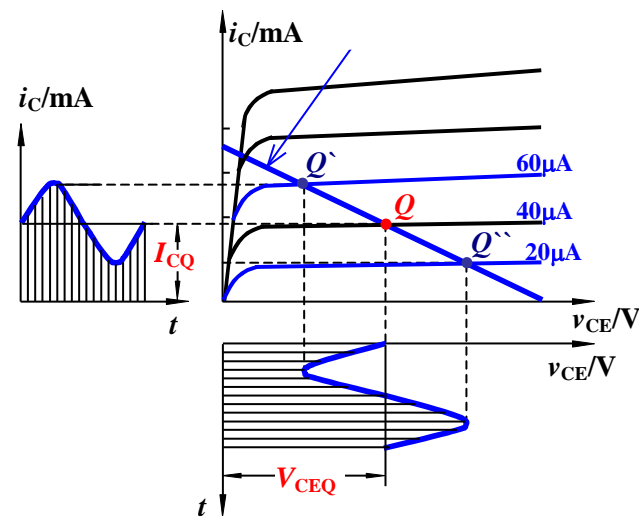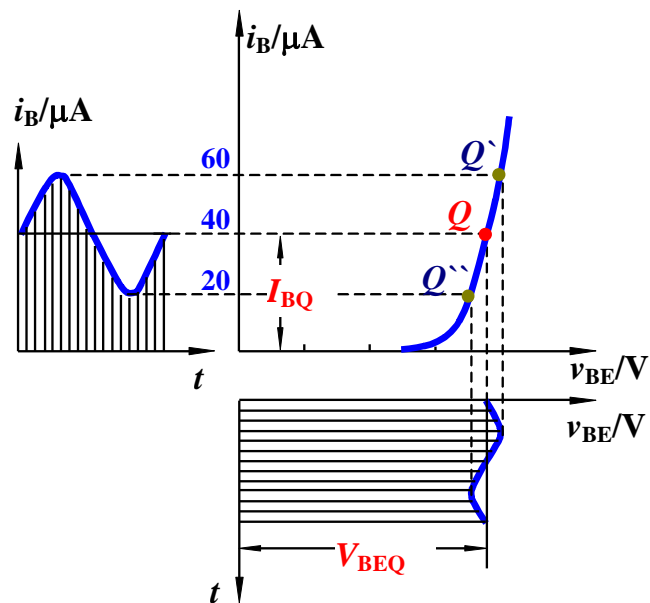The effects of Q point on waveform distortion:






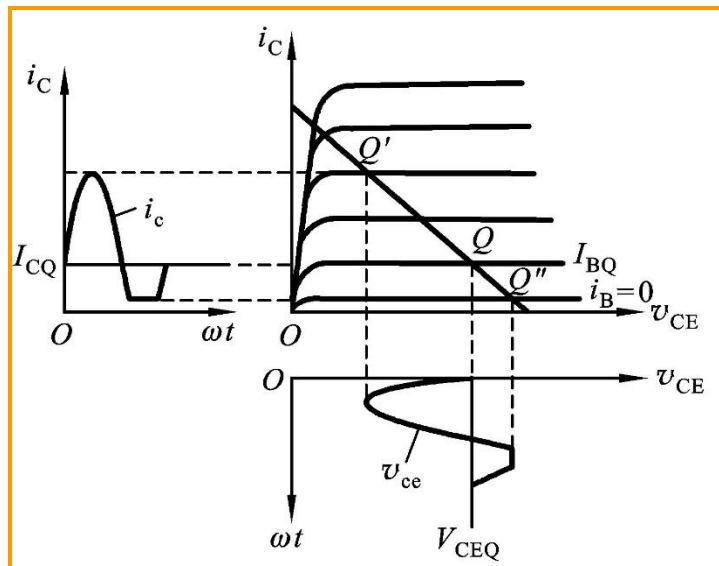
The effects of Q point on waveform distortion:



Cutoff distortion


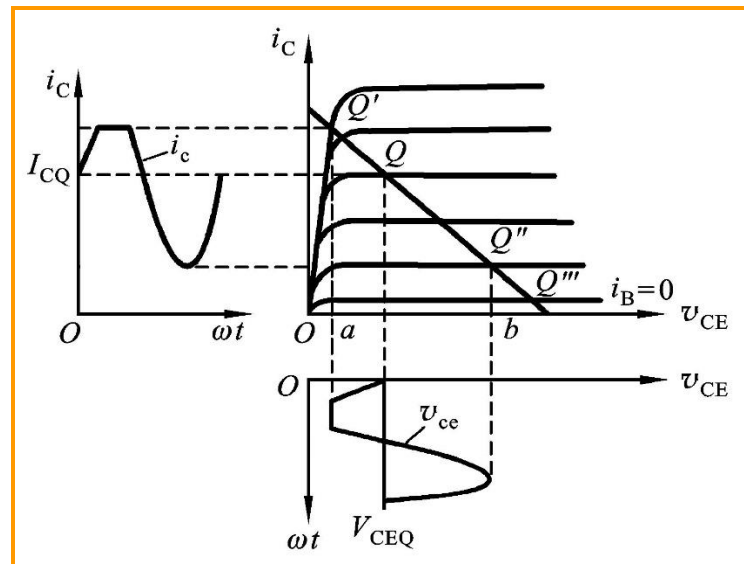


Saturation distortion

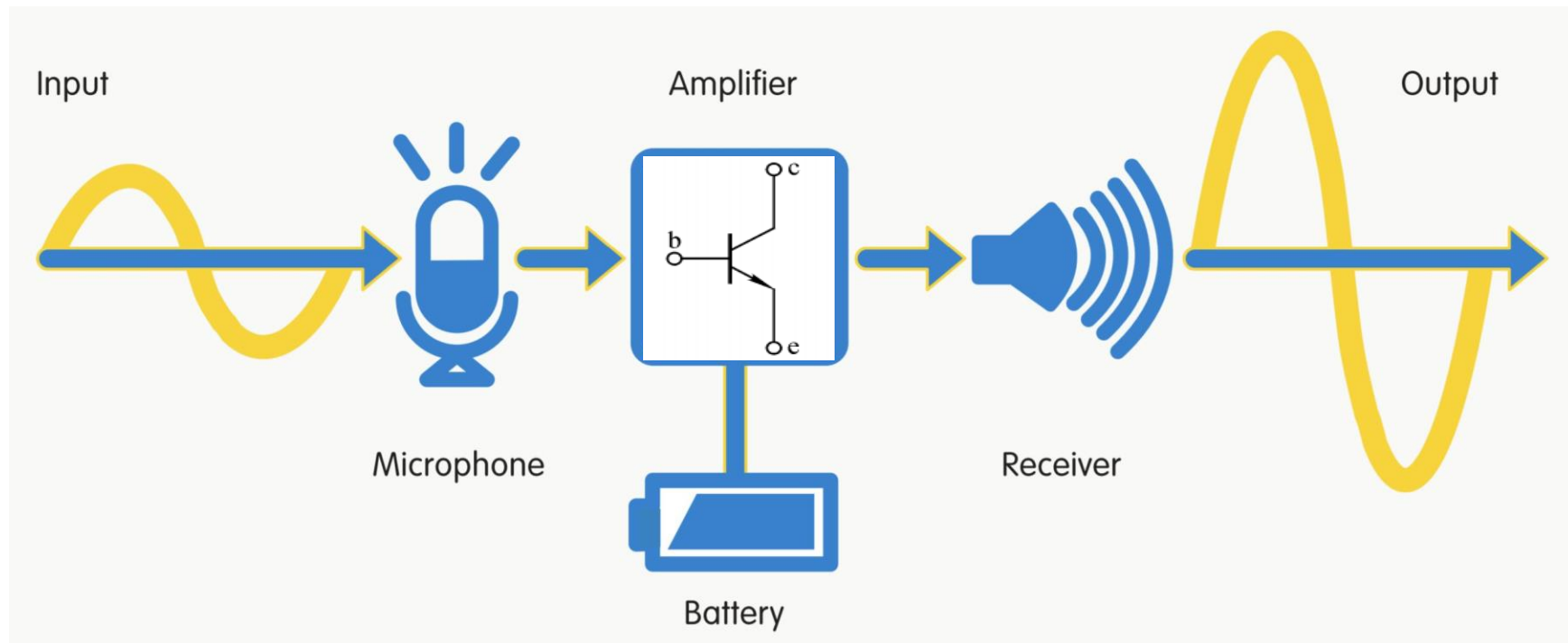





For the AC signal diagram:

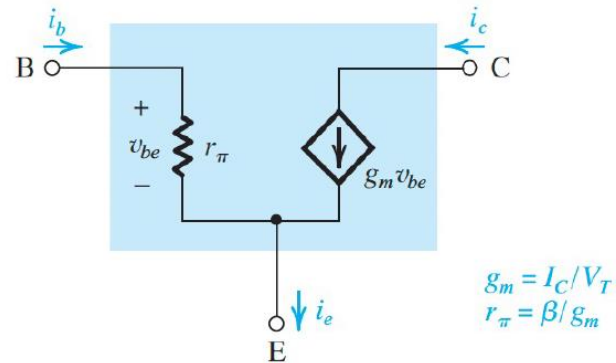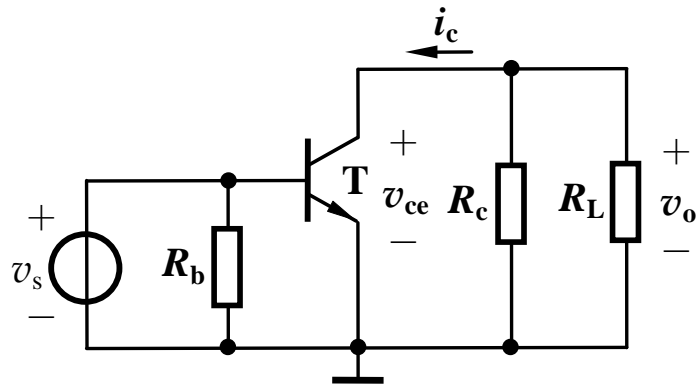

Small-signal model of a BJT

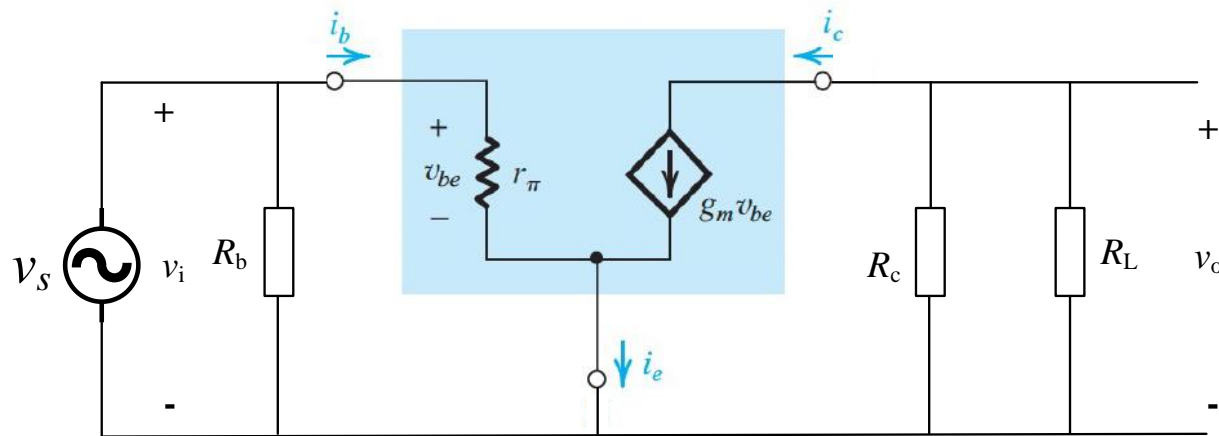

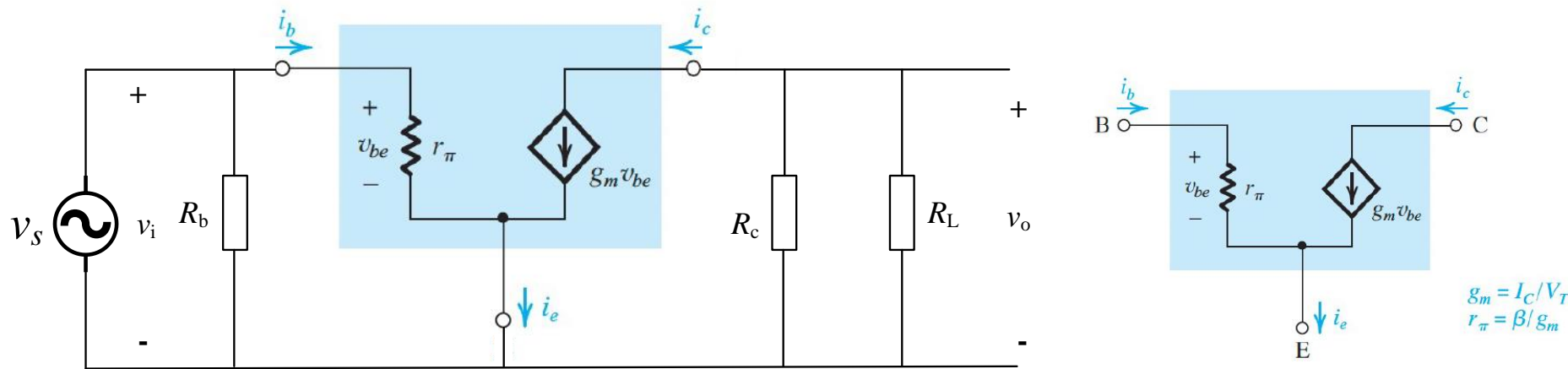

$$v_i = v_{be} = i_b r_\pi$$

$$i_c = g_m v_{be} = g_m i_b r_\pi = g_m i_b \beta / g_m$$
$$= \beta i_b$$



$$v_o = -i_c \cdot \left(\frac{R_c R_L}{R_c + R_L} \right)$$

AC small-signal amplification coefficient:

$$A_V = \frac{v_o}{v_i} = \frac{-i_c \cdot \left(\frac{R_c R_L}{R_c + R_L} \right)}{i_b r_\pi} = -\frac{\beta \cdot R_c R_L}{r_\pi (R_c + R_L)}$$



Input and output impedances:

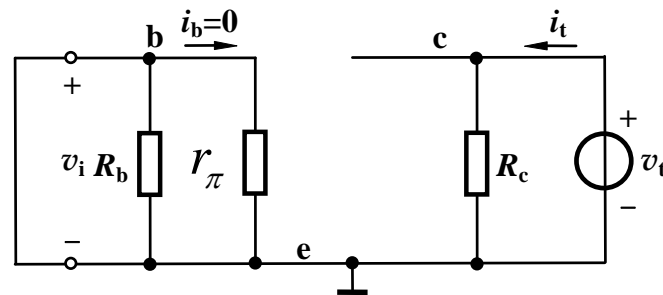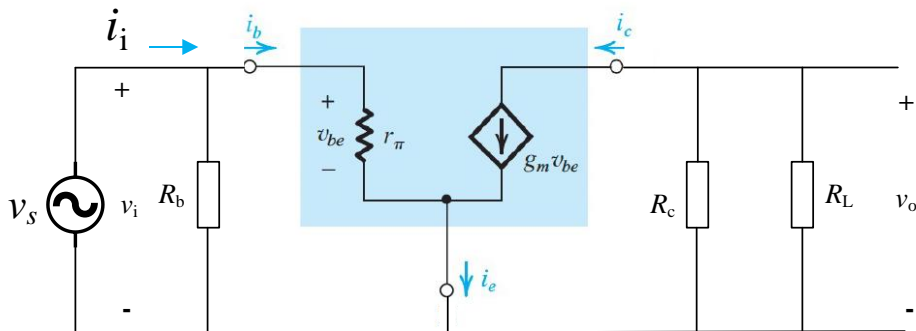

Input impedance:

$$R_i = \frac{v_i}{i_i} = \frac{R_b r_\pi}{R_b + r_\pi}$$

Output impedance:


$$R_o = \left. \frac{v_t}{i_t} \right|_{v_s=0, R_L=\infty} = R_c$$

R_L is replaced with a voltage source (v_t):

Input source is short:



For a more complicated circuit:

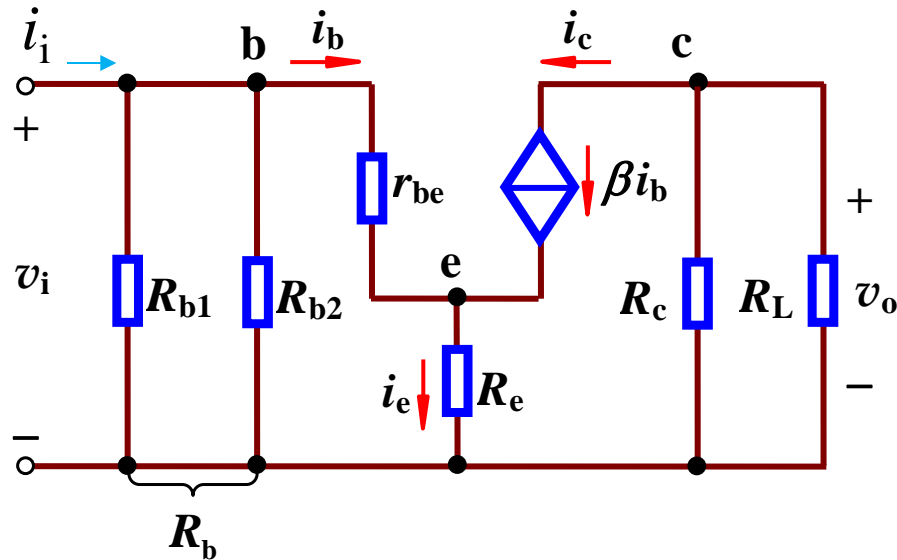

Input impedance:

$$R_i = \frac{v_i}{i_i}$$


$$R_i = R_{b1} \parallel R_{b2} \parallel [r_{be} + (1 + \beta)R_e]$$

Output impedance:

$$R_o = \left. \frac{v_t}{i_t} \right|_{v_s=0, R_L=\infty} \approx R_c$$





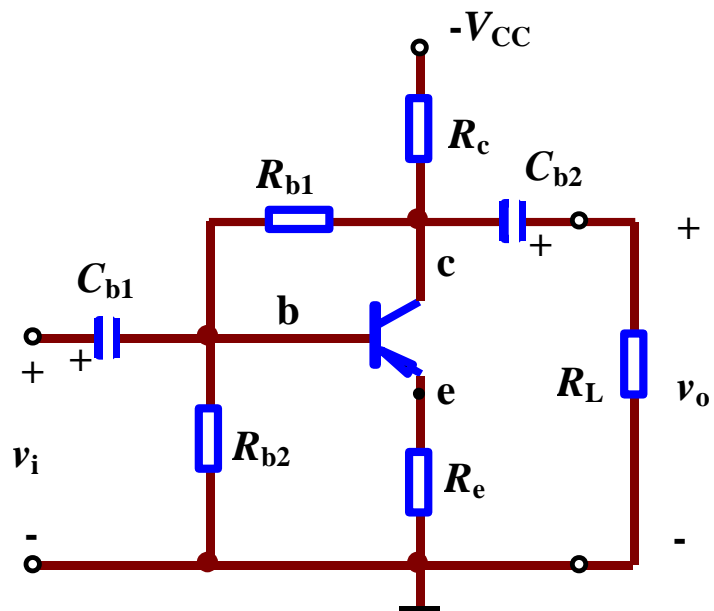
Please draw the corresponding small-signal equivalent circuit:





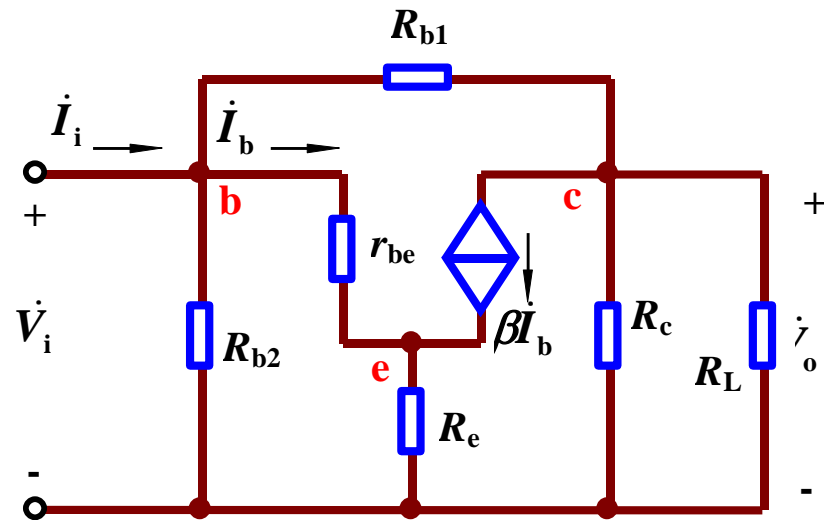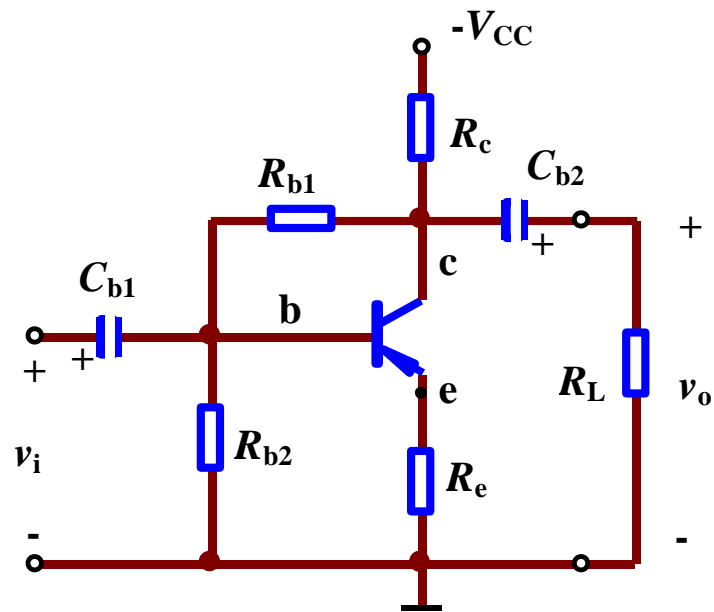Please draw the corresponding small-signal equivalent circuit:



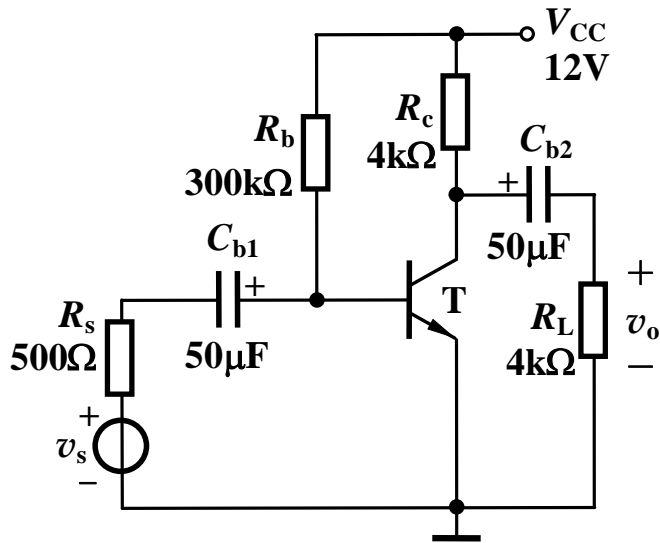


$$\beta = 50$$

a. Calculate Q point ?



b. Calculate AC small-signal amplification coefficient ?

Draw the small-signal equivalent circuit

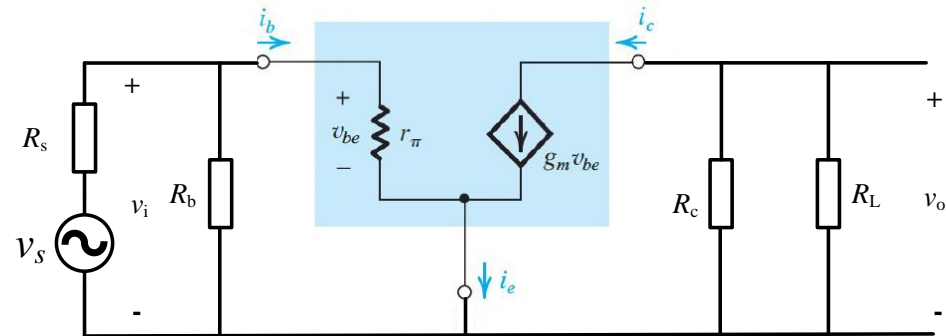



For a more complicated BJT circuit:

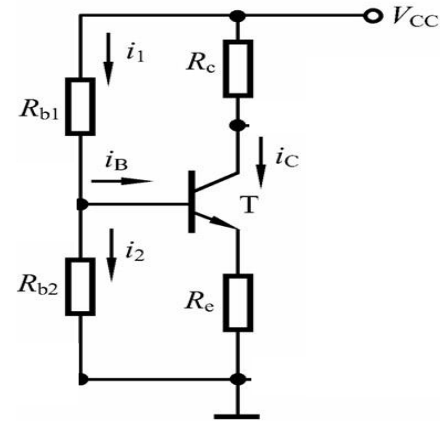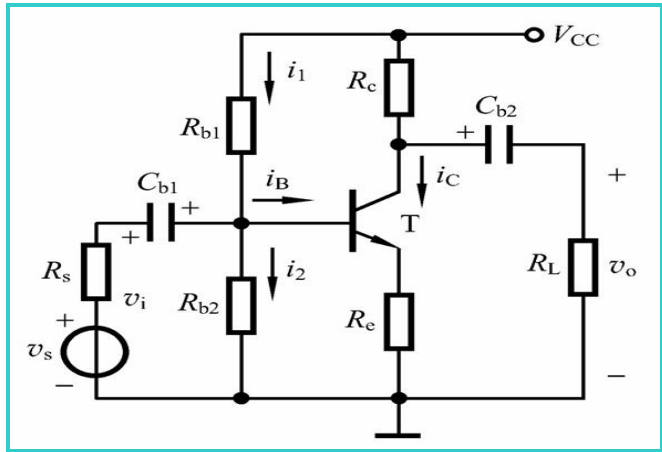

DC circuit

Q point:

$$V_{BQ} \approx \frac{R_{b2}}{R_{b1} + R_{b2}} \cdot V_{CC}$$



$$I_{CQ} \approx I_{EQ} = \frac{V_B - V_{BEQ}}{R_e}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta}$$

$$V_{CEQ} \approx V_{CC} - I_{CQ}(R_c + R_e)$$



For a more complicated BJT circuit:

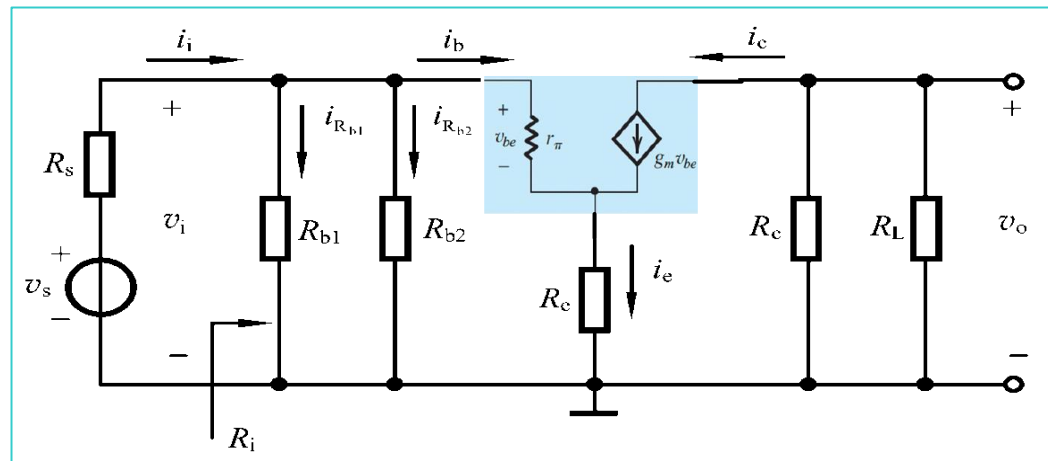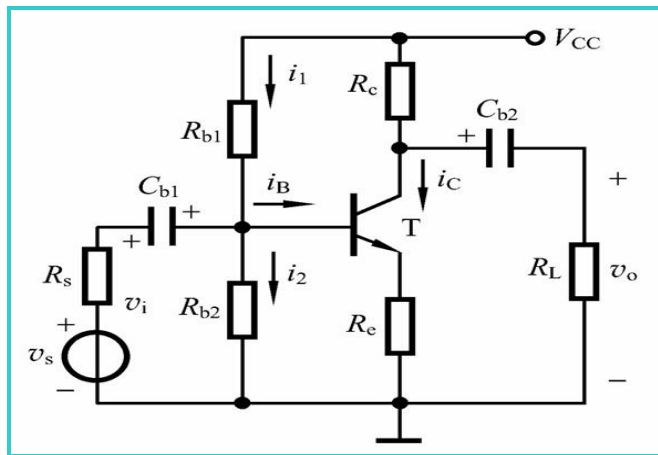

AC circuit

$$v_i = v_{be} + i_e R_e = i_b r_\pi + i_e R_e = i_b r_\pi + (1 + \beta) i_b R_e$$


$$i_c = g_m v_{be} = g_m i_b r_\pi = g_m i_b \beta / g_m \\ = \beta i_b$$

$$v_o = -i_c \cdot \left(\frac{R_c R_L}{R_c + R_L} \right)$$

$$A_V = \frac{v_o}{v_i} = \frac{-i_c \cdot \left(\frac{R_c R_L}{R_c + R_L} \right)}{i_b r_\pi + (1 + \beta) i_b R_e} = - \frac{\beta \cdot R_c R_L}{(r_\pi + (1 + \beta) R_e)(R_c + R_L)}$$



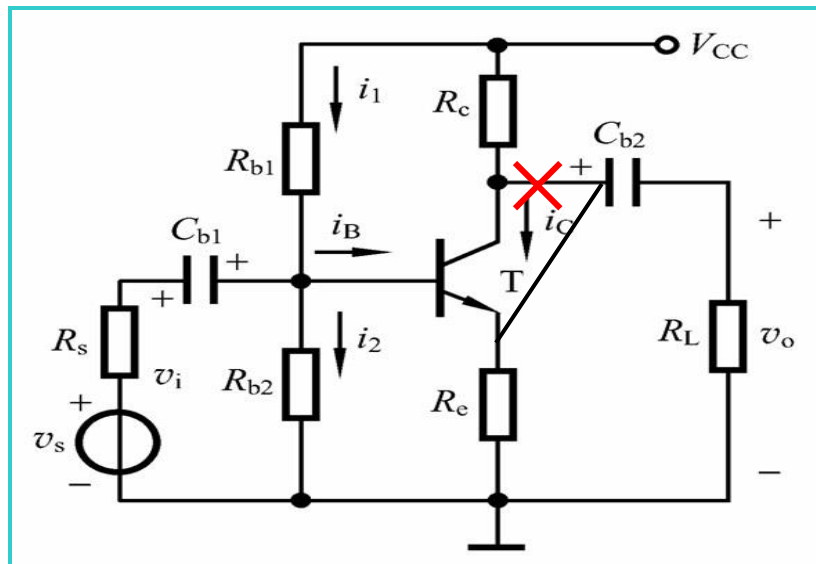
Formulate the voltage amplification coefficient:



Interesting results found here!




Lab session:

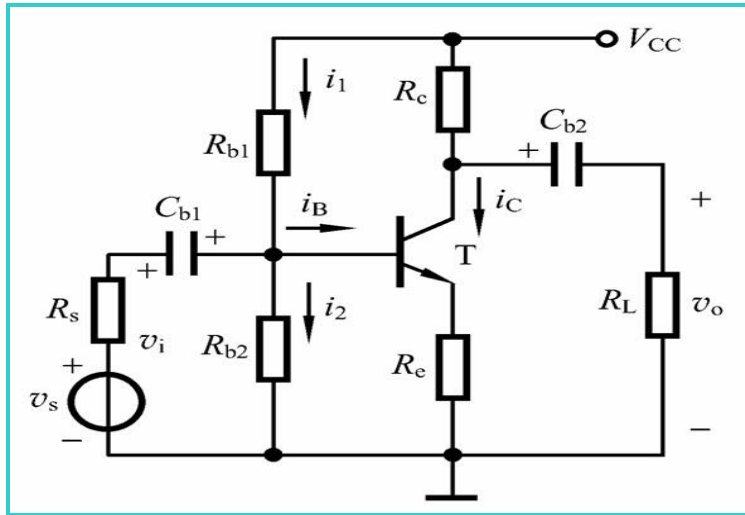

$V_{CC} = 15 \text{ V}$, $R_{b1} = 309 \text{ k}\Omega$, $R_{b2} = 110 \text{ k}\Omega$,
 $R_e = 3.01 \text{ k}\Omega$, $R_c = 6.98 \text{ k}\Omega$, $C_{b1} = 1 \text{ }\mu\text{F}$,
 $C_{b2} = 1 \text{ }\mu\text{F}$, $R_L = 10 \text{ k}\Omega$.




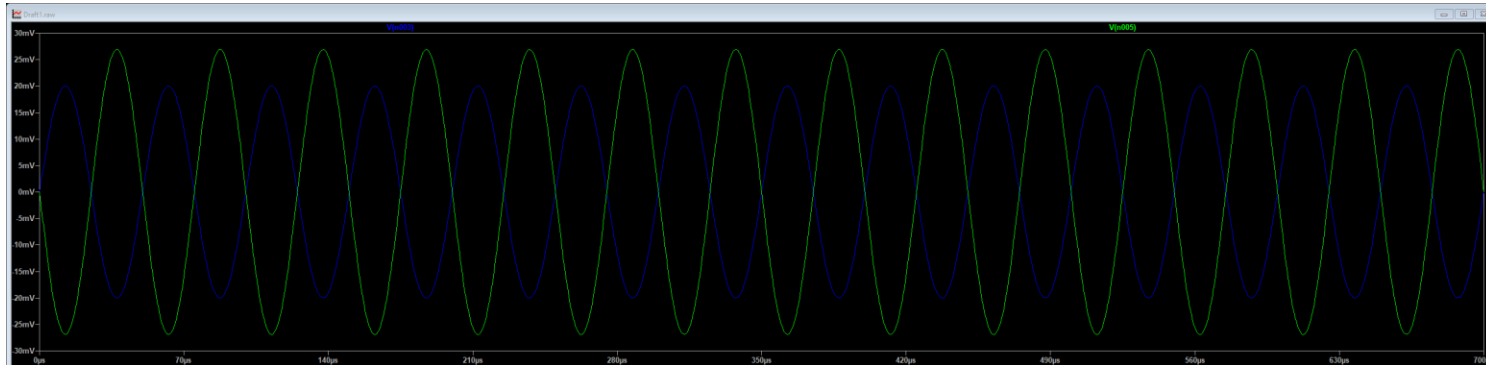If $v_s = 20\sin(2\pi f)$ mV, $f = 20$ kHz, please measure v_i and v_o , and calculate the amplitude amplification coefficient A_v .






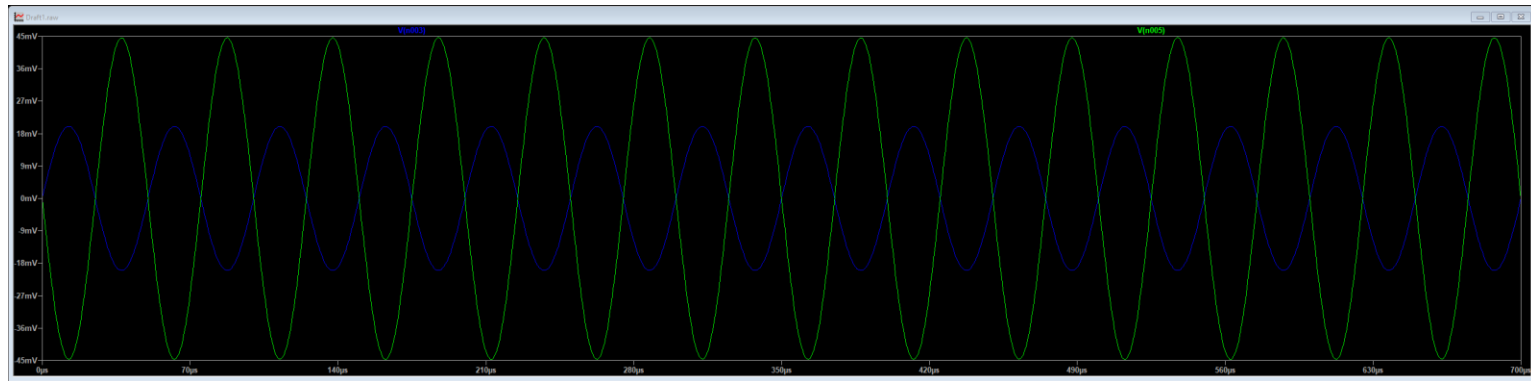If $R_L = 300 \text{ k}\Omega$, please please measure v_i and v_o , and calculate the amplitude amplification coefficient A_v .





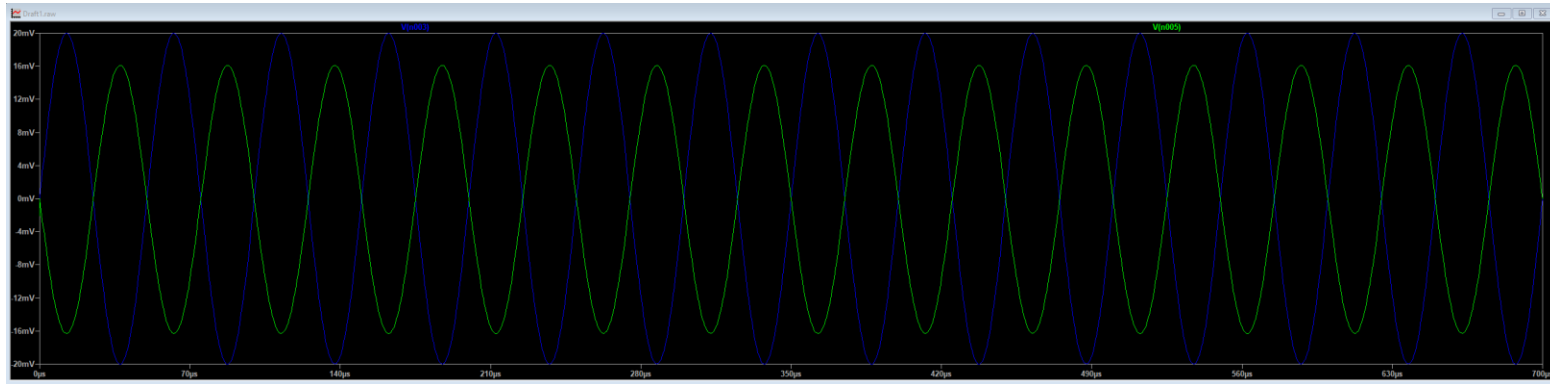If $R_e = 5 \text{ k}\Omega$, please measure v_i and v_o , and calculate the amplitude amplification coefficient A_v .





Thanks