

Literature:

Frequency response: p 679-706 p716-740

Nonlinearity: the book does not adequately support this topic, which is why the notes, accessible from the course page, are the only literature.

Assignments:

9.1:

Use the short-circuit time constant method to determine the capacitor values of  $C_1$ ,  $C_2$  and  $C_3$ , so that  $f_L = 100$  Hz can be achieved for the circuit in Fig. 1. Where  $g_m = 3.82 \cdot 10^{-2}$ ,  $\beta = 301$ .

Hint:  $r_\pi = \beta/g_m$ ,  $r_e = 1/g_m$ .

- (1)  $C_1$ ,  $C_2$  and  $C_3 = ?$
- (2) Run the LTspice simulation to check your calculation by comparing with the simulated  $f_L$ .
- (3) Run the LTspice simulation to find the  $f_H$ .
- (4) Run the LTspice simulation to observe harmonic distortion.

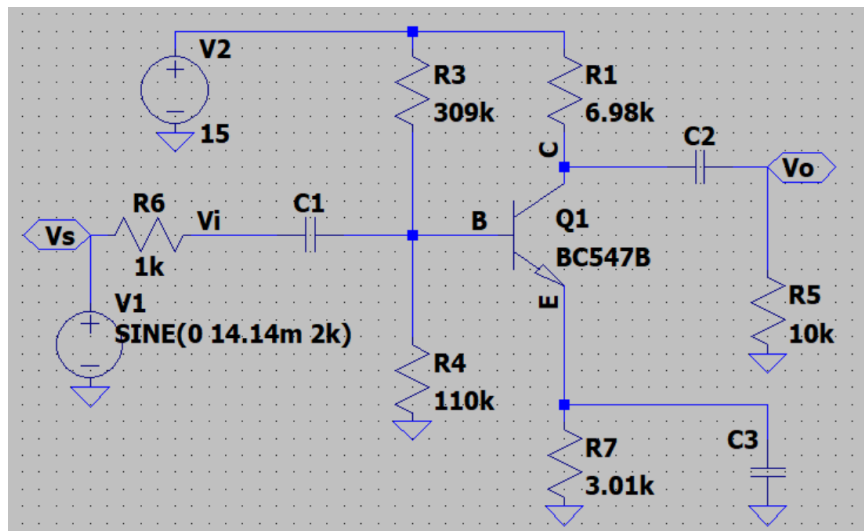


Fig. 1 A CE stage

Solution:

(1)

$$f_{C_1} = f_{C_2} = 0.1f_L = 10 \text{ Hz}$$

$$f_{C_E} = 0.8f_L = 80 \text{ Hz}$$

$$r_\pi = \frac{\beta}{g_m} = 7.88 \text{ K}\Omega$$

$$R_B = R_3 || R_4 = 81.1 \text{ K}\Omega$$

$$R_E = R_7 = 3.01 \text{ K}\Omega$$

$$R_{C_1} = (R_B || r_\pi) + R_{sig} = 8.18 \text{ K}\Omega$$

$$R_{C_E} = R_E || \left( \frac{1}{g_m} + \frac{R_B || R_{sig}}{\beta + 1} \right) = 29.16 \Omega$$

$$R_{C_2} = R_C + R_L = R_1 + R_5 = 16.98 \text{ K}\Omega$$


$$2\pi f_{C_1} = \frac{1}{C_{C_1} R_{C_1}} \rightarrow C_{C_1} = \frac{1}{2\pi f_{C_1} R_{C_1}} = 1.94 \mu\text{F}$$

$$2\pi f_{C_E} = \frac{1}{C_{C_E} R_{C_E}} \rightarrow C_{C_E} = \frac{1}{2\pi f_{C_E} R_{C_E}} = 68.2 \mu\text{F}$$


$$2\pi f_{C_2} = \frac{1}{C_{C_2} R_{C_2}} \rightarrow C_{C_2} = \frac{1}{2\pi f_{C_2} R_{C_2}} = 0.94 \mu\text{F}$$

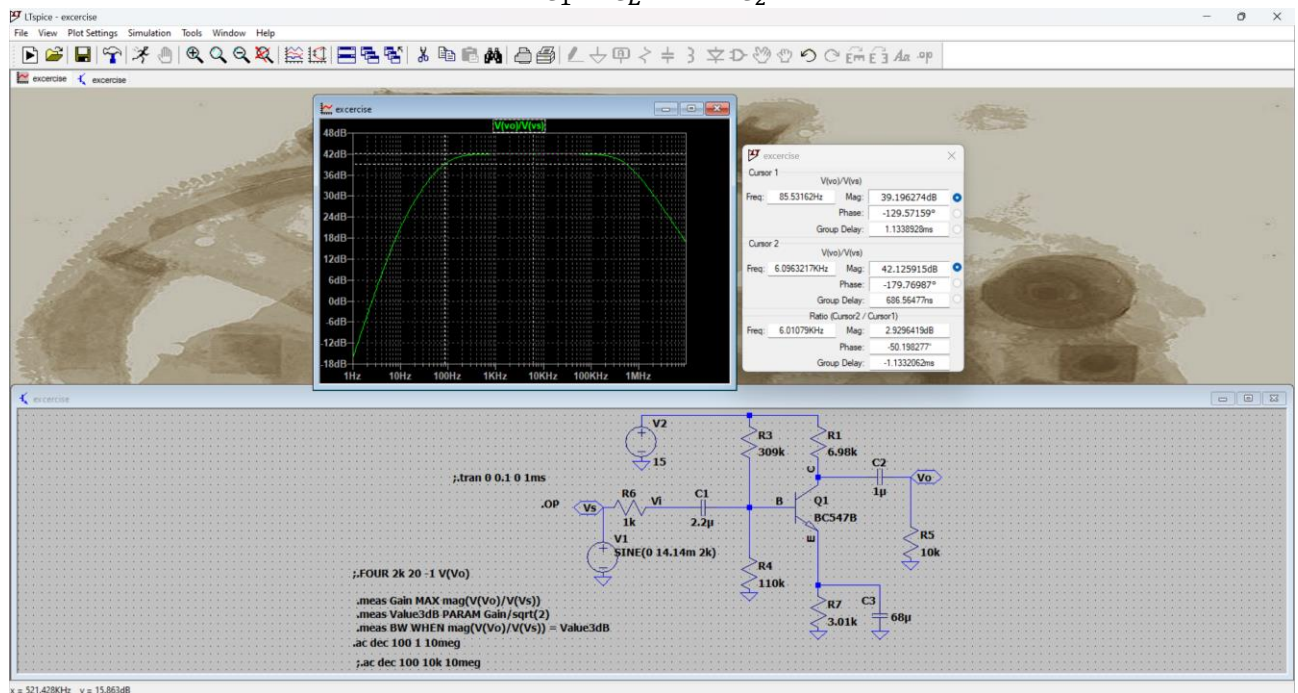(2)


Select the standard capacitors for  $C_{C_1}$ ,  $C_{C_E}$  and  $C_{C_2}$ .



(3)

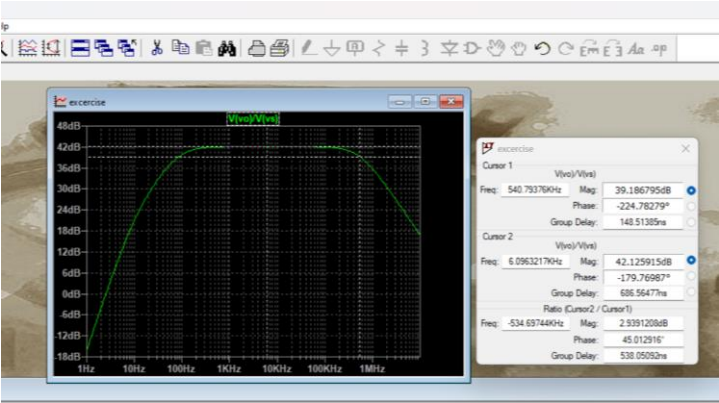

(4)

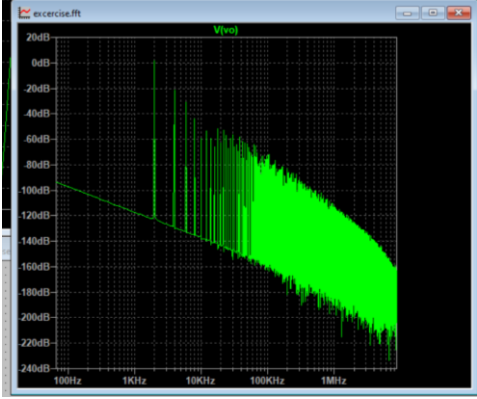

Total Harmonic Distortion: 7.589737%